

VE215

Quiz #5


Chapter 10 to Chapter 11 are covered in this quiz.

Problem #1

Please calculate the RMS values of the following signals:

(1) $V_0(t) = 1 + 2\sin(100t + 30^\circ)$ V

(2) $I_0(t)$ (See the graph below)

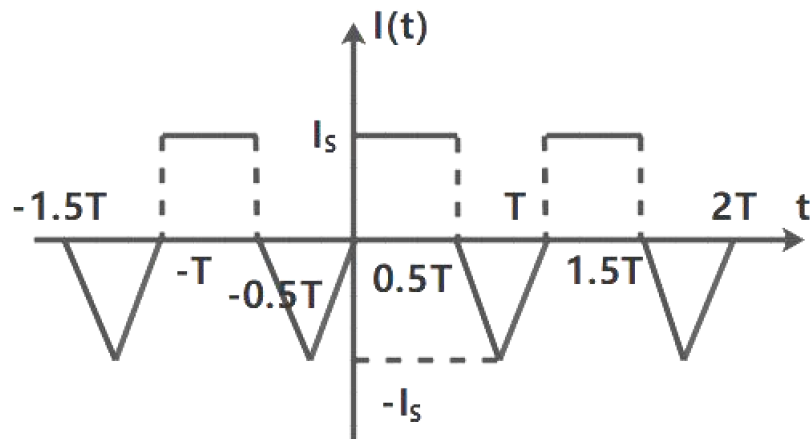

Problem #2

For a linear circuit, suppose the Thevenin's equivalent voltage is V_{TH} and the equivalent impedance is $Z_{eq} = R_{eq} + jX_{eq}$. If we'd like to connect another impedance Z_L as the load, please derive the expression of Z_L that will absorb the maximum power and the expression of that maximum power if

(1) $R_{eq} > 0$

(2) $R_{eq} < 0$