

# Ve215 Introduction to Circuits

## Homework 8



JOINT INSTITUTE

交大密西根学院

Please name your file as *NAME\_HW8\_STUDENTID*.

In order to receive full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.

**Exercise 8.1** (30%) Find the transfer function  $H(\omega) = V_o/V_i$  of the circuits.


(a)  $R \parallel \frac{1}{j\omega C} = \frac{R}{1 + j\omega RC}$

$$H(\omega) = \frac{V_o}{V_i} = \frac{\frac{R}{1 + j\omega RC}}{j\omega L + \frac{R}{1 + j\omega RC}} = \frac{R}{R + j\omega L(1 + j\omega RC)}$$


$$H(\omega) = \frac{R}{-\omega^2 RLC + R + j\omega L}$$

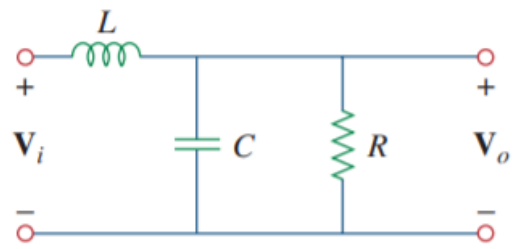(b)  $H(\omega) = \frac{R + j\omega L}{R + j\omega L + 1/j\omega C} = \frac{j\omega C(R + j\omega L)}{1 + j\omega C(R + j\omega L)}$

$$H(\omega) = \frac{-\omega^2 LC + j\omega RC}{1 - \omega^2 LC + j\omega RC}$$



(a)

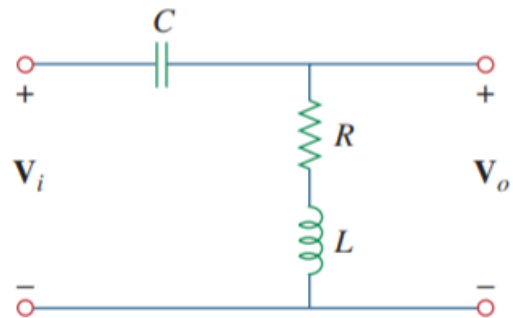

(b)

**Exercise 8.2** (30%) Sketch the bode plots for


$$H(\omega) = \frac{250(j\omega + 1)}{j\omega(-\omega^2 + 10j\omega + 25)}$$

$$\mathbf{H}(\omega) = \frac{250}{25} \frac{1 + j\omega}{j\omega \left( 1 + \frac{j\omega 10}{25} + \left( \frac{j\omega}{5} \right)^2 \right)}$$


$$H_{dB} = 20 \log_{10} 10 + 20 \log_{10} |1 + j\omega| - 20 \log_{10} |j\omega| \\ - 20 \log_{10} \left| 1 + j\omega 2/5 + (j\omega/5)^2 \right|$$

$$\phi = -90^\circ + \tan^{-1} \omega - \tan^{-1} \left( \frac{\omega 10/25}{1 - \omega^2/5} \right)$$

**The magnitude and phase plots are shown below.**

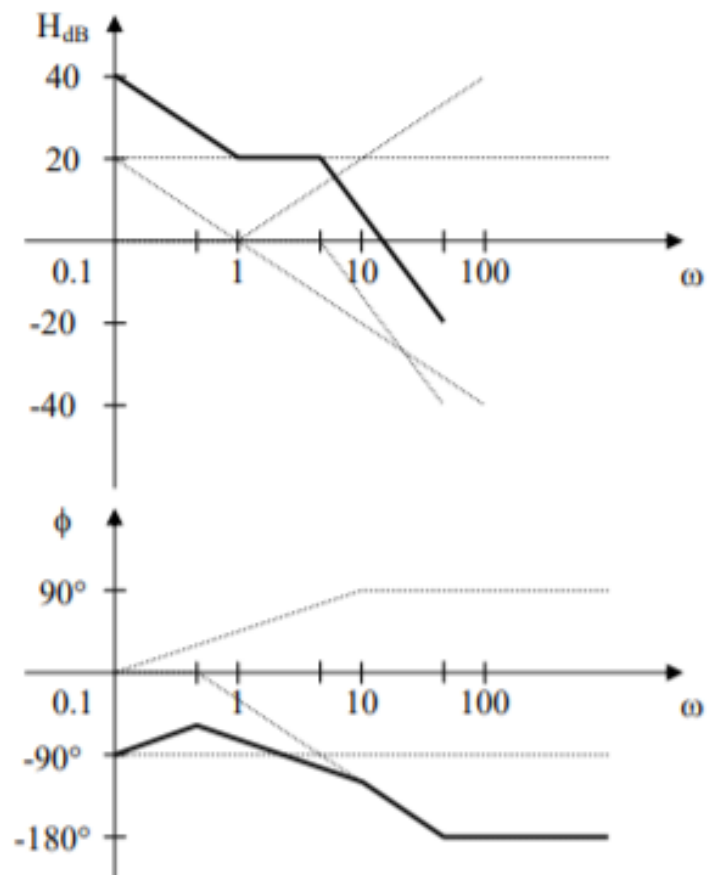

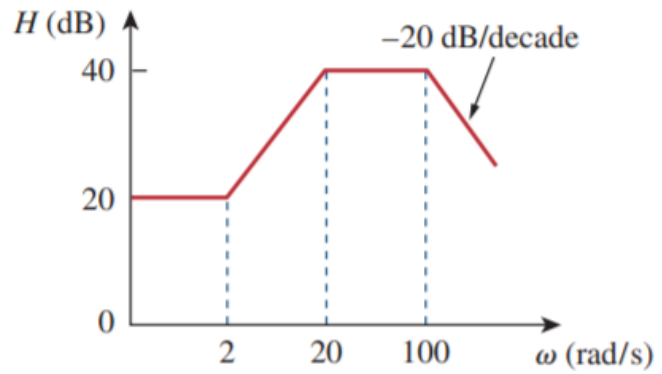**Exercise 8.3** (30%) Find the transfer function  $H(\omega)$  with the Bode magnitude plot



$$20 = 20 \log_{10} k \longrightarrow k = 10$$

$$\text{A zero of slope } +20 \text{ dB/dec at } \omega = 2 \longrightarrow 1 + j\omega/2$$

$$\text{A pole of slope } -20 \text{ dB/dec at } \omega = 20 \longrightarrow \frac{1}{1 + j\omega/20}$$

$$\text{A pole of slope } -20 \text{ dB/dec at } \omega = 100 \longrightarrow \frac{1}{1 + j\omega/100}$$

Hence,

$$\mathbf{H}(\omega) = \frac{10(1 + j\omega/2)}{(1 + j\omega/20)(1 + j\omega/100)}$$

$$\mathbf{H}(\omega) = \frac{10^4 (2 + j\omega)}{(20 + j\omega)(100 + j\omega)}$$

**Exercise 8.4** (10%) Congratulations! You've finished the last assignment of this course. You can leave whatever you want here. It's good to be with you in VE215. Good luck in the final exam!

