

ECE2150J 2025FA Assignment 6




GLOBAL COLLEGE
SHANGHAI JIAO TONG UNIVERSITY

Due Date: 23:59 December 20th


In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.

Exercise 6.1 (25%)

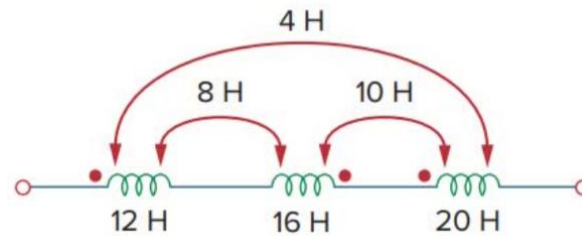(a) Find the total inductance for the three coupled coils.



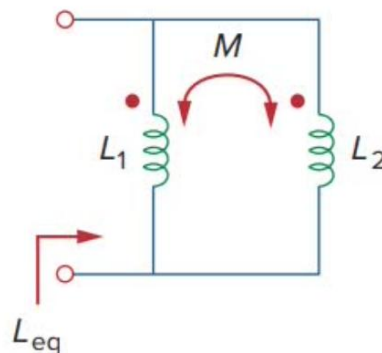(b) Find the equivalent inductance L_{eq} .




ECE2150J 2025FA Assignment 6



GLOBAL COLLEGE
SHANGHAI JIAO TONG UNIVERSITY

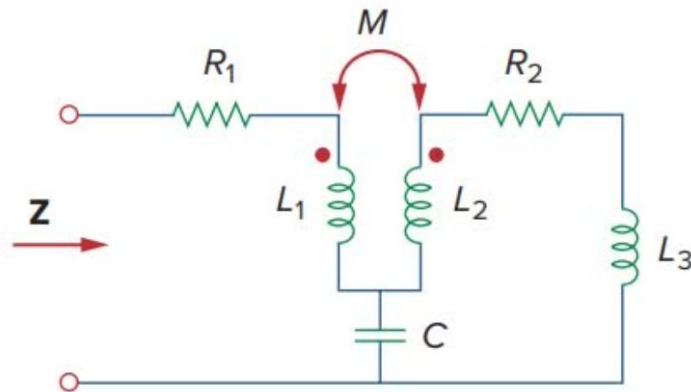Exercise 6.2 (25%)

$R_1 = R_2 = 5\text{k}\Omega$, $M = 20\text{ H}$, $L_1 = 10\text{ H}$, $L_2 = 5\text{ H}$, $L_3 = 10\text{ H}$, $C = 0.1\text{ F}$. Suppose frequency of source is $\omega = 10\text{ k rad/s}$. Find the equivalent impedance Z . All currents flow clockwise.




ECE2150J 2025FA Assignment 6



GLOBAL COLLEGE
SHANGHAI JIAO TONG UNIVERSITY

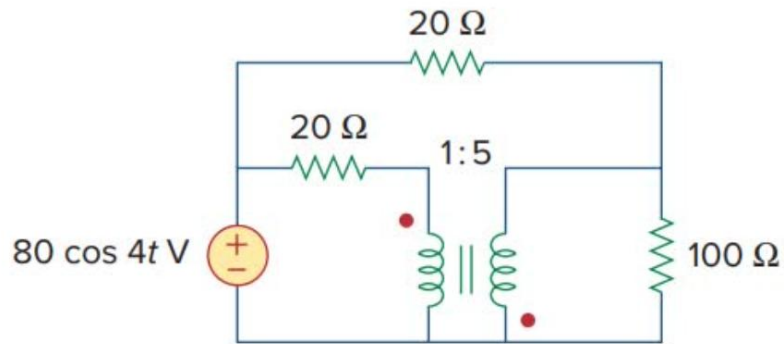Exercise 6.3 (25%)

Determine the average power absorbed by each resistor in this circuit. All currents flow clockwise.



ECE2150J 2025FA Assignment 6



GLOBAL COLLEGE
SHANGHAI JIAO TONG UNIVERSITY

Exercise 6.4 (25%)

$M = 0.2 \text{ H}$, $v_s = 12 \cos 10t \text{ V}$.

Find i_1 and i_2 . Calculate the energy stored in the coupled coils at $t = 15 \text{ ms}$.

