

# VE215 2025SU Assignment 1



**Due Date: 23:59, May.29th, 2025**

In order to get full marks, you shall write all the intermediate steps of calculation or proof, unless otherwise indicated.

**Exercise 1.1** (15%) The voltage  $v$ (unit:V) across a device and the current  $i$  (unit:A) through it are

$$v(t) = 10 \cos \frac{\pi t}{2} + 10 \quad i(t) = \begin{cases} 0 & t < 0 \\ -10t^2 + 20t & 0 \leq t < 1 \\ 10e^{-t+1} & 1 \leq t < \ln 2 + 1 \\ 5 & t \geq \ln 2 + 1 \end{cases}$$

- (a)(5%) Calculate the total charge in the device at  $t = 1.5$  s.
- (b)(5%) Calculate the power delivered to the element at  $t = 1.5$  s.
- (c)(5%) Calculate the energy delivered to the device between 3 and 5 s.

**Exercise 1.2** (25%) In the circuit below, all resistors have a resistance of  $R$ .

(a) (12%) Determine the number of branches, nodes, loops, and meshes. Write your answers directly.

(b) (13%) Calculate the equivalent resistance between the terminals.

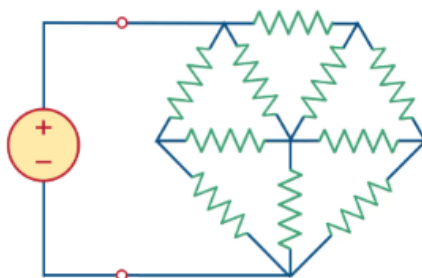


Figure 1: Exercise 1.2

(a) (10%) Calculate the unknown current  $I_x$  using mesh analysis.

3

**Exercise 1.4**(20%) Solve the following questions with the given methods.  
 (a)(10%) Using nodal analysis **by inspection**, find  $V_1$ ,  $V_2$ ,  $V_3$  and  $V_0$  in the following circuit.

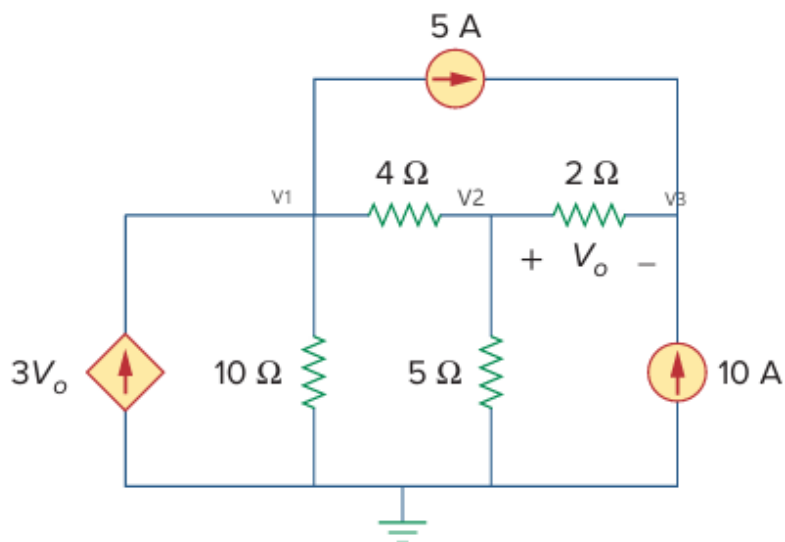


Figure 3: Exercise1.4(a)

(b)(10%) Using mesh analysis **by inspection** to solve the mesh currents in the following circuit.

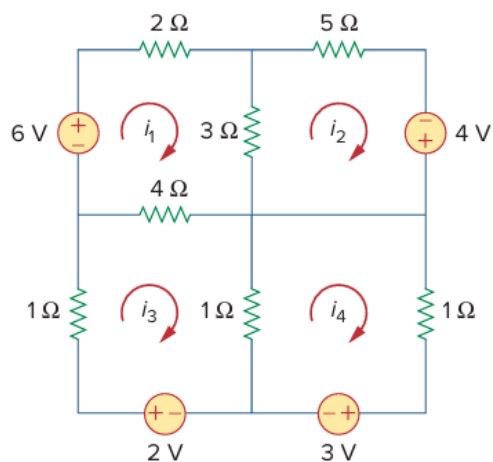


Figure 4: Exercise1.4(b)

**Exercise 1.5(15%)** For the circuit below, find the node voltages  $v_1$ ,  $v_2$ ,  $v_3$ .

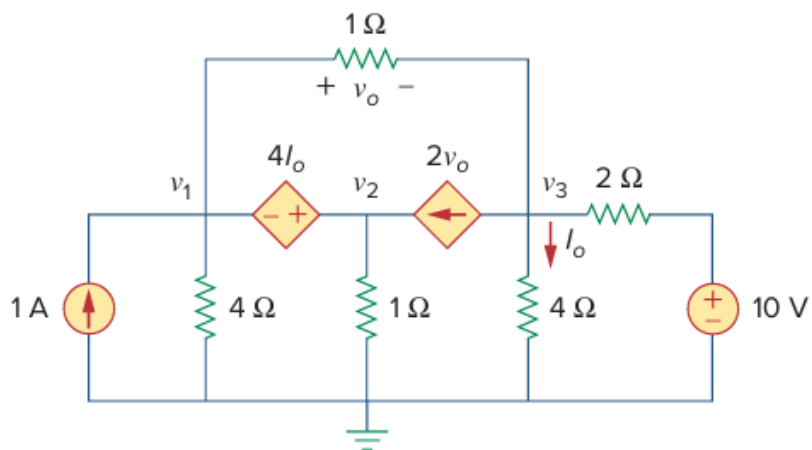


Figure 5: Exercise 1.5