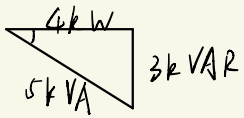


Three loads are connected in parallel across a 300 V(rms) line, as shown in Fig. P10.28. Load 1 absorbs 3 kW at unity power factor; Load 2 absorbs 5 kVA at 0.8 leading; Load 3 absorbs 5 kW and delivers 6 kvars.

- Find the impedance that is equivalent to the three parallel loads.
- Find the power factor of the equivalent load as seen from the line's input terminals.

$$a) S_1 = 3 \text{ kW}$$

$$|S_2| = 5 \text{ kVA} \Rightarrow S_2 = 4 \text{ k} - j3 \text{ k}$$




$$S_3 = 5 \text{ k} - j6 \text{ k}$$

$$S = S_1 + S_2 + S_3 = 12 \text{ k} - j9 \text{ k}$$

$$300 \tilde{I}_{rms}^* = (12 - j9) \times 10^3 \quad \tilde{I}_{rms} = 40 + j30 \text{ A}$$

$$Z = \frac{300}{40 + j30} = 4.8 - j3.6 = 6 \angle -36.87^\circ$$
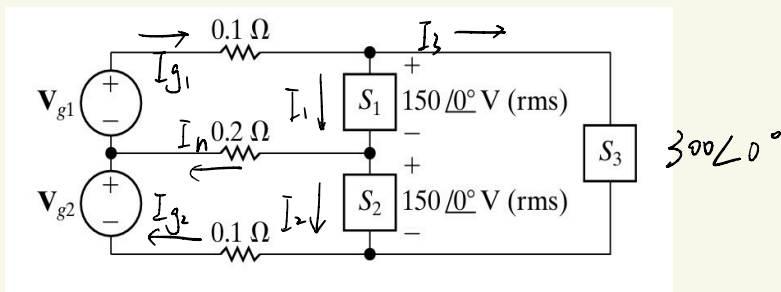
$$(b) \text{ pf} = \cos(-36.87^\circ) = 0.80 \text{ leading.}$$



$$S_1 = (6 + j3)k \quad S_2 = (7.5 - j4.5)k \quad S_3 = (12 + j9)k$$

$$\tilde{V}_1 = 150 \angle 0^\circ \Rightarrow \tilde{I}_1 = \left(\frac{S_1}{\tilde{V}_1} \right)^* = \frac{(6 - j3)k}{150} = 40 - j20 \text{ A}$$

$$\tilde{I}_2 = \left(\frac{S_2}{\tilde{V}_2} \right)^* = \frac{(7.5 + j4.5)k}{150} = 50 + j30 \text{ A}$$

$$\tilde{I}_3 = \frac{(12 - j9)k}{300} = 40 - j30 \text{ A}$$

$$\tilde{I}_{g1} = \tilde{I}_1 + \tilde{I}_3 = 80 - j50 \text{ A}$$

$$\tilde{I}_n = \tilde{I}_1 - \tilde{I}_2 = -10 - j50 \text{ A}$$

$$\tilde{I}_{g2} = \tilde{I}_2 + \tilde{I}_3 = 90 + j0 \text{ A}$$


$$\tilde{V}_{g1} = 0.1 \tilde{I}_{g1} + 150 + 0.2 \tilde{I}_n = 156 - j15 \text{ V (rms)}$$

$$\tilde{V}_{g2} = -0.2 \tilde{I}_n + 150 + 0.1 \tilde{I}_{g2} = 161 + j10 \text{ V (rms)}$$

$$S_{g1} = -[(156 - j15)(80 + j50)] = -13230 - j6600 \text{ VA}$$

$$S_{g2} = -[(161 + j10)(90 + j0)] = -14490 - j900 \text{ VA}$$

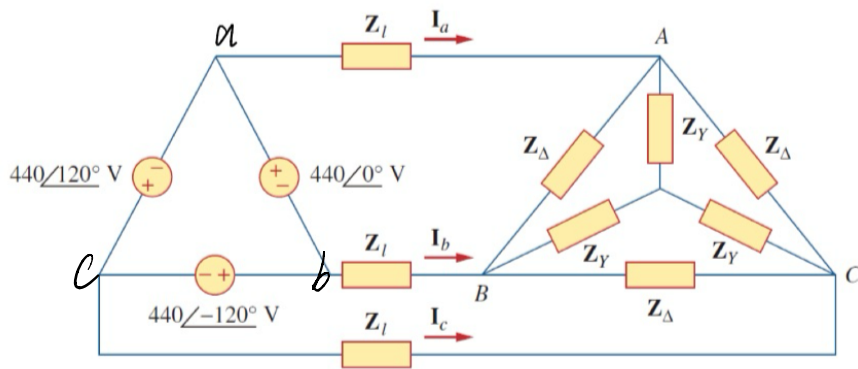Find the line currents in the three-phase network. Take $Z_{\Delta} = 12 - j15 \Omega$, $Z_Y = 4 + j6 \Omega$, $Z_L = 2 \Omega$.



Convert Δ -connected source to Y -connected.

$$\tilde{V}_{an} = \frac{\tilde{V}_{ab}}{\sqrt{3}} \angle -30^\circ = \frac{440}{\sqrt{3}} \angle -30^\circ = 254 \angle -30^\circ$$


Convert Δ -connected load to Y -connected load.

$$Z = Z_Y \parallel \frac{Z_{\Delta}}{3} = (4 + j6) \parallel (4 - j5) = 5.723 - j0.2153$$

$$\tilde{I}_a = \frac{\tilde{V}_{an}}{Z_L + Z} = \frac{254 \angle -30^\circ}{7.723 - j0.2153} = 32.88 \angle -28.4^\circ \text{ A}$$

$$\tilde{I}_b = \tilde{I}_a \angle -120^\circ = 32.88 \angle -148.4^\circ \text{ A}$$
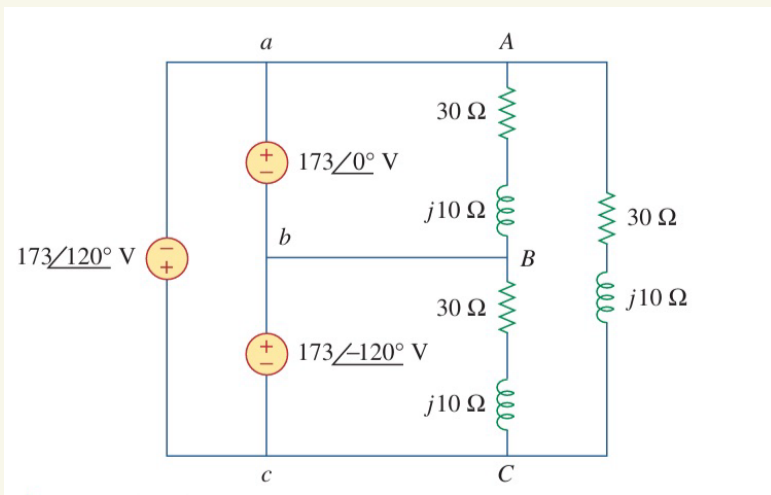
$$\tilde{I}_c = \tilde{I}_a \angle 120^\circ = 32.88 \angle 91.6^\circ \text{ A}$$



$$Z_{\Delta} = 30 + j10 \Omega$$

$$\text{Phase Current } \tilde{I}_{AB} = \frac{\tilde{V}_{ab}}{Z_{\Delta}} = \frac{173 \angle 0^\circ}{31.62 \angle 18.43^\circ} = 5.47 \angle -18.43^\circ \text{ A}$$

$$\tilde{I}_{BC} = \tilde{I}_{AB} \angle -120^\circ = 5.47 \angle -138.43^\circ \text{ A}$$

$$\tilde{I}_{CA} = \tilde{I}_{AB} \angle 120^\circ = 5.47 \angle 101.57^\circ \text{ A}$$

$$\text{Line Current } \tilde{I}_a = \tilde{I}_{AB} - \tilde{I}_{CA} = \tilde{I}_{AB} \sqrt{3} \angle -30^\circ = 9.474 \angle -48.43^\circ \text{ A}$$

$$\tilde{I}_b = \tilde{I}_a \angle -120^\circ = 9.474 \angle -168.43^\circ \text{ A}$$

$$\tilde{I}_c = \tilde{I}_a \angle 120^\circ = 9.474 \angle 71.57^\circ \text{ A}$$