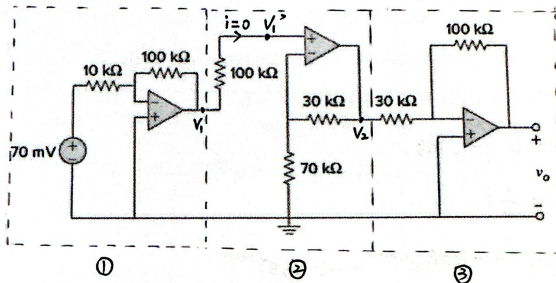


Due Date: 23:59, June.12th, 2025

In order to get full marks, you shall write all the intermediate steps of calculation or proof, unless otherwise indicated.

Exercise 3.1 (20%) Find v_o in the following op amp circuit.



$$\textcircled{1} \quad V_1 = -\frac{R_f}{R_i} V_i = -\frac{100 \times 10^3}{10 \times 10^3} \times 70 \times 10^{-3} = -0.7 \text{ V}$$

$$\textcircled{2} \quad i = 0$$

$$V_1' = V_1 = -0.7 \text{ V}$$

$$V_2 = \left(1 + \frac{30 \times 10^3}{70 \times 10^3}\right) \times -0.7 = -1 \text{ V}$$

$$\textcircled{3} \quad v_o = -\frac{R_f}{R_i} V_2 = -\frac{100}{30} \times -1 = \frac{10}{3} \text{ V} \approx 3.33 \text{ V}$$



Exercise 3.2 (30%) A 4-mF capacitor has the terminal voltage

$$v(t) = \begin{cases} 50 \text{ V}, & t \leq 0 \\ Ae^{-100t} + Be^{-600t} \text{ V}, & t > 0 \end{cases}$$

If the capacitor has an initial current of 2A, find:

- (a) (10%) the constants A and B ,
 (b) (10%) the energy stored in the capacitor at $t = 0$,
 (c) (10%) the capacitor current for $t > 0$.

(a) $v(t) = \frac{1}{C} \int_0^t i dt$

$$\frac{dv}{dt} = \frac{1}{C} i$$

$$\frac{2}{4 \times 10^{-3}} = -100Ae^{-100 \cdot 0} + -600Be^{-600 \cdot 0}$$

$$-100A - 600B = 500 \quad \textcircled{1}$$

$$A + B = 50 \quad \textcircled{2}$$

$$\textcircled{1} \textcircled{2} \Rightarrow \begin{cases} A = 61 \\ B = -11 \end{cases}$$

(b) $w = \frac{1}{2} C v^2 = \frac{1}{2} \times 4 \times 10^{-3} \times 50^2 = 5 \text{ J}$

(c) $i = C \frac{dv}{dt}$

$$= C (-100Ae^{-100t} - 600Be^{-600t})$$

$$= 4 \times 10^{-3} (-6100e^{-100t} + 6600e^{-600t})$$

$$= -24.4e^{-100t} + 26.4e^{-600t} \text{ A}$$




VE215 2025SU Assignment 1




JOINT INSTITUTE
交大密西根学院

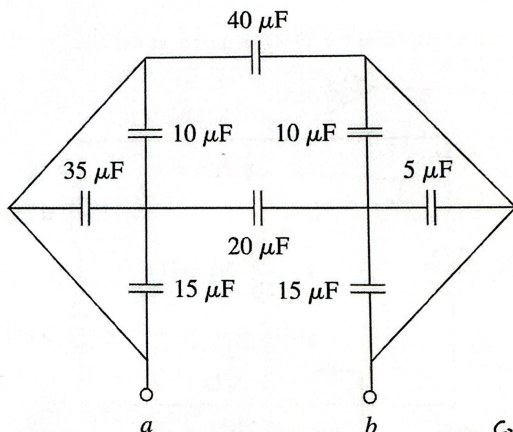Exercise 3.3(10%) Determine C_{eg} for the circuit.


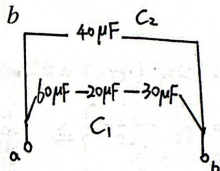
$$\begin{aligned} 10\mu\text{F} \parallel 35\mu\text{F} \parallel 15\mu\text{F} &= 60\mu\text{F} \\ 10\mu\text{F} \parallel 5\mu\text{F} \parallel 15\mu\text{F} &= 30\mu\text{F} \end{aligned} \rightarrow$$



$$\frac{1}{C_1} = \frac{1}{60\mu\text{F}} + \frac{1}{20\mu\text{F}} + \frac{1}{30\mu\text{F}} \Rightarrow C_1 = 10\mu\text{F}$$

$$C_{eg} = C_1 + C_2 = 50\mu\text{F}$$




CS 扫描全能王

3亿人都在用的扫描App

Exercise 3.4 (20%) Find:

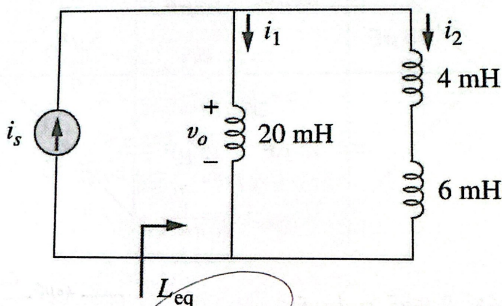- (a) (10%) L_{eq} , $i_1(t)$, and $i_2(t)$ if $i_s = 3e^{-t}$ mA,
 (b) (5%) $v_o(t)$,
 (c) (5%) energy stored in the 20-mH inductor at $t = 1$ s.



(a) $L_{eq} = 20 \parallel (4 + 6) = \frac{20}{3} \text{ mH} = 6.67 \text{ mH}$

$$\left. \begin{aligned} \frac{di_s}{dt} &= \frac{di_1}{dt} + \frac{di_2}{dt} \\ 20 \frac{di_1}{dt} &= 10 \frac{di_2}{dt} \end{aligned} \right\} \Rightarrow \begin{aligned} \frac{di_1}{dt} &= \frac{10}{30} \frac{di_s}{dt} \\ \frac{di_2}{dt} &= \frac{20}{30} \frac{di_s}{dt} \end{aligned}$$

(b) $V_o = 20 \times 10^{-3} \frac{di_1}{dt} = 20 \times 10^{-3} \cdot -e^{-t} \times 10^{-3}$
 $= -2 \times 10^{-5} e^{-t} \text{ V}$

$$\begin{aligned} i_1 &= \frac{1}{3} i_s = e^{-t} \text{ mA} \\ i_2 &= \frac{2}{3} i_s = 2e^{-t} \text{ mA} \end{aligned}$$

(c) $w = \frac{1}{2} L i^2 = \frac{1}{2} \times 20 \times 10^{-3} \times (e^{-1} \times 10^{-3})^2 = 1.35 \times 10^{-9} \text{ J}$




VE215 2025SU Assignment 1



JOINT INSTITUTE
交大密西根学院

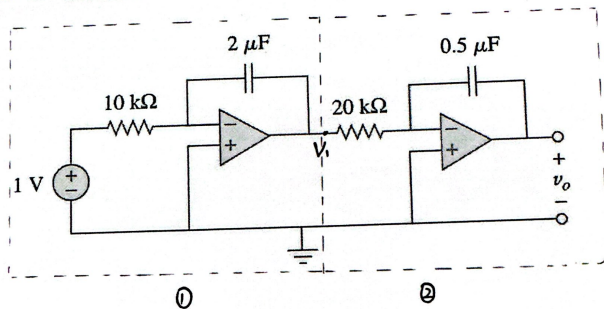Exercise 3.5 (20%) At $t = 1.5\text{ms}$, calculate v_o , due to the cascaded integrators, Assume that the integrators are reset to 0V at $t = 0$.



$$\begin{aligned} \textcircled{1} \quad V_1 &= -\frac{1}{RC} \int_0^t 1 \, dt + V_1(0) \\ &= -\frac{1}{1 \times 10^4 \times 2 \times 10^{-6}} t + 0 \\ &= -50t \, (\text{V}) \end{aligned}$$

$$\begin{aligned} \textcircled{2} \quad V_o &= -\frac{1}{RC} \int_0^t -50t \, dt + V_o(0) \\ &= -\frac{1}{2 \times 10^4 \times 0.5 \times 10^{-6}} (-25t^2) + 0 \\ &= 2500t^2 \, (\text{V}) \end{aligned}$$

$$\begin{aligned} V_o(1.5\text{ms}) &= 2500 \times (1.5 \times 10^{-3})^2 \\ &= 5.625 \times 10^{-3} \, \text{V} \end{aligned}$$



CS 扫描全能王

3亿人都在用的扫描App