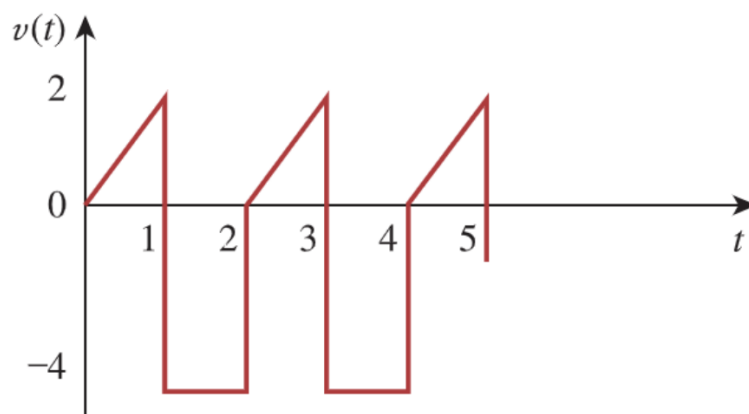


VE215 2025SU Assignment 6


Due Date: 23:59, July.22th, 2025

In order to get full marks, you shall write all the intermediate steps of calculation or proof, unless otherwise indicated.

Exercise 6.1 (10%) Find the rms value of the signal.



Exercise 6.2 (20%) Assuming that the load impedance is to be purely resistive, what load should be connected to terminals a – b of the circuit so that the maximum power is transferred to the load?

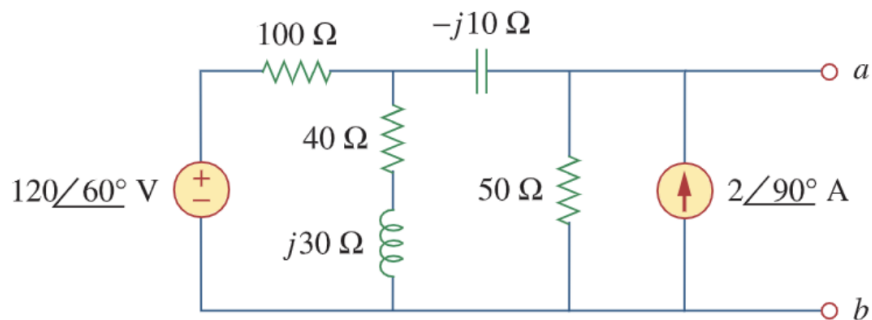

Exercise 6.3 (30%)


A 240-V rms 60-Hz source supplies a parallel combination of a 5-kW heater and a 30-kVA induction motor whose power factor is 0.82. Determine:

1. the system apparent power
2. the system reactive power
3. Sketch the power triangle for the current system and label $|S|$, P , and Q
4. the power factor of the current system
5. the kVA rating of a capacitor required to adjust the system power factor to 0.9 lagging
6. the value of the capacitor required

Exercise 6.4 (20%)

Two wattmeters are properly connected to the unbalanced load supplied by a balanced source such that $V_{ab} = 208\angle 0^\circ$ V with positive phase sequence.

1. Determine the reading of each wattmeter.
2. Calculate the total apparent power absorbed by the load.

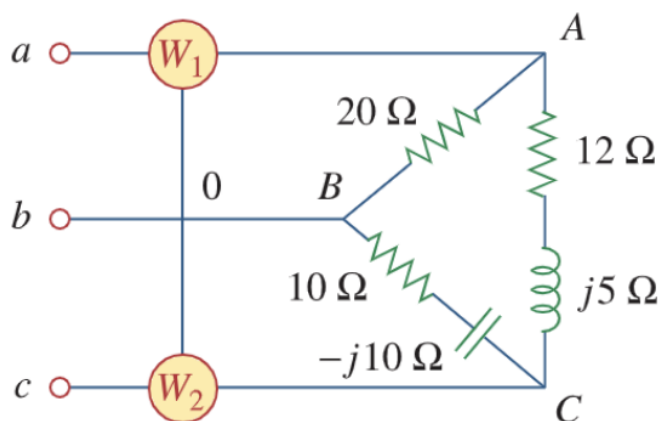

Exercise 3.5 (20%) For the three-phase circuit below, find the average power absorbed by the delta-connected load with

$$Z_{\Delta} = 21 + j24 \Omega.$$

