

# ECE215 HW4

November 14, 2025

**Due Date: 28th November**

Hint: In this homework, final answers should be expressed as  $Ans = A\angle\phi$ .

## Problem 1

Set  $i_s = 2 \cos 10^3 t \text{ A}$  in Fig. 1. Try to find:

- (1) Use Y- $\Delta$  transformation to find the equivalent  $Z$  of this circuit.
- (2) Find  $v_0$ .

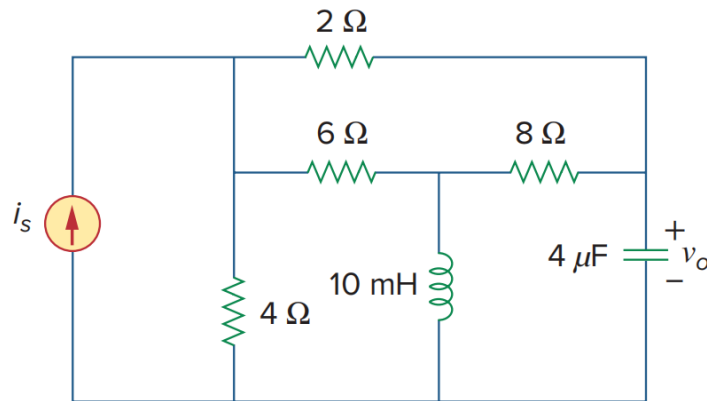


Figure 1: Circuit of Problem 1.

## Problem 2

Let  $V_{in} = V_m \cos \omega t$ , try to find  $Z_{in}$  in Fig. 2.  $Z_{in} = \frac{V_{in}}{I_{in}}$ .

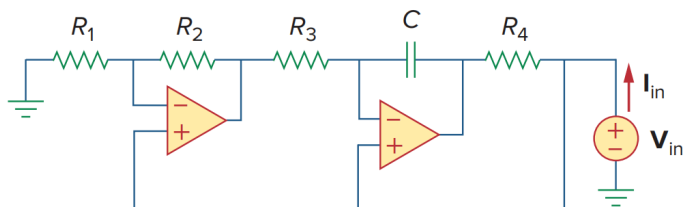


Figure 2: Circuit of Problem 2.

### Problem 3

Find  $I_o$  in the circuit of Fig. 3.

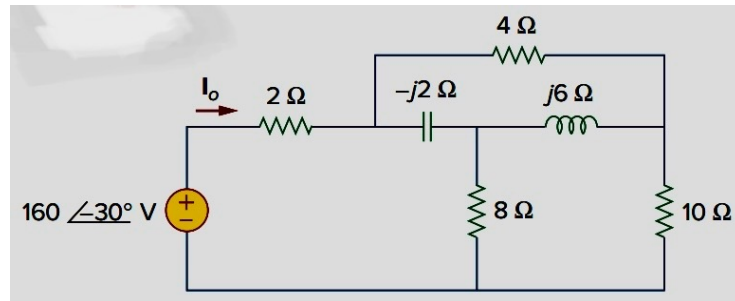


Figure 3: Circuit of Problem 3.

## Problem 4

The AC bridge circuit of Fig. 4 is called a Wien bridge. It is used for measuring the frequency of a source. Try to find the frequency of the source when the bridge is balanced.

Hint: The bridge is balanced means the value shown on AC meter is zero.  $R_1$  and  $R_3$  could be any purely resistive resistances.

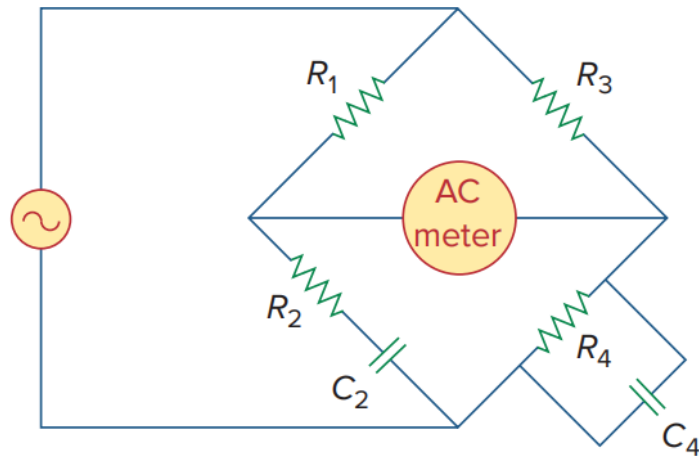


Figure 4: Circuit of Problem 4.