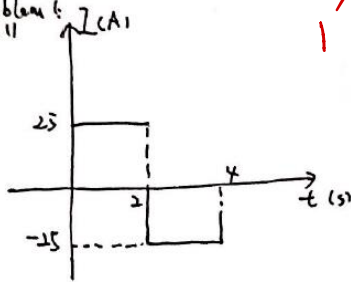


1.


Problem 4



$$\omega W = \int_0^4 p dt = 500\text{ J}$$

$$\text{Since } p = UI = 125\text{ W}$$

2.

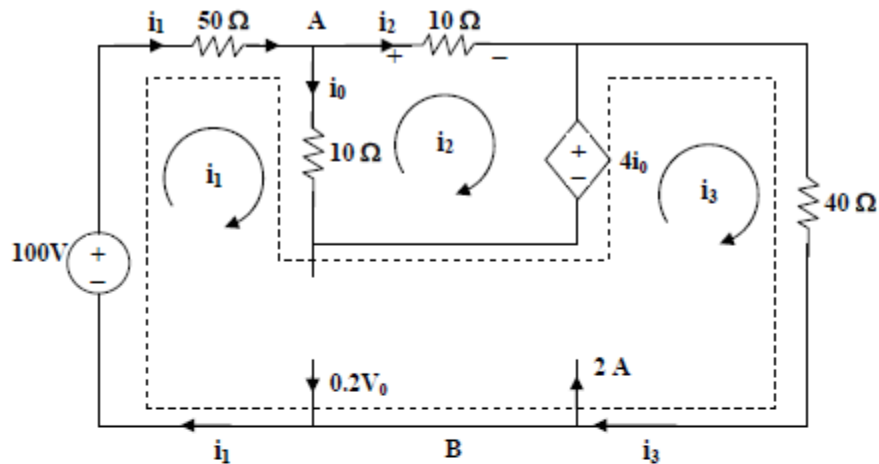

For mesh 2, $20i_2 - 10i_1 + 4i_0 = 0$

But at node A, $i_0 = i_1 - i_2$ so that (1) becomes $i_1 = (16/6)i_2$

For the supermesh, $-100 + 50i_1 + 10(i_1 - i_2) - 4i_0 + 40i_3 = 0$

or $50 = 28i_1 - 3i_2 + 20i_3$

At node B, $i_3 + 0.2V_0 = 2 + i_1$

But, $V_0 = 10i_2$ so that (4) becomes $i_3 = 2 + (2/3)i_2$



Solving (1) to (5), $i_2 = 0.11764$,

$V_0 = 10i_2 = \underline{1.1764\text{ volts}}$, $i_0 = i_1 - i_2 = (5/3)i_2 = \underline{196.07\text{ mA}}$


3.

Problem 3.

By γ -delta transformation.

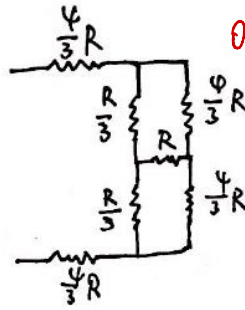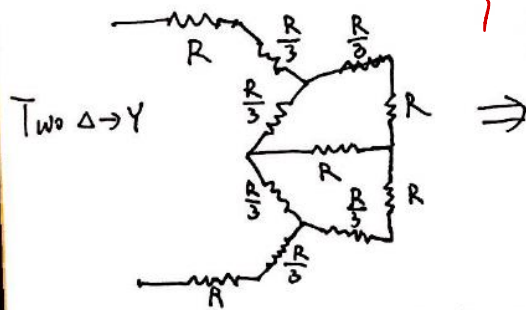

$\Delta \rightarrow \gamma$

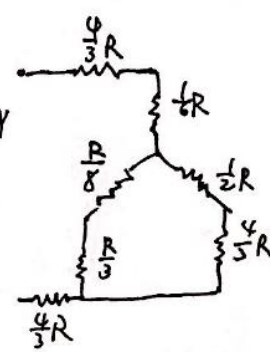

$$S_1 \quad R_{eq} = \frac{4}{3}R + \frac{1}{6}R + \frac{\left(\frac{R}{8} + \frac{R}{3}\right) \cdot \left(\frac{R}{2} + \frac{4}{3}R\right)}{\frac{R}{8} + \frac{R}{3} + \frac{R}{2} + \frac{4}{3}R} = \frac{4}{3}R + \frac{16}{5}R.$$