

## Exercise 1.1

$$(a) \quad i = \frac{dq}{dt} = 20\pi \cos(4\pi t) \text{ mA}$$

$$p = vi = 100\pi \cos^2(4\pi t) \text{ mW}$$


$$\text{At } t = 0.3 \text{ s}, \quad p = 205.62 \text{ mW}$$

$$(b) \quad W = \int p dt = 100\pi \int_0^{0.6} \cos^2(4\pi t) dt = 97.92 \text{ mJ}$$

## Exercise 1.2
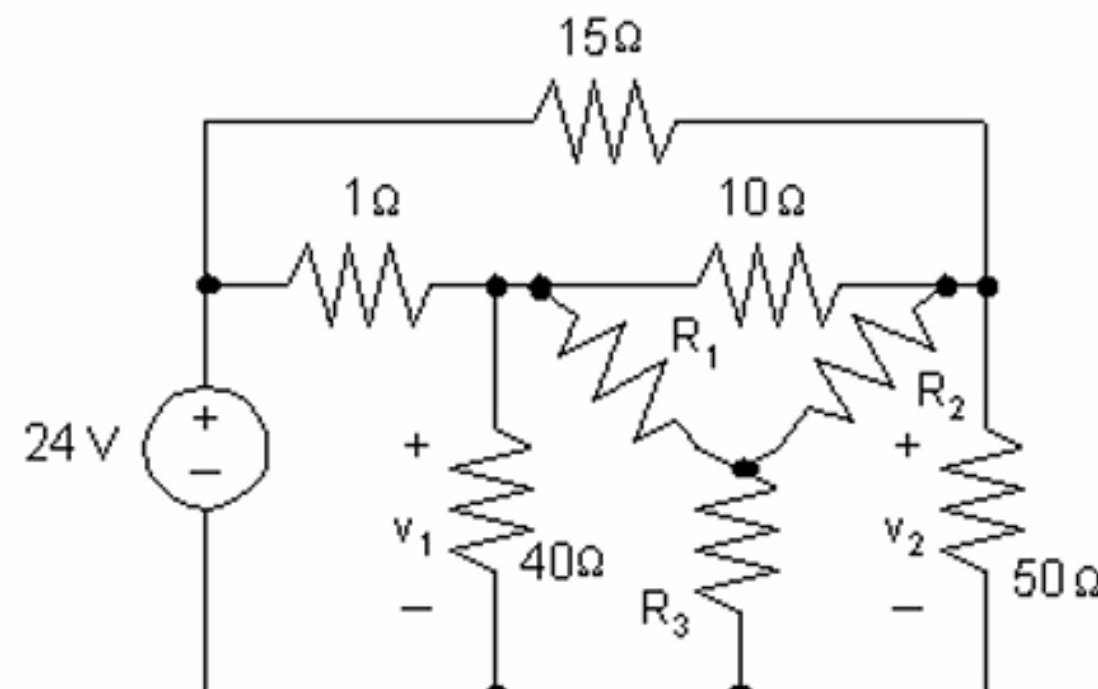
### Method 1


P 3.59 Begin by transforming the  $\Delta$ -connected resistors ( $10\Omega$ ,  $40\Omega$ ,  $50\Omega$ ) to Y-connected resistors. Both the Y-connected and  $\Delta$ -connected resistors are shown below to assist in using Eqs. 3.44 – 3.46:



Now use Eqs. 3.44 – 3.46 to calculate the values of the Y-connected resistors:

$$R_1 = \frac{(40)(10)}{10 + 40 + 50} = 4\Omega; \quad R_2 = \frac{(10)(50)}{10 + 40 + 50} = 5\Omega; \quad R_3 = \frac{(40)(50)}{10 + 40 + 50} = 20\Omega$$

The transformed circuit is shown below:

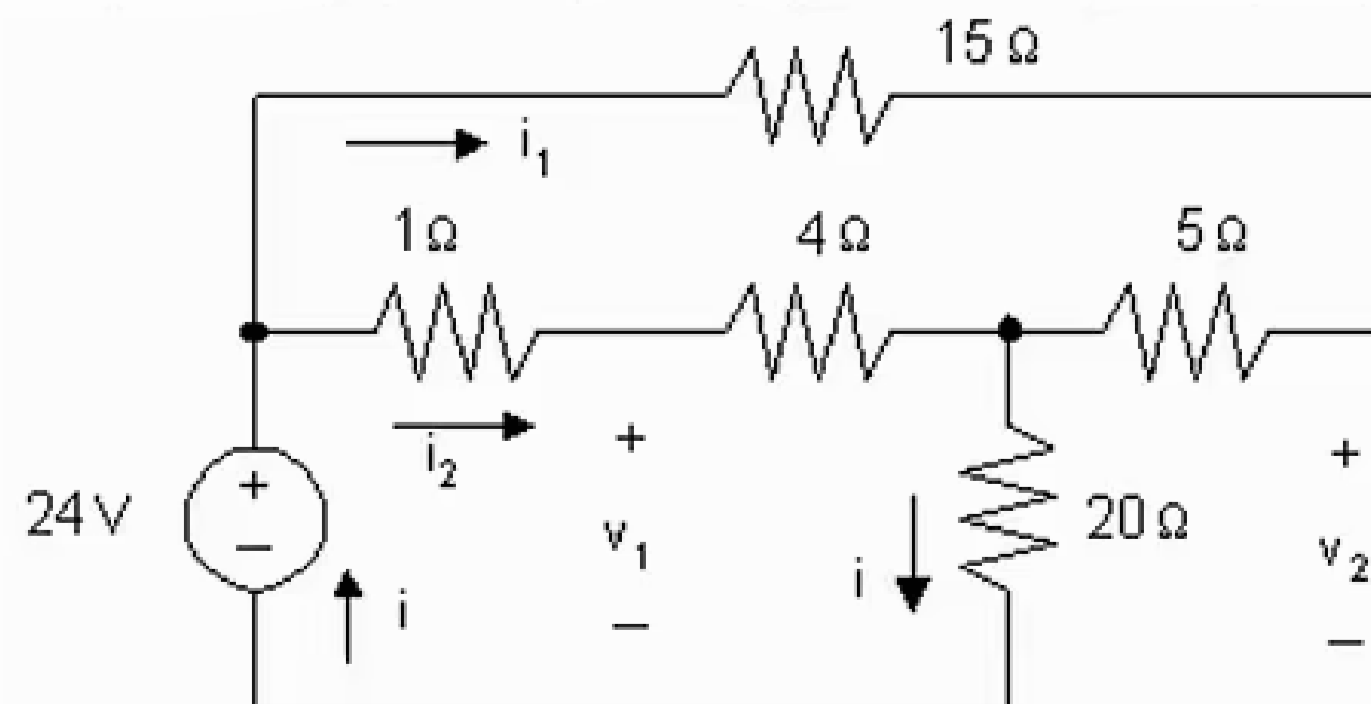

The equivalent resistance seen by the 24 V source can be calculated by making series and parallel combinations of the resistors to the right of the 24 V source:

$$R_{eq} = (15 + 5) \parallel (1 + 4) + 20 = 20 \parallel 5 + 20 = 4 + 20 = 24\Omega$$

Therefore, the current  $i$  in the 24 V source is given by

$$i = \frac{24 \text{ V}}{24\Omega} = 1 \text{ A}$$

Use current division to calculate the currents  $i_1$  and  $i_2$ . Note that the current  $i_1$  flows in the branch containing the  $15\Omega$  and  $5\Omega$  series connected resistors, while the current  $i_2$  flows in the parallel branch that contains the series connection of the  $1\Omega$  and  $4\Omega$  resistors:

$$i_1 = \frac{4}{15 + 5}(i) = \frac{4}{20}(1 \text{ A}) = 0.2 \text{ A}, \quad \text{and} \quad i_2 = 1 \text{ A} - 0.2 \text{ A} = 0.8 \text{ A}$$


Now use KVL and Ohm's law to calculate  $v_1$ . Note that  $v_1$  is the sum of the voltage drop across the  $4\Omega$  resistor,  $4i_2$ , and the voltage drop across the  $20\Omega$  resistor,  $20i$ :

$$v_1 = 4i_2 + 20i = 4(0.8 \text{ A}) + 20(1 \text{ A}) = 3.2 + 20 = 23.2 \text{ V}$$

Finally, use KVL and Ohm's law to calculate  $v_2$ . Note that  $v_2$  is the sum of the voltage drop across the  $5\Omega$  resistor,  $5i_1$ , and the voltage drop across the  $20\Omega$  resistor,  $20i$ :

$$v_2 = 5i_1 + 20i = 5(0.2 \text{ A}) + 20(1 \text{ A}) = 1 + 20 = 21 \text{ V}$$

Method 2

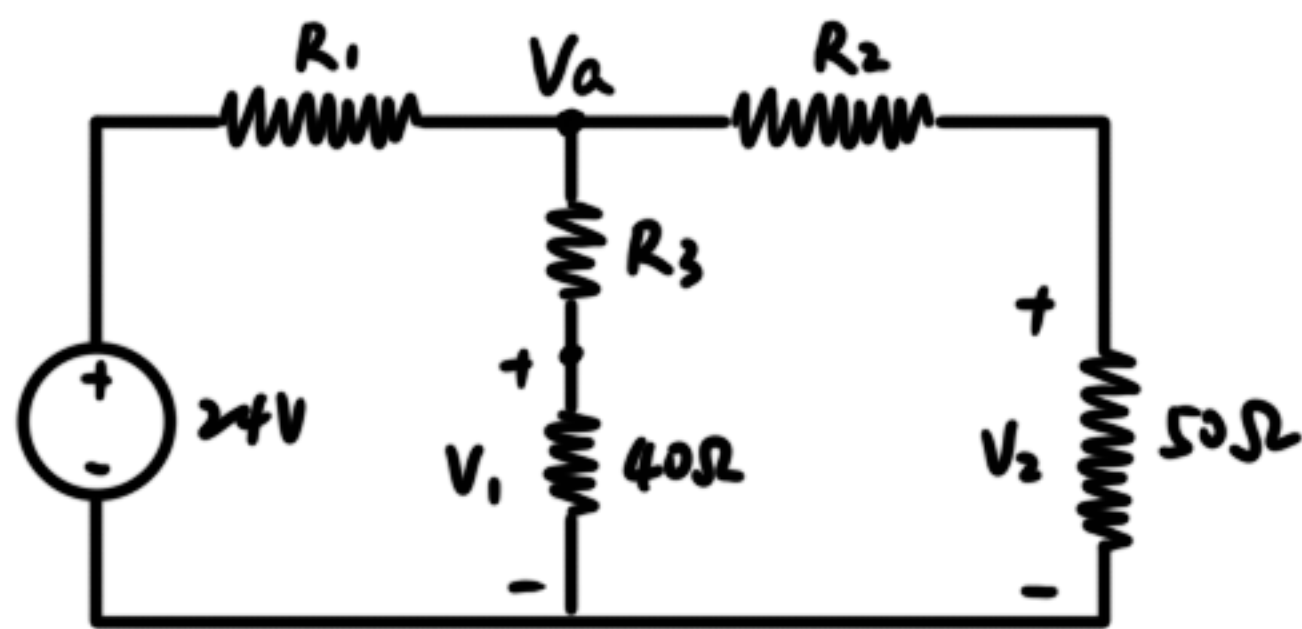

$$R_1 = \frac{15}{26} \Omega \quad R_2 = \frac{150}{26} \Omega \quad R_3 = \frac{10}{26} \Omega$$

$$R_{11} = \frac{1}{\frac{1}{R_2 + 50\Omega} + \frac{1}{R_3 + 40\Omega}} = \frac{609}{26} \Omega$$

$$V_a = 24V \times \frac{R_{11}}{R_1 + R_{11}} = \frac{609}{26} V$$

$$V_1 = V_a \times \frac{40\Omega}{R_3 + 40\Omega} = 23.2 V$$

$$V_2 = V_a \times \frac{50\Omega}{R_2 + 50\Omega} = 21 V$$

Exercise 1.3 (a) 9 branches . 5 nodes . 5 meshes

$$(b) \quad 40i_2 + \frac{5}{40} + \frac{5}{10} = 0; \quad i_2 = -15.625 \text{ mA}$$

$$v_1 = 80i_2 = -1.25 \text{ V}$$


$$25i_1 + \frac{(-1.25)}{20} + (-0.015625) = 0; \quad i_1 = 3.125 \text{ mA}$$

$$v_g = 60i_1 + 260i_2 = 320i_1$$

Therefore,  $v_g = 1 \text{ V}$ .

Exercise 1.4 (a)

Chapter 3, Solution 17

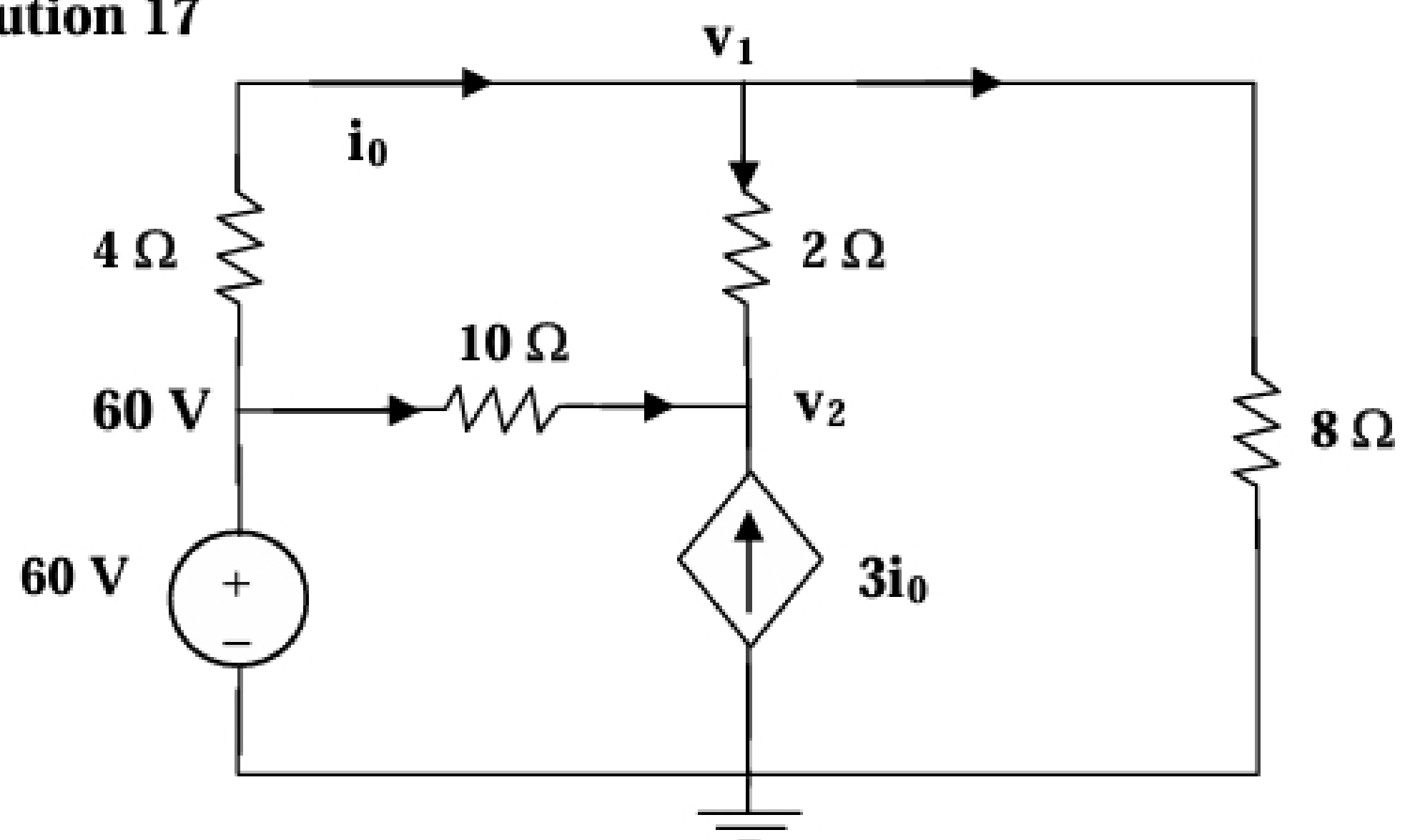

$$\text{At node 1, } \frac{60 - v_1}{4} = \frac{v_1}{8} + \frac{v_1 - v_2}{2} \quad 120 = 7v_1 - 4v_2 \quad (1)$$

$$\text{At node 2, } 3i_0 + \frac{60 - v_2}{10} + \frac{v_1 - v_2}{2} = 0$$


$$\text{But } i_0 = \frac{60 - v_1}{4}.$$

Hence

$$\frac{3(60 - v_1)}{4} + \frac{60 - v_2}{10} + \frac{v_1 - v_2}{2} = 0 \longrightarrow 1020 = 5v_1 + 12v_2 \quad (2)$$

$$\text{Solving (1) and (2) gives } v_1 = 53.08 \text{ V. Hence } i_0 = \frac{60 - v_1}{4} = 1.73 \text{ A}$$

(b) Consider the circuit shown below.

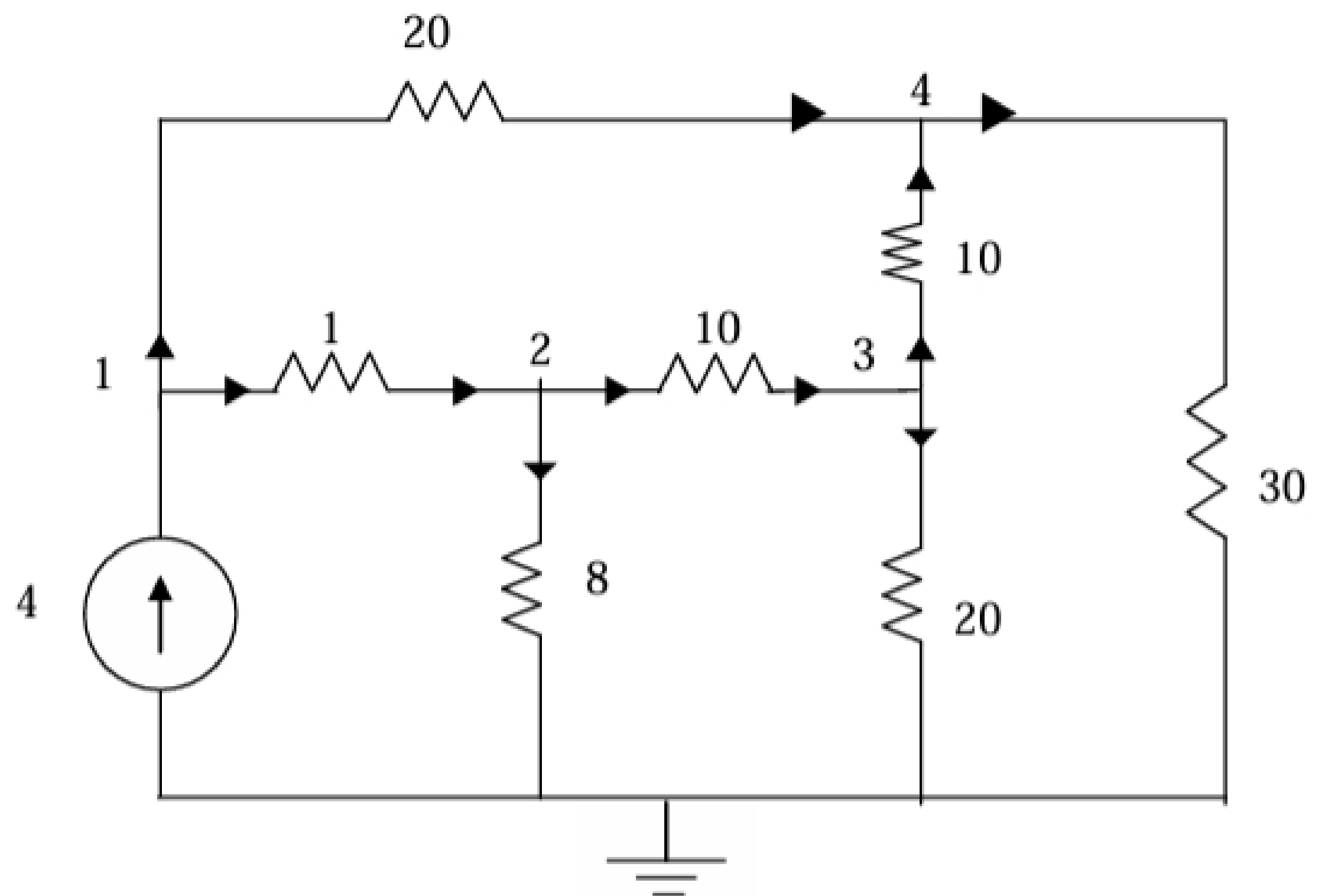

At node 1.

$$4 = \frac{V_1 - V_2}{1} + \frac{V_1 - V_4}{20} \longrightarrow 80 = 21V_1 - 20V_2 - V_4 \quad (1)$$

At node 2,

$$\frac{V_1 - V_2}{1} = \frac{V_2}{8} + \frac{V_2 - V_3}{10} \longrightarrow 0 = -80V_1 + 98V_2 - 8V_3 \quad (2)$$

At node 3,

$$\frac{V_2 - V_3}{10} = \frac{V_3}{20} + \frac{V_3 - V_4}{10} \longrightarrow 0 = -2V_2 + 5V_3 - 2V_4 \quad (3)$$

At node 4,

$$\frac{V_1 - V_4}{20} + \frac{V_3 - V_4}{10} = \frac{V_4}{30} \longrightarrow 0 = 3V_1 + 6V_3 - 11V_4 \quad (4)$$

Putting (1) to (4) in matrix form gives:


$$\begin{bmatrix} 80 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 21 & -20 & 0 & -1 \\ -80 & 98 & -8 & 0 \\ 0 & -2 & 5 & -2 \\ 3 & 0 & 6 & -11 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix}$$

$$B = A V \longrightarrow V = A^{-1} B$$

Using MATLAB leads to

$$V_1 = 25.52 \text{ V}, \quad V_2 = 22.05 \text{ V}, \quad V_3 = 14.842 \text{ V}, \quad V_4 = 15.055 \text{ V}$$

Exercise 1.5 (a)

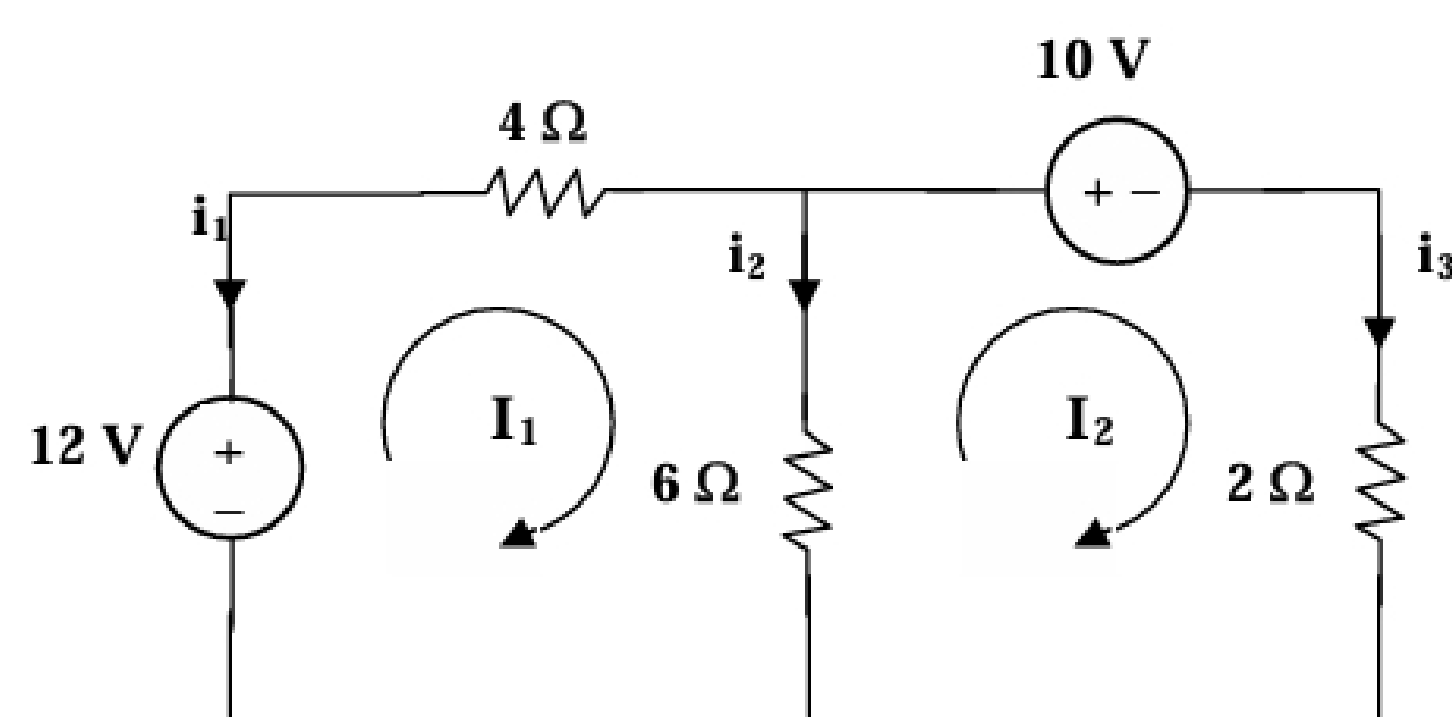

Applying mesh analysis gives,


$$10I_1 - 6I_2 = 12 \text{ and } -6I_1 + 8I_2 = -10$$

$$\text{or} \quad \begin{bmatrix} 6 \\ -5 \end{bmatrix} = \begin{bmatrix} 5 & -3 \\ -3 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 6 \\ -5 \end{bmatrix} \text{ or } \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \frac{\begin{bmatrix} 4 & 3 \\ 3 & 5 \end{bmatrix}}{11} \begin{bmatrix} 6 \\ -5 \end{bmatrix}$$

$$I_1 = (24-15)/11 = 0.8182 \text{ and } I_2 = (18-25)/11 = -0.6364$$

$$i_1 = -I_1 = -818.2 \text{ mA}; \quad i_2 = I_1 - I_2 = 0.8182 + 0.6364 = 1.4546 \text{ A}; \text{ and } i_3 = I_2 = -636.4 \text{ mA}.$$

(b)

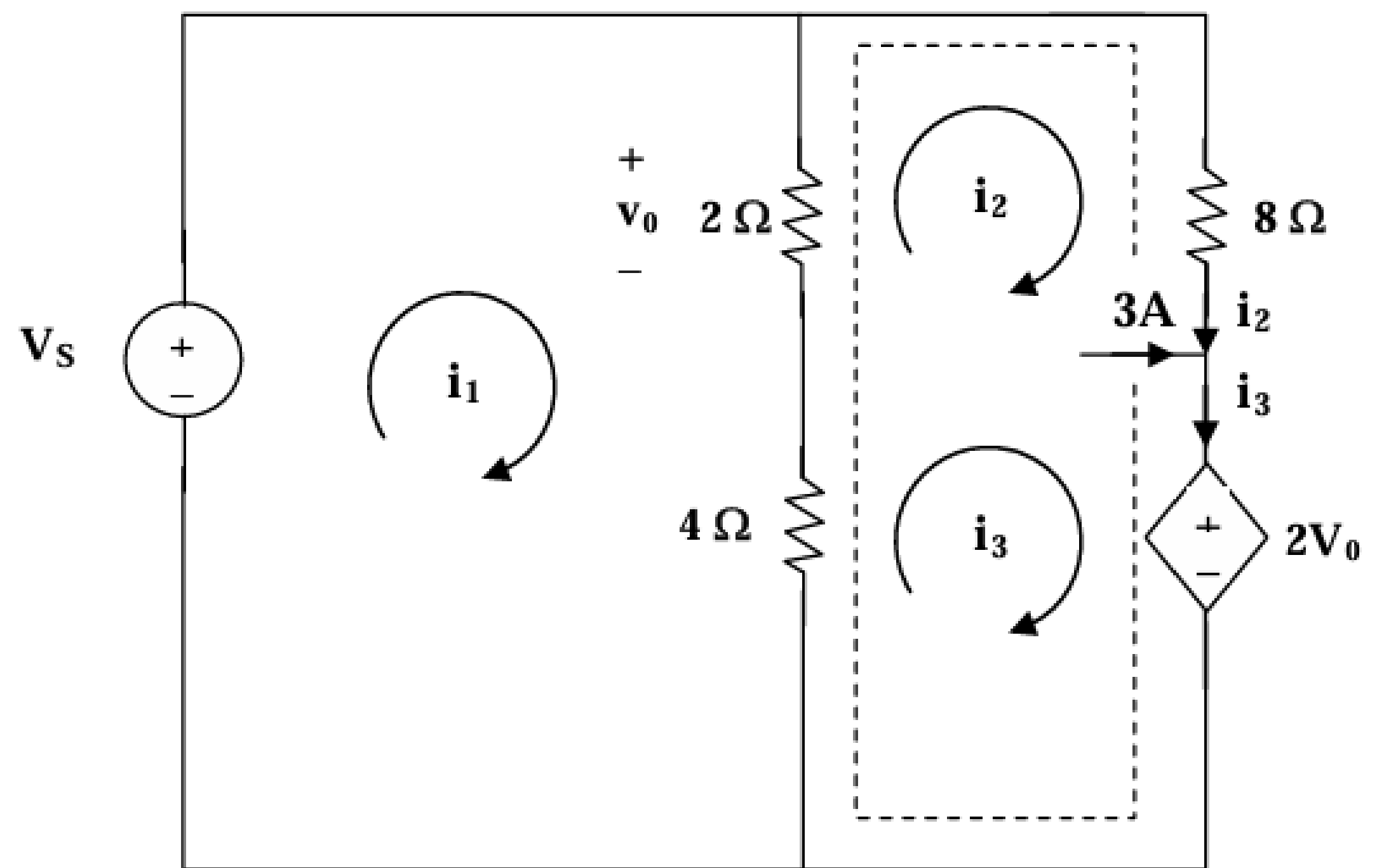

For mesh 1,

$$2(i_1 - i_2) + 4(i_1 - i_3) - 12 = 0 \text{ which leads to } 3i_1 - i_2 - 2i_3 = 6 \quad (1)$$

For the supermesh,  $2(i_2 - i_1) + 8i_2 + 2v_0 + 4(i_3 - i_1) = 0$

But  $v_0 = 2(i_1 - i_2)$  which leads to  $-i_1 + 3i_2 + 2i_3 = 0$   
(2)

For the independent current source,  $i_3 = 3 + i_2$  (3)

Solving (1), (2), and (3), we obtain,

$$i_1 = \mathbf{3.5 \text{ A}}, \quad i_2 = \mathbf{-0.5 \text{ A}}, \quad i_3 = \mathbf{2.5 \text{ A}}.$$