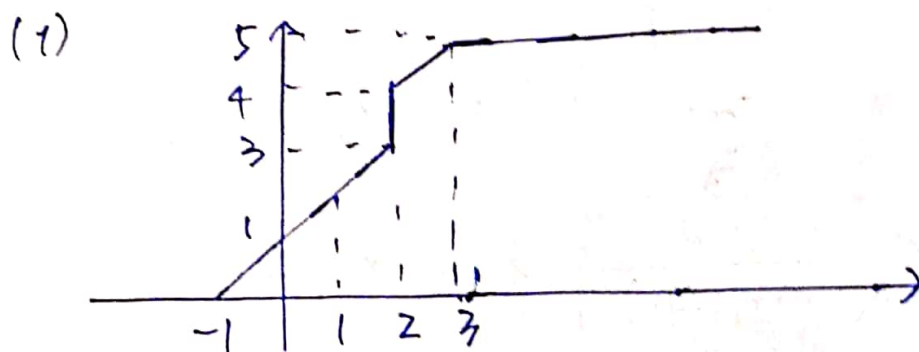


Quiz 3 Solution

Problem # 1.



$$(2) \int_{-\infty}^{+\infty} f'(t) \delta(t-5) dt = f'(5)$$

$$f'(t) = u(t+1) + \delta(t-2) - u(t-3)$$

$$f'(5) = 0 \quad (\text{or from the curve, } f'(5) = 0)$$

$$\text{Thus, } \int_{-\infty}^{+\infty} f'(t) \delta(t-5) dt = 0$$

Problem # 2.

(1) Charging process: the switch is turned on ($\text{---} \circ \text{---} \downarrow \text{---} \circ \text{---}$), it performs as an R - L circuit and the inductor stores charges.

(2) Ignition process: the switch is turned off ($\text{---} \nearrow \text{---}$) in a short time, which means the voltage variance is large during the short time period. Then, it can make the air breakdown and the ignition happens.




$$(2) \quad |U_s| = L \frac{di}{dt} = L \frac{\Delta I}{\Delta t} \quad (\text{suppose } \Delta t \text{ is small})$$

since

$$\Delta t = \frac{L \Delta I}{|U_s|} = \frac{L \frac{U}{R}}{U_s} = \frac{LU}{RU_s}$$

Problem #3.

Step #1:

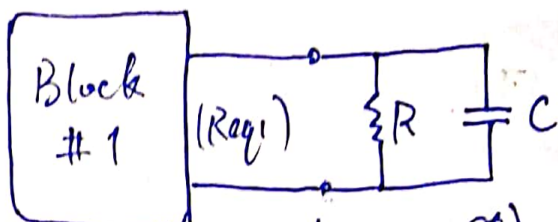


$$R_{eq} = \frac{R \cdot Req_1}{R + Req_1}$$

$$C_{eq} = C$$

Measure the (charging) time (the time interval between starting and the readout of current meter is ~~zero~~) as t_1 , not change ($t_1 \approx 5\tau_1$)

Step #2

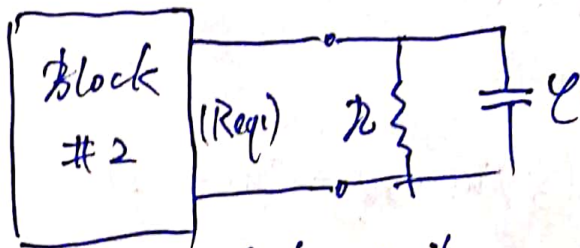

$$R_{eq} = \frac{R \cdot Req_2}{R + Req_2}$$

$$C_{eq} = C$$

Measure the (charging) time as t_2 ($t_2 \approx 5\tau_2$)

$$T_1 \approx 5\tau_1 = 5 \cdot \frac{R \cdot Req_1}{R + Req_1} \cdot C \quad T_2 = 5\tau_2 = 5 \cdot \frac{R \cdot Req_2}{R + Req_2} \cdot C$$

$$\frac{\frac{R \cdot Req_1}{R + Req_1}}{\frac{R \cdot Req_2}{R + Req_2}} = \frac{T_1}{T_2} \Rightarrow R = \frac{Req_1 Req_2 (T_1 - T_2)}{Req_1 T_2 - Req_2 T_1} \quad C = \frac{T_1 T_2 (Req_1 - Req_2)}{5 Req_1 Req_2 (T_1 - T_2)}$$

