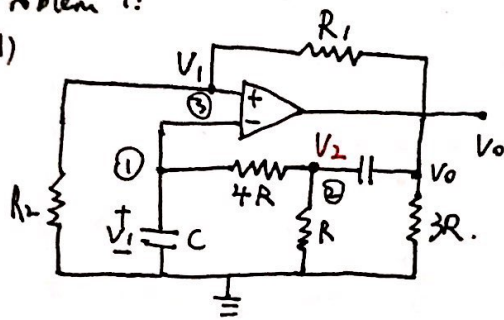


Problem 1:

(1)

Assume V_2 .

From the property of op-amp, we know $V_1 = V_- = V_+$.

Then we can apply KCL, considering node ① and node ②

$$Z_C = \frac{1}{j\omega C}$$

$$\left\{ \begin{aligned} \frac{V_1}{\frac{1}{j\omega C}} &= \frac{V_2 - V_1}{4R} \Rightarrow V_1 = \frac{V_2 - V_1}{4Rj\omega C} \Rightarrow (4Rj\omega C + 1)V_1 = V_2 \quad \text{Formula A} \end{aligned} \right.$$

$$\frac{V_2 - V_1}{4R} = \frac{V_0 - V_2}{\frac{1}{j\omega C}} + \frac{-V_2}{R} \quad \text{Formula B.}$$

We plug Formula A into Formula B.

$$\frac{4Rj\omega C V_1}{4R} = \frac{V_0 - (4Rj\omega C + 1)V_1}{\frac{1}{j\omega C}} - \frac{(4Rj\omega C + 1)V_1}{R}$$

$$\Rightarrow j\omega C V_1 = j\omega C V_0 + 4R^2\omega^2 C^2 V_1 - j\omega C V_1 - 4j\omega C V_1 - \frac{1}{R} V_1$$

$$\Rightarrow 6j\omega C V_1 - 4R^2\omega^2 C^2 V_1 + \frac{1}{R} V_1 = j\omega C V_0$$

$$\text{Then } \frac{V_0}{V_1} = \frac{6j\omega C - 4R^2\omega^2 C^2 + \frac{1}{R}}{j\omega C} = 6 + 4Rj\omega C + \frac{1}{Rj\omega C} = 6 + 4Rj\omega C - \frac{1}{R\omega C}j$$

$$\text{To make this real, } 4R\omega C - \frac{1}{R\omega C} = 0 \Rightarrow 4R^2\omega^2 C^2 = 1 \Rightarrow \boxed{\omega = \frac{1}{2RC}}$$

Here $\frac{V_0}{V_1} = 6$, which is real


And then we also apply KCL to node ③.

$$\frac{V_1 - 0}{R_2} + \frac{V_1 - V_0}{R_1} = 0$$

$$\Rightarrow V_1 R_1 + (V_1 - V_0) R_2 = 0 \Rightarrow V_1 (R_1 + R_2) = V_0 R_2 \Rightarrow \frac{V_0}{V_1} = \frac{R_1 + R_2}{R_2} = 6$$

$$\Rightarrow \frac{V_0}{V_1} = 1 + \frac{R_1}{R_2} = 6 \Rightarrow \boxed{\frac{R_1}{R_2} = 5}$$

Problem 2:

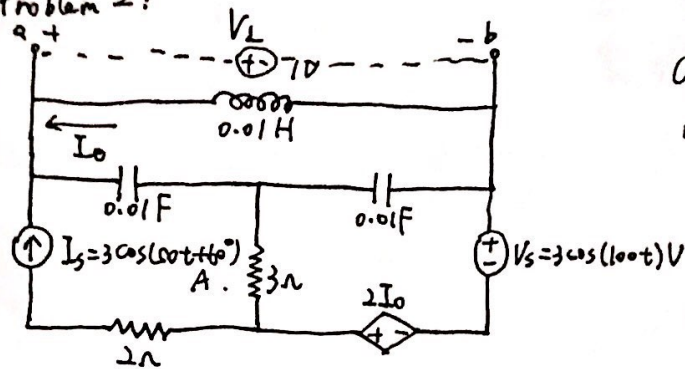


Clearly, there are two independent sources of two different frequencies.

1. First, we find thevenin resistance when all independent sources are turned off.

Since there is a dependent source,

so we assume a,b are connected to ^{ac} source of $\omega = 50$.
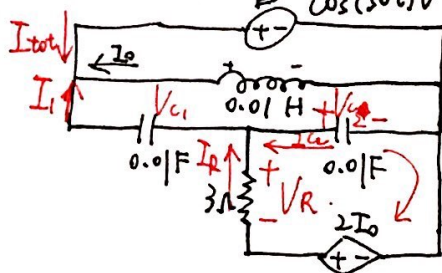
$$\cos(50t) V = 1 \angle 0^\circ \quad \omega = 50$$



$$I_0 = -\frac{1 \angle 0^\circ}{Z_C} = -\frac{1 \angle 0^\circ}{j \cdot 50 \cdot 0.01} = 2 \angle -90^\circ A$$

$$\text{So voltage of dependent source} = 2I_0 = 4j V$$

So by KVL

$$V_R + V_C = 0 \Rightarrow V_R = -V_C = 12j V$$

$$\text{Then current through } C_2 \text{ is } I_{C2} = \frac{V_C}{Z_{C2}} = \frac{12j}{j \cdot 50 \cdot 0.01} = -6 A$$

$$\text{By KCL, } I_1 = I_R + I_{C2} = (4j - 6) A$$

$$\text{Then } I_{tot} + I_0 + I_1 = 0 \quad (\text{KCL})$$

$$I_{tot} = -I_0 - I_1 = (6 - 6j) A$$


$$\text{Then } Z_{TH} (\text{under } \omega = 50) = \frac{1 \angle 0^\circ}{6 - 6j} = \frac{1}{6} + \frac{1}{6}j \Omega$$

And V_{TH} is calculated by turning off V_S and curating on I_S



Then the graph can be simplified to.

assume b side is connected to gnd

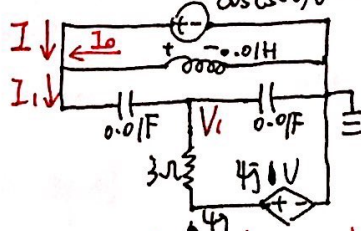

Assume node voltage V_1 .

$$\text{then } \frac{1 - V_1}{-2j} = \frac{V_1}{-2j} + \frac{V_1 - 4j}{3} \Rightarrow (6 - 2j)V_1 = 3 - 8j$$


$$3 - 3V_1 = 3V_1 - 8j - 2jV_1 \Rightarrow V_1 = \frac{3 - 8j}{6 - 2j}$$

$$I_1 = \frac{1 - V_1}{-2j} = \left(\frac{11}{40} - \frac{13}{40}j \right) A$$

Then $I + I_0 = I_1$ $\frac{11}{40} - \frac{13}{40}j$ A
 $\Rightarrow I = I_1 - I_0 = \frac{11}{40} - \frac{13}{40}j - \frac{11}{40} + \frac{93}{40}j = \frac{80}{40}j = 2j$ A.

Then $Z_{TH} = \frac{1 \angle 0^\circ}{\frac{11}{40} - \frac{93}{40}j} = \frac{40}{(11 - 93j)} \Omega$. (under $\omega = 50$)

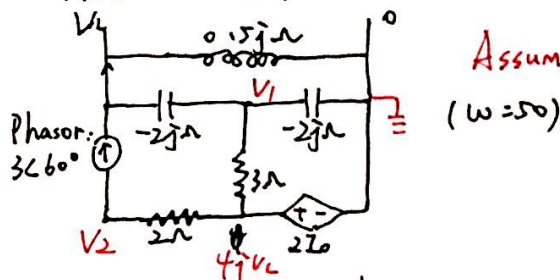Then we need to calculate V_{TH} by turning off V_s and turning on I_s .




Then by KCL,

$$\begin{cases} \frac{V_L - 0}{0.5j} + \frac{V_L - V_1}{-2j} = 3 \angle 60^\circ \\ \frac{V_1 - V_L}{-2j} + \frac{V_1 - 0}{-2j} + \frac{V_1 - 4jV_L}{3} = 0 \\ \frac{V_2 - 4jV_L}{2} = -3 \angle 60^\circ \end{cases} \Rightarrow \begin{cases} -1.5jV_L - 0.5jV_1 = \frac{3}{2} + \frac{3\sqrt{3}}{2}j \quad \textcircled{1} \\ (\frac{1}{3} + j)V_1 - (0.5j + \frac{4}{3}j)V_L = 0 \quad \textcircled{2} \\ \frac{1}{2}V_2 - 2jV_L = -\frac{3}{2} - \frac{3\sqrt{3}}{2}j \quad \textcircled{3} \end{cases}$$

by $\textcircled{2}$
 $\Rightarrow V_1 = \frac{0.5j + \frac{4}{3}j}{\frac{1}{3} + j} V_L$

by $\textcircled{1}$
 $-1.5jV_L - 0.5j \cdot \frac{0.5j + \frac{4}{3}j}{\frac{1}{3} + j} V_L = \frac{3}{2} + \frac{3\sqrt{3}}{2}j \Rightarrow V_L = \frac{-1.0207 + 0.7677j}{-0.561 + 0.115j} = \frac{1.282 \angle -36.75^\circ}{0.561 \angle 11.5^\circ} = 2.28 \angle -48.25^\circ$ V

When $\omega = \infty$ (I_s)

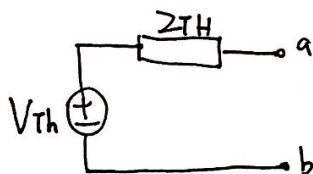

$V_{TH} = 1.282 \angle -36.75^\circ$
 $Z_{TH} = \frac{1}{\frac{1}{8j} + \frac{372}{8j}j} \Omega$

II. For another independent source V_s

Z_{TH} is calculated by the same way but $\omega = 100$.

$I_0 = -\frac{1 \angle 0^\circ}{Z_L} = -\frac{1 \angle 0^\circ}{j \cdot 100 \times 0.01} = j$ A.

$Z_C = \frac{1}{j\omega C} = \frac{1}{j \cdot 100 \cdot 0.01} = -j \Omega$

voltage of dependent source $= 2I_0 = 2j$ V.


$\frac{1 - V_1}{-j} = \frac{V_1}{-j} + \frac{V_1 - 2j}{3}$

$\Rightarrow 3 - 3V_1 = 3V_1 - 2 - jV_1 \Rightarrow (6 - j)V_1 = 5 \Rightarrow V_1 = \frac{5}{6 - j}$

$I_1 = \frac{1 - V_1}{-j} = (\frac{5}{37} + \frac{7}{37}j) A$ $I = I_1 - I_0 = (\frac{5}{37} - \frac{30}{37}j) A$

$Z_{TH} (\omega = 100) = (0.2 + 1.2j) \Omega$

Then we also need to calculate V_{TH} .

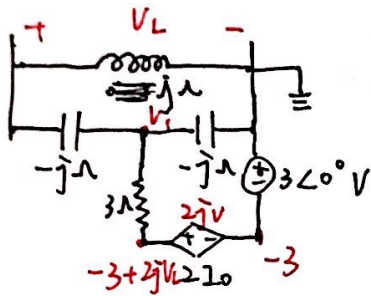


Assume node voltage V_1

Then by KCL,

$$\begin{cases} \frac{V_L - 0}{-j} + \frac{V_L - V_1}{-j} = 0 \\ \frac{V_1 - V_L}{-j} + \frac{V_1 - 0}{-j} + \frac{V_1 - (-3 + 2jV_L)}{3} = 0 \end{cases} \Rightarrow \begin{cases} V_1 = 0 \\ -jV_L + \frac{3 - 2jV_L}{3} = 0 \end{cases}$$
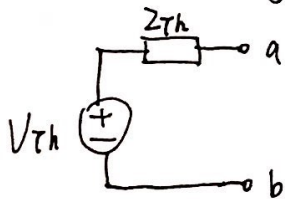
$$\Rightarrow V_L = \frac{1}{j + \frac{2}{3}j} = -0.6j = 0.6 \angle -90^\circ \text{ V.}$$



$$Z_{TH} = (0.2 + 1.2j) \Omega$$

$$V_{TH} = 0.6 \angle -90^\circ \text{ V.}$$