

10'

11.31 Find the rms value of the signal shown in Fig. 11.62.

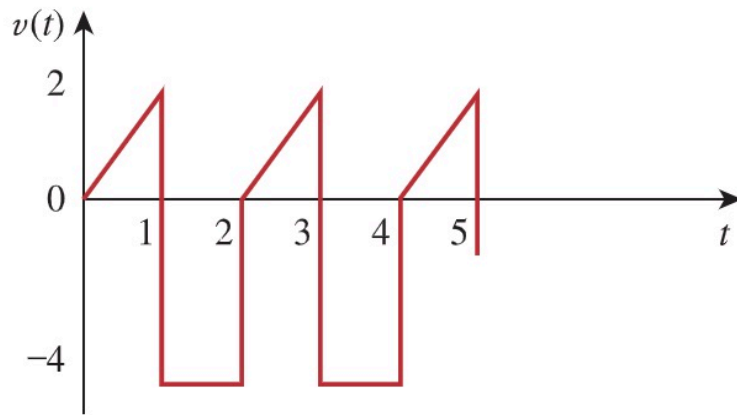


Figure 11.62

For Prob. 11.31.

Exercise 6.1 (10%)

$$\begin{aligned}
 V_{\text{rms}} &= \sqrt{\frac{1}{T} \int_0^T [v(t)]^2 dt} = \sqrt{\frac{1}{2} \left[\int_0^1 4t^2 dt + \int_1^2 16 dt \right]} \\
 &= \sqrt{\frac{1}{2} \left(\left[\frac{4}{3} t^3 \right]_0^1 + [16t]_1^2 \right)} = \sqrt{\frac{1}{2} \left(\frac{4}{3} + 16 \right)} = \boxed{\frac{\sqrt{78}}{3} \approx 2.944 \text{ (V)}}
 \end{aligned}$$

20'

11.21 Assuming that the load impedance is to be purely resistive, what load should be connected to terminals a - b of the circuits in Fig. 11.52 so that the maximum power is transferred to the load?


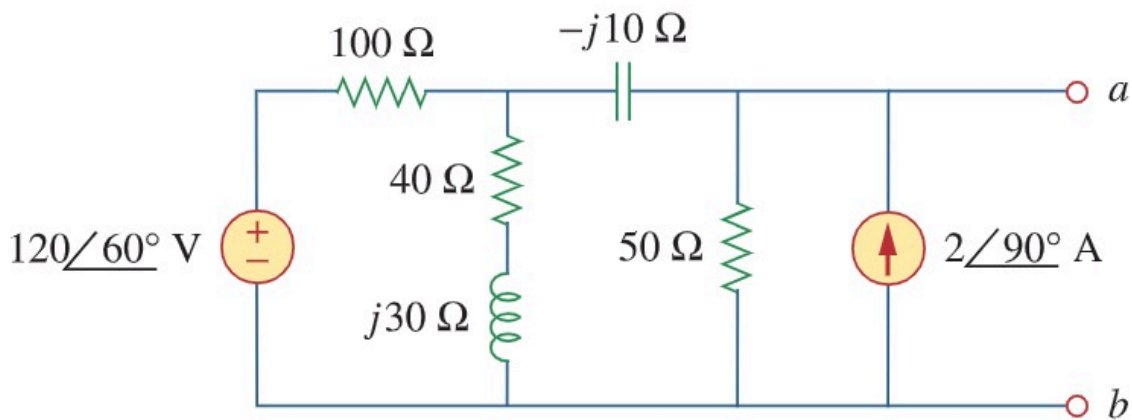


Figure 11.52

For Prob. 11.21.

⇒ turn off all independent sources

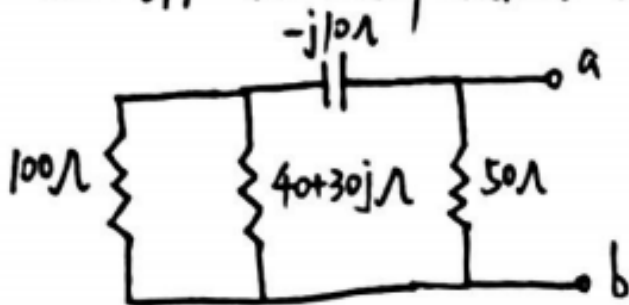

$$\begin{aligned}
 Z_{ab} = Z_{th} &= ((100 \parallel 40 + j30) + (-j10)) \parallel 50 \\
 &= \left(\frac{4000 + j3000}{140 + j30} - j10 \right) \parallel 50 \\
 &= 19.5 + j1.73
 \end{aligned}$$

Z_L purely resistive

$$Z_L = R_L = \sqrt{19.5^2 + 1.73^2} = 19.58 \Omega$$

Exercise 6.3 (30%)

A 240-V rms 60-Hz source supplies a parallel combination of a 5-kW heater and a 30-kVA induction motor whose power factor is 0.82. Determine:


1. the system apparent power
2. the system reactive power
3. Sketch the power triangle for the current system and label $|S|$, P , and Q
4. the power factor of the current system
5. the kVA rating of a capacitor required to adjust the system power factor to 0.9 lagging
6. the value of the capacitor required

Exercise 6.3 (30%).

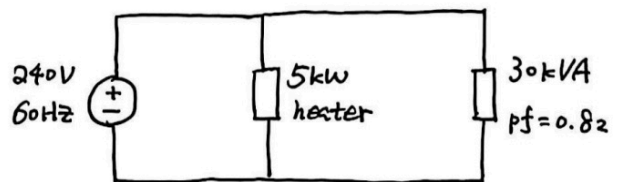(1). $S_{\text{total}} = S_{\text{heater}} + S_{\text{motor}}$


$$= 5 \times 10^3 + 30 \times 10^3 \times 0.82 + 30 \times 10^3 \times \sqrt{1 - 0.82^2}$$

$$\doteq 29.6 + 17.17j \text{ (kVA)}, \text{ lagging, inductive}$$



So, the system apparent power is $|S| = \sqrt{29.6^2 + 17.17^2} \doteq 34.22 \text{ (kVA)}$

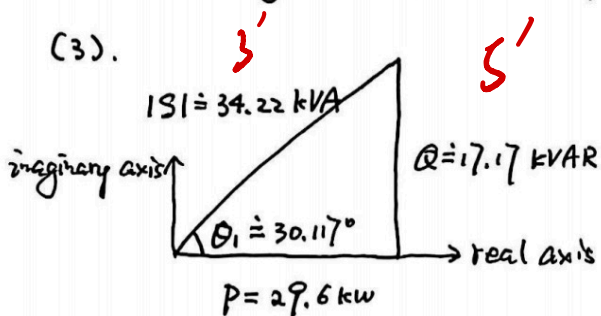(2). the system's reactive power is $Q \doteq 17.17 \text{ (kVAR)}$



(4). $\text{pf} = \cos \theta_1 = \frac{29.6}{34.22} \doteq 0.865$, the system is lagging and inductive.

(5). $P = 29.6 \times 10^3 \text{ W}$, $\tan \theta_1 = \frac{\sin \theta_1}{\cos \theta_1} \doteq 0.58$, $\tan \theta_2 = \frac{\sqrt{1 - \cos^2 \theta_2}}{\cos \theta_2} = \frac{\sqrt{1 - 0.9^2}}{0.9} \doteq 0.484$

$\omega = 2\pi f = 120\pi$, $V = 240$, $Q_c = Q_2 - Q_1 = P(\tan \theta_2 - \tan \theta_1) \doteq -2832.7 \text{ (VAR)}$

(6) so, $C = \frac{P(\tan \theta_1 - \tan \theta_2)}{\omega V^2} = \frac{29.6 \times 10^3 (0.58 - 0.4843)}{120\pi \times 240^2} \doteq 1.305 \times 10^{-4} \text{ F}$

20

12.71 In Fig. 12.73, two wattmeters are properly connected to the unbalanced load supplied by a balanced source such that $\mathbf{V}_{ab} = 208 \angle 0^\circ \text{ V}$ with positive phase sequence.

- Determine the reading of each wattmeter.
- Calculate the total apparent power absorbed by the load.

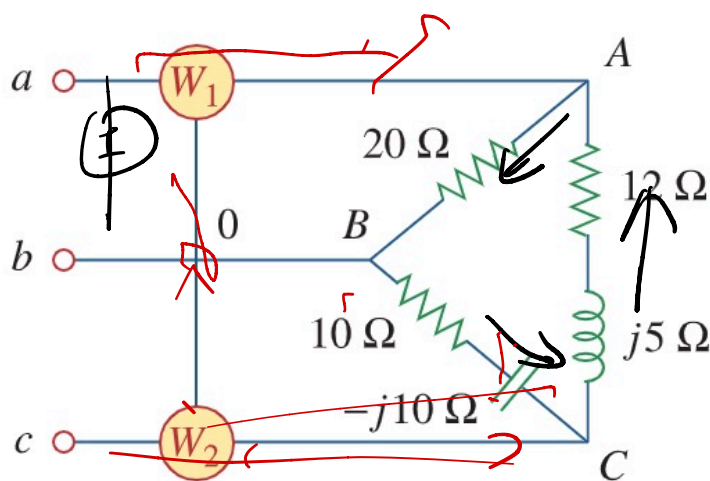


Figure 12.73

For Prob. 12.71.

$$V_{ab} = 208$$

$$V_{bc} = 208 \angle -120^\circ$$

$$V_{ca} = 208 \angle 120^\circ$$

$$I_{AB} = \frac{V}{Z} \text{ A} \quad S_{AB} = I^2 R = \frac{10816}{5} \text{ W}$$

$$I_{BC} = 3.806 - 14.20j \text{ A} \quad S_{BC} = \left(\frac{10816}{5} \text{ W} - \frac{10816}{5} j \text{ VAR} \right)$$

$$I_{CA} = -2.051 + 15.867j \text{ A} \quad S_{CA} = 3072 \text{ W} + 1280 j \text{ VAR}$$

$$P_I = \operatorname{Re}(V_{AB} I_A^*) = \operatorname{Re}[(I_{AB} - I_{CB})^* V_{AB}]$$

$$\approx \frac{12.43 - 13.86j}{2} \approx 2590 \text{ W}$$

$$I_C = (I_{CA} - I_{BC})$$

$$\approx -5.86 + 30.07j \text{ A}$$

$$P_{II} = \operatorname{Re}(V_{CB} I_C^*) \approx 4808 \text{ W}$$

$$S_{AB} = 2663.2 \text{ W}$$

$$S_{BC} = \frac{10816}{5} - \frac{10816}{5}j \text{ VAR}$$



$$S_{AC} = 3072 + 1280j$$

$$|S|_{\text{total}} \approx 7430.9 \text{ VA}$$

Exercise 5.2 (20%)

For the three-phase circuit below, find the average power absorbed by the delta-connected load with

$$Z_{\Delta} = 21 + j24 \Omega.$$

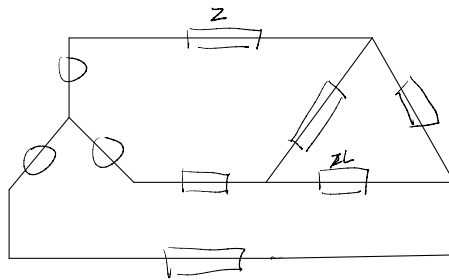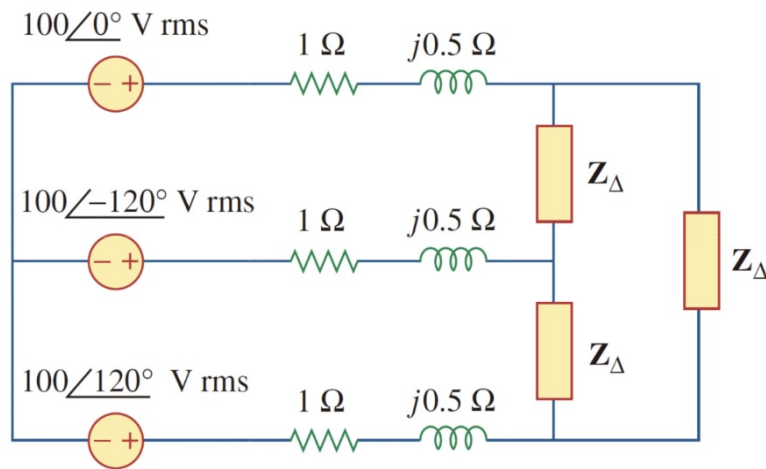

Firstly transform $Z_{\Delta} \Rightarrow Z_Y$

Then $Z_Y = 7 + 8j$ 4'

$Z_{total} = 8 + 8.5j$ 2'

Then $I_a = 8.567 \angle -46.73^\circ$

$I_b = 8.567 \angle -166.73^\circ$

$I_c = 8.567 \angle 73.26^\circ$

$P_b = P_c = P_a = I^2 R_Y$ 4'

$= 513.76 \text{ W}$

The $P_{total} = 3P_a = 1541.28 \text{ W}$ 4'