

Due Date: 23:59, June.5th, 2025

In order to get full marks, you shall write all the intermediate steps of calculation or proof, unless otherwise indicated.

Please box your answers

Exercise 2.1 (15%) Use superposition to find V_o in the circuit below.

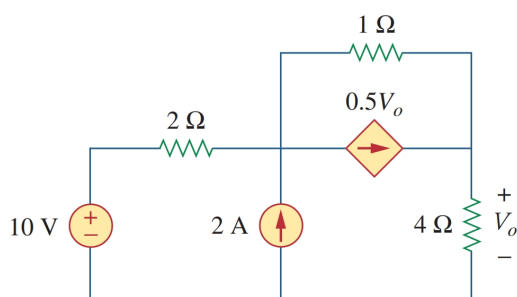


Figure 1: Exercise 2.1

Exercise 2.2 (15%) use source transformation to determine the current and power absorbed by the $8\ \Omega$ resistor

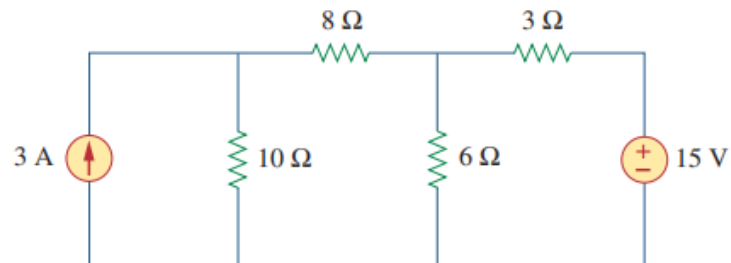


Figure 2: Exercise 2.2

Exercise 2.3(25%)

- (a) (20%) Obtain the Thevenin and Norton equivalent circuits at terminals a-b of the circuit. Draw the circuit
- (b) (5%) Calculate the maximum power transferred to a resistor that connects between terminals a-b.

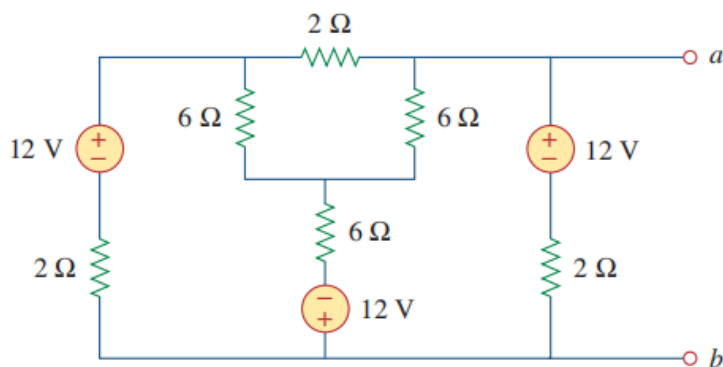


Figure 3: Exercise 2.3

Exercise 2.4 (20%) Find the maximum power transferred to the resistor R

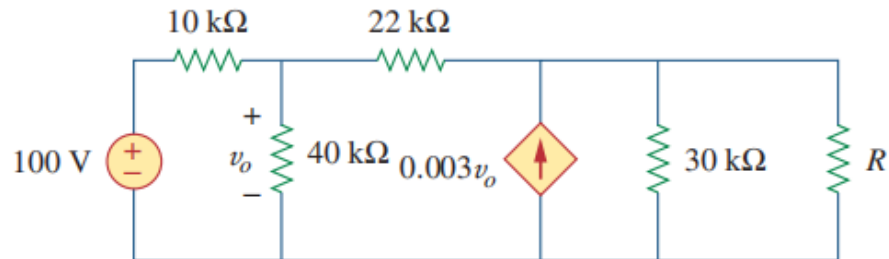


Figure 4: Exercise 2.4

Exercise 2.5(25%)

- (a) (20%) Obtain the Thevenin and Norton equivalent circuits at terminals a-b of the circuit. Draw the circuit.
- (b) (5%) Calculate the power transferred to a resistor of $10\ \Omega$ that connects between terminals a-b.

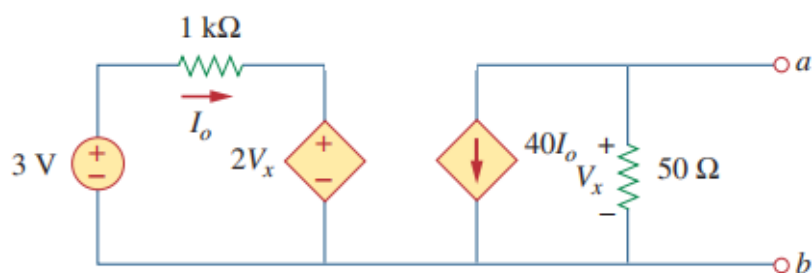


Figure 5: Exercise 2.5