

ECE2150J 2025FA Assignment 6




GLOBAL COLLEGE
SHANGHAI JIAO TONG UNIVERSITY

Due Date: 23:59 December 20th

In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated.

Exercise 6.1 (25%)


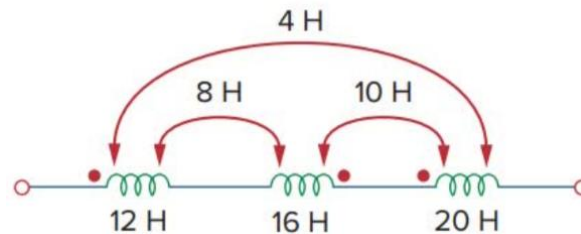
(a) Find the total inductance for the three coupled coils.



$$L = L_1 + L_2 + L_3 - 2M_{12} - 2M_{23} + 2M_{13}$$

$$= 12 + 16 + 20 - 2 \cdot 8 - 2 \cdot 10 + 2 \cdot 4 = 20 \text{ H}$$

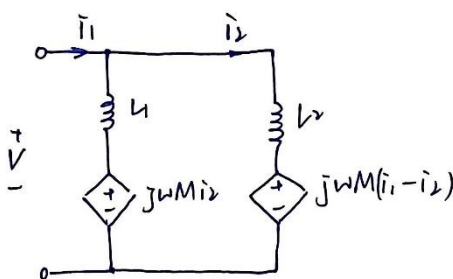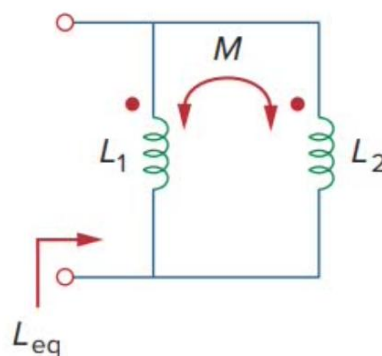(b) Find the equivalent inductance L_{eq} .



$$V = j\omega L_1 (i_1 - i_2) + j\omega M i_2$$

$$V = j\omega L_2 i_2 + j\omega M (i_1 - i_2)$$

$$i_2 = \frac{L_1 - M}{L_1 + L_2 - 2M} i_1$$

$$V = j\omega M i_1 + j\omega (L_2 - M) \frac{L_1 - M}{L_1 + L_2 - 2M} i_1 = j\omega \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} i_1$$

$$V = j\omega L_{eq} i_1, \text{ so } L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$


ECE2150J 2025FA Assignment 6



GLOBAL COLLEGE
SHANGHAI JIAO TONG UNIVERSITY

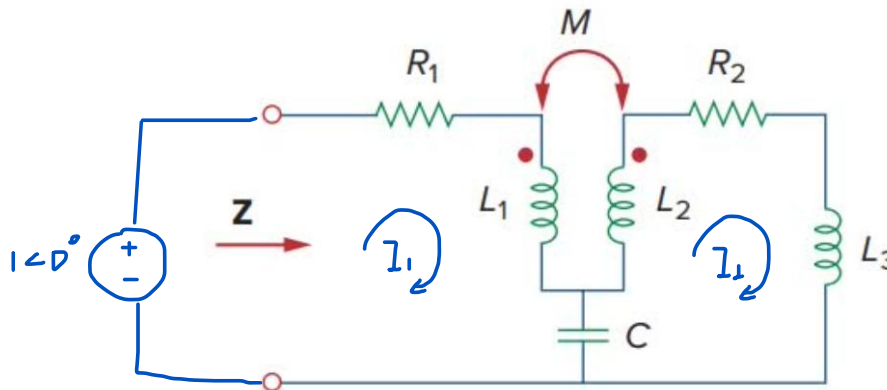Exercise 6.2 (25%)

$R_1 = R_2 = 5\text{k}\Omega$, $M = 20\text{ H}$, $L_1 = 10\text{ H}$, $L_2 = 5\text{ H}$, $L_3 = 10\text{ H}$, $C = 0.1\text{ F}$. Suppose frequency of source is $\omega = 10\text{ k rad/s}$. Find the equivalent impedance Z . All currents flow clockwise.



$$Z_{L1} = j\omega L_1 = j100\text{ k}\Omega$$

$$Z_{L2} = j\omega L_2 = j50\text{ k}\Omega$$

$$Z_M = j\omega M = j200\text{ k}\Omega$$

$$Z_C = \frac{1}{j\omega C} = -j10^{-3}\Omega$$

Apply test voltage $V = 1\angle 0^\circ\text{ V}$

$$V = (R_1 + Z_{L1} + Z_C) I_1 - Z_C I_2 - Z_M I_2$$

$$0 = (Z_C + Z_{L2} + R_2 + Z_{L3}) I_2 - Z_C I_1 - Z_M I_1$$

$$1 = (5 \times 10^3 + j(10^5 - 10^3)) I_1 + j(10^3 - 2 \times 10^5) I_2$$

$$0 = (5 \times 10^3 + j(1.5 \times 10^5 - 10^3)) I_2 + j(10^3 - 2 \times 10^5) I_1$$

$$I_2 = (1.3319 + j0.0444) I_1$$

$$1 = (13879.0 - j166370.7) I_1$$

$$I_1 = 5.99 \times 10^{-6} \angle 85.23^\circ\text{ A}$$

Therefore, $Z = \frac{V}{I_1} = 1.67 \times 10^5 \angle -85.23^\circ \Omega$


ECE2150J 2025FA Assignment 6



GLOBAL COLLEGE
SHANGHAI JIAO TONG UNIVERSITY

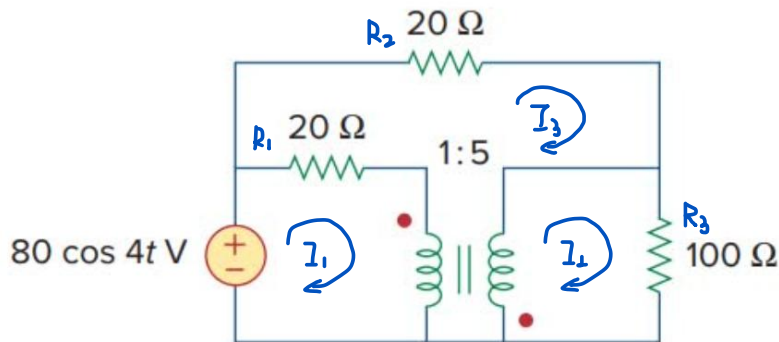Exercise 6.3 (25%)

Determine the average power absorbed by each resistor in this circuit. All currents flow clockwise.



$$\begin{cases} 80 \angle 0^\circ = 20(I_1 - I_2) + V_1 \\ V_2 = 100 I_2 \\ 20 I_2 + V_2 - V_1 + 20(I_1 - I_2) = 0 \end{cases}$$

ideal transformer: $V_2 = -5 V_1$
 $I_1 - I_2 = -5(I_2 - I_1)$

$$V_1 = -20 I_2$$

$$40 I_2 - 20 I_1 + 100 I_2 = 0 \quad 80 = 20 I_1 - 20 I_2 - 20 I_2$$

$$11 I_2 - 4 I_1 = 0 \quad 4 = 5 I_2 - 6 I_2$$

$$I_2 = 1.419 \text{ A}$$

$$I_3 = 0.516 \text{ A}$$

$$I_1 = 5.935 \text{ A}$$

Therefore, $P_{R1} = \frac{1}{2} (I_1 - I_2)^2 R_1 = 203.94 \text{ W}$

$$P_{R2} = \frac{1}{2} I_2^2 R_2 = 20.14 \text{ W}$$

$$P_{R3} = \frac{1}{2} I_3^2 R_3 = 13.31 \text{ W}$$

ECE2150J 2025FA Assignment 6




GLOBAL COLLEGE
SHANGHAI JIAO TONG UNIVERSITY

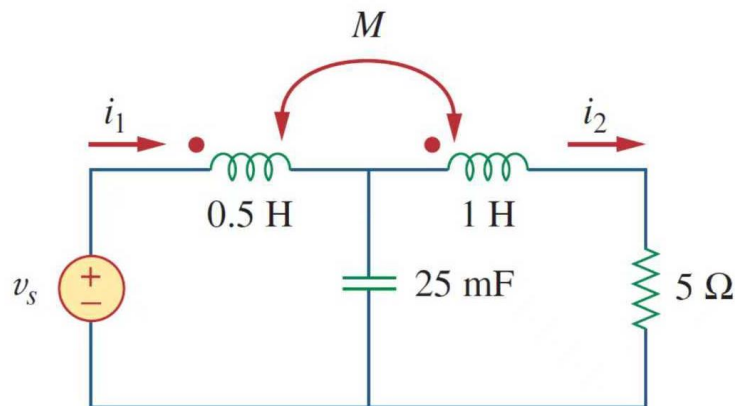
Exercise 6.4 (25%)

$M = 0.2 \text{ H}$, $v_s = 12 \cos 10t \text{ V}$.

Find i_1 and i_2 . Calculate the energy stored in the coupled coils at $t = 15 \text{ ms}$.


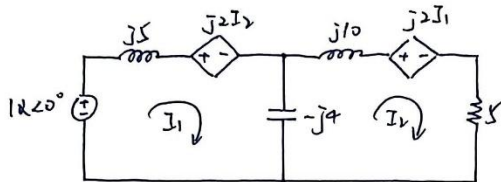
$$V_s = 12 \angle 0^\circ \text{ V} \quad \omega = 10 \text{ rad/s}$$



$$12 - j5I_1 - j2I_2 - (-j4)(I_1 - I_2) = 0$$

$$j10I_2 + j2I_1 + 5I_2 + (-j4)(I_2 - I_1) = 0$$

$$j1I_1 + j6I_2 = 12$$

$$j6I_1 + (j6 + 5)I_2 = 0$$

$$\Rightarrow I_1 = 3.08 \angle 40.73^\circ \quad I_1 = 3.08 \cos(10t + 40.73^\circ) \text{ A}$$

$$I_2 = 2.367 \angle -99.46^\circ \quad I_2 = 2.367 \cos(10t - 99.46^\circ) \text{ A}$$

At $t = 15 \text{ ms}$:

$$10 \times 15 \times 10^{-3} = 0.15 \text{ rad} = 8.594^\circ$$

$$I_1 = 2.008 \text{ A}$$

$$I_2 = -0.036 \text{ A}$$

$$E_1 = \frac{1}{2} L_1 I_1^2 = 1.008 \text{ J}$$

$$E_2 = \frac{1}{2} L_2 I_2^2 = 6.4 \times 10^{-4} \text{ J}$$

$$E_{\text{coupling}} = M I_1 I_2 = -7.22 \times 10^{-3} \text{ J}$$

$$\text{Therefore, } E_{\text{total}} = E_1 + E_2 + E_{\text{coupling}} = 1.001 \text{ J}$$