

Due time: 23:59, Oct. 19th, 2025

In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated. This assignment covers content from chapter 1 to 3.


Exercise 1.1 (20%)

The charge entering the positive terminal of an element is $q = 5 \sin 4\pi t$ mC. While the voltage across the element (plus to minus) is $v = 5 \cos 4\pi t$ V.

- (a) Find the power delivered to the element at $t = 0.3$ s.
- (b) Calculate the energy delivered to the element between 0 and 0.6 s.

Exercise 1.2 (20%)


Please find the voltage v_1 and v_2 in the circuit below by using delta-to-wye transformation.

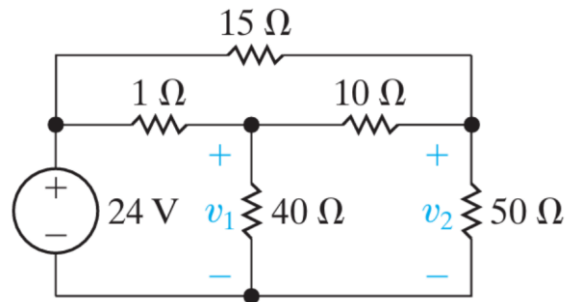

Exercise 1.3 (20%)


In the circuit below

- Determine the number of branches, nodes and meshes.
- Find v_1 and v_g in the circuit when v_o equals 5 V. (Hint: Start at the right end of the circuit and work back toward v_g)

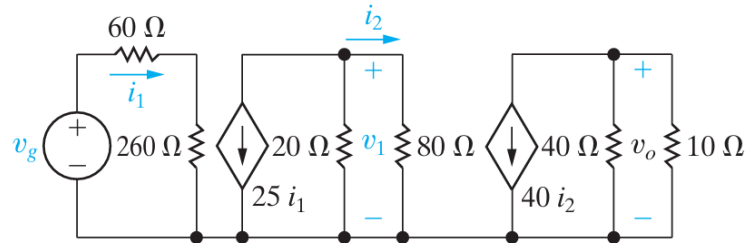


Exercise 1.4 (10%+10%)

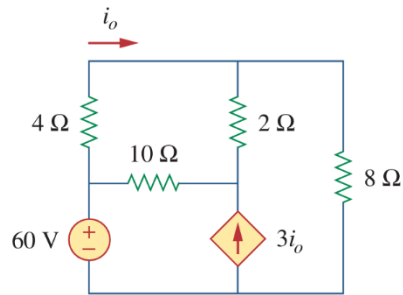(a) Using nodal analysis, find current i_o , in the circuit.




(b) Use nodal analysis to determine the node voltages in the circuit.

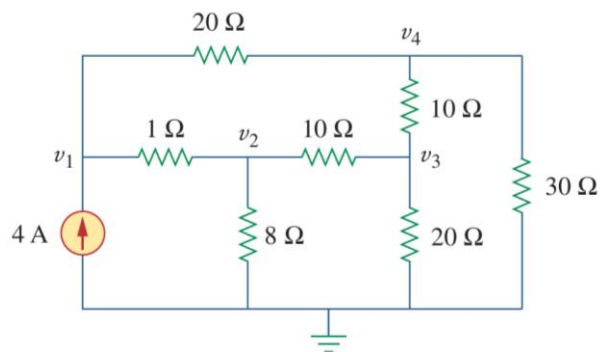

Exercise 1.5 (10%+10%)

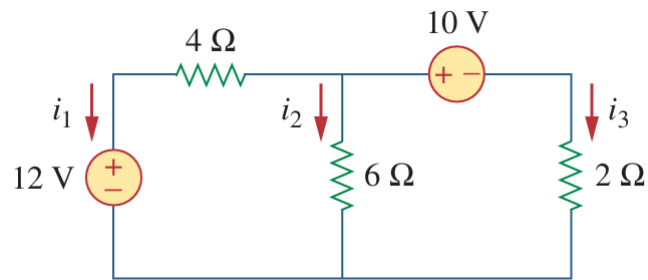(a) Use mesh analysis to obtain i_1 , i_2 and i_3 in the circuit.



(b) Use mesh analysis to find i_1 , i_2 and i_3 in the circuit.

