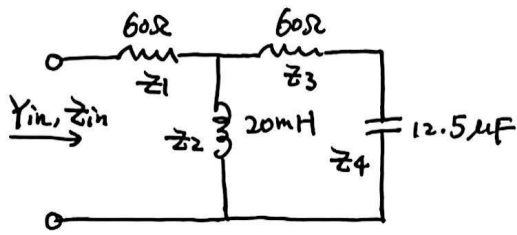


Exercise 5.1 (25%)

(a) (5%)




$$Z_1 = 60 \Omega, Z_2 = 20 \times 10^{-3} \times 50 j = j \Omega$$

$$Z_3 = 60 \Omega, Z_4 = -\frac{1}{12.5 \times 10^{-6} \times 50} j = -1600 j \Omega$$

$$Z_{in} = Z_1 + Z_2 \parallel (Z_3 + Z_4) \doteq 60 + j \Omega$$

$$\text{So, } Y_{in} = \frac{1}{Z_{in}} = \frac{1}{60 + j} \doteq \boxed{1.67 \times 10^{-2} - 2.78 \times 10^{-4} j \text{ (S)}}$$

(b) (10%)

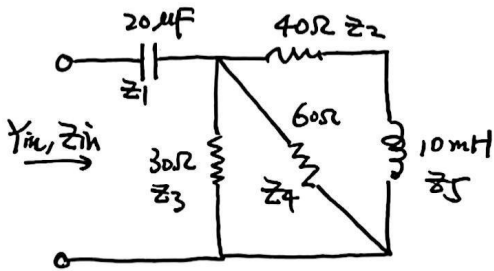

$$Z_1 = -\frac{1}{20 \times 10^{-6} \times 50} j = -1000 j \Omega$$

$$Z_5 = 10 \times 10^{-3} \times 50 j = 0.5 j \Omega$$




$$Z_3 = 30 \Omega, Z_4 = 60 \Omega, Z_2 = 40 \Omega$$

$$Z_{in} = Z_1 + Z_3 \parallel Z_4 \parallel (Z_2 + Z_5) \doteq 13.33 - 999.94 j \Omega$$



$$\text{So, } Y_{in} = \frac{1}{Z_{in}} \doteq \boxed{1.33 \times 10^{-5} + 9.999 \times 10^{-4} j \text{ (S)}}$$

(c) (10%)

Use Y-Δ transformation:

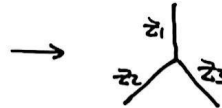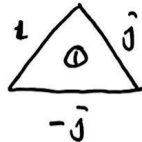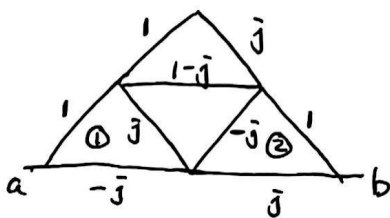

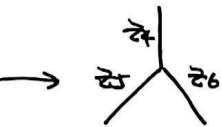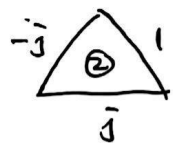
$$\begin{cases} Z_1 = \frac{1 \times j}{1 + j - j} = j \Omega \\ Z_2 = \frac{1 \times (-j)}{1 + j - j} = -j \Omega \\ Z_3 = \frac{j \times (-j)}{1 + j - j} = 1 \Omega \end{cases}$$



$$\begin{cases} Z_4 = \frac{1 \times (-j)}{1 + j - j} = -j \Omega \\ Z_5 = \frac{j \times (-j)}{1 + j - j} = 1 \Omega \\ Z_6 = \frac{1 \times j}{1 + j - j} = j \Omega \end{cases}$$

So, the equivalent circuit is:

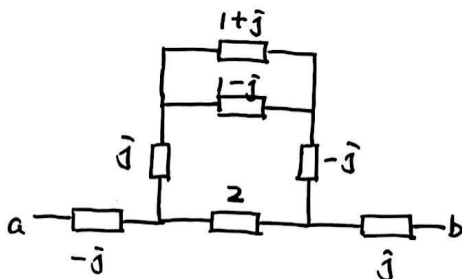

$$Z_{ab} = -j + j + 2 \parallel (j - j + (1 - j) \parallel (1 + j))$$


$$= 0 + 2 \parallel (0 + (1 - j) \parallel (1 + j))$$

$$= 2 \parallel 1$$

$$= \boxed{\frac{2}{3} \text{ (}\Omega\text{)}}$$

Exercise 5.2 (30%)

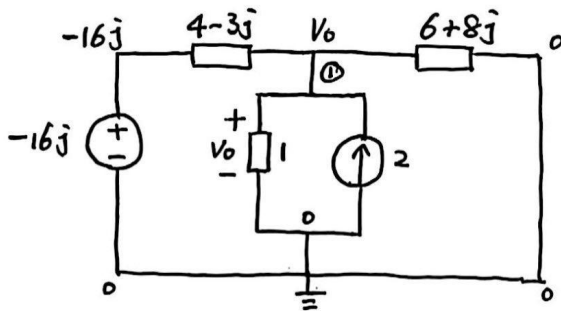(a) (15%) we transform this circuit into \hat{z} -Domain: $\omega = 4 \text{ rad/s}$.



$$\begin{cases} \hat{z}(\frac{1}{12}F) = -\frac{1}{12 \times 4}j = -3j \\ \hat{z}(2H) = 2 \times 4j = 8j \end{cases}$$


use node 0, we have:

$$V_0 + \frac{V_0 + 16j}{4 - 3j} + \frac{V_0}{6 + 8j} = 2 \Rightarrow V_0 = \frac{468}{149} - \frac{328}{149}j \text{ V}$$

transform back to time domain: $\tilde{V}_0 = 3.836 \angle -35.025^\circ$.

$$\boxed{V_0 = 3.836 \cos(4t - 35.025^\circ) \text{ (V)}}$$

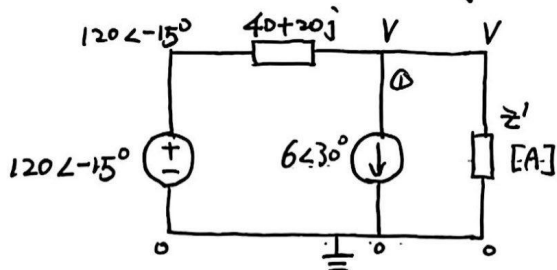(b) (15%) It is already in \hat{z} -Domain.



$$\hat{z}' = 50 \parallel (-30j) = \frac{225}{17} - \frac{375}{17}j \text{ (}\Omega\text{)} = [A]$$


use node 0, we have:

$$\frac{V - 120 \angle -15^\circ}{40 + 20j} + \frac{V}{[A]} + 6 \angle 30^\circ = 0$$

$$\Rightarrow \boxed{V = -111.49 - 54.47j = 124.08 \angle -153.96^\circ \text{ (V)}}$$

Exercise 5.3 (30%)

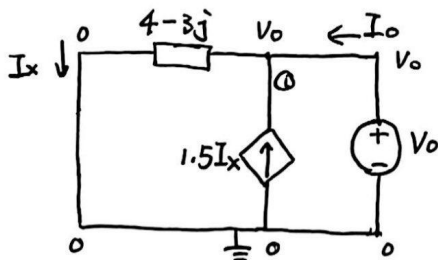(a) (15%) First, we find Z_{Th} , shut off all independent sources:




use node 0, we have:

$$\frac{V_0}{4 - 3j} = I_0 + 1.5I_x, \text{ where } \frac{V_0}{4 - 3j} = I_x$$

$$\Rightarrow \frac{V_0}{I_0} = -2 \times (4 - 3j) = \boxed{-8 + 6j = 10 \angle 143.13^\circ = Z_{Th}}$$



Second, we find V_{Th} ,
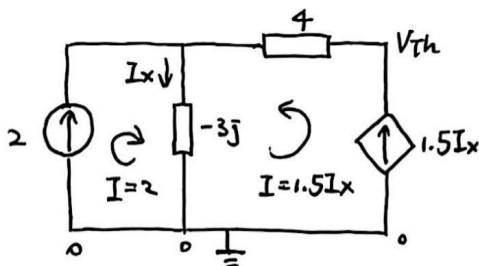
$$2 + 1.5I_x = I_x \Rightarrow I_x = -4 \text{ (A)}$$




$$V_{Th} = 4 \times 1.5I_x - 3j \times I_x = \boxed{-24 + 12j \text{ (V)}} \\ \doteq \boxed{12\sqrt{5} \angle 153.43^\circ \text{ (V)}}$$

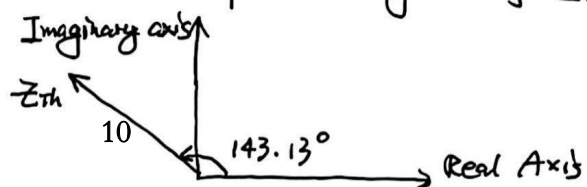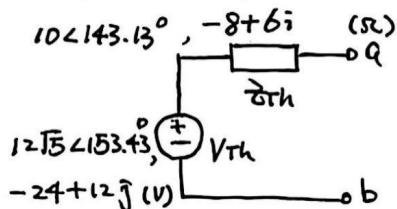So, the Thevenin equivalent circuit at a-b is: and phasor diagram of Z_{Th} is:



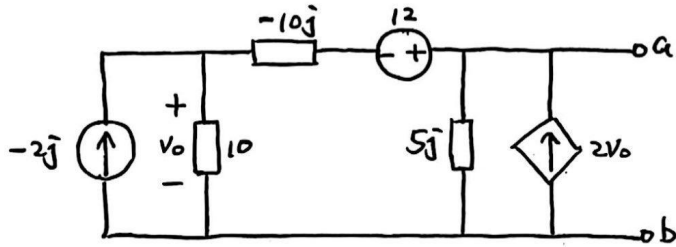
(b) (15%) First, we transform the circuit to \bar{z} -Domain, $\omega = 10 \text{ rad/s}$



$$\bar{z}(10\text{mF}) = -\frac{1}{10 \times 10^{-3} \times 10} j = -10j (\Omega)$$

$$\bar{z}(\frac{1}{2}\text{H}) = \frac{1}{2} \times 10j = 5j (\Omega)$$

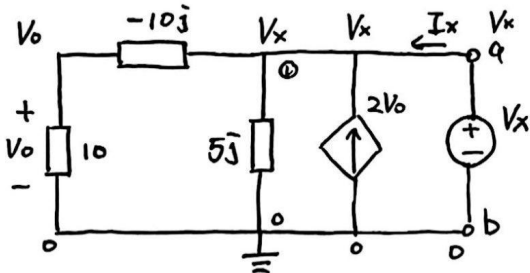Then, we find \bar{z}_N , shut off all independent sources.




use node ①, we have:

$$\frac{V_x}{5j} + \frac{V_x - V_0}{-10j} = 2V_0 + I_x, \text{ where } V_0 = \frac{10}{10-10j} V_x$$

$$\Rightarrow \bar{z}_N = \frac{V_x}{I_x} = \boxed{-\frac{38}{89} + \frac{46}{89}j \approx 0.67 \angle 129.56^\circ (\Omega)}$$

Next, we find I_N :

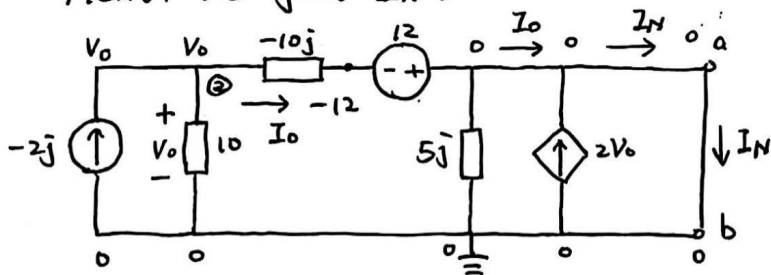


use node ②, we have:


$$\frac{V_0}{10} + \frac{V_0 + 12}{-10j} = -2j \Rightarrow V_0 = -16 - 16j (\text{V})$$

$$\Rightarrow I_N = I_0 + 2V_0 = \frac{V_0 + 12}{-10j} + 2V_0 = \boxed{-\frac{152}{5} - \frac{162}{5}j \approx 44.43 \angle -133.18^\circ (\text{A})}$$


So, the Norton equivalent circuit is:

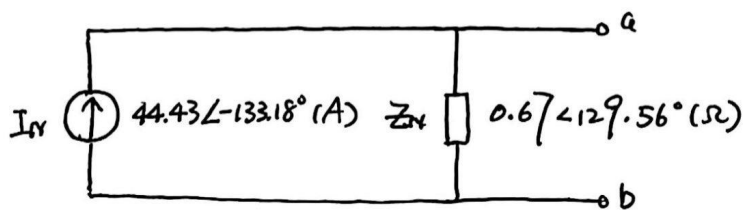

The phasor diagram of \bar{z}_N is:

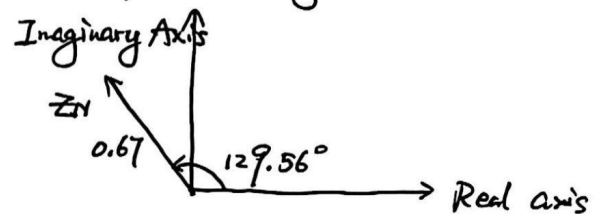

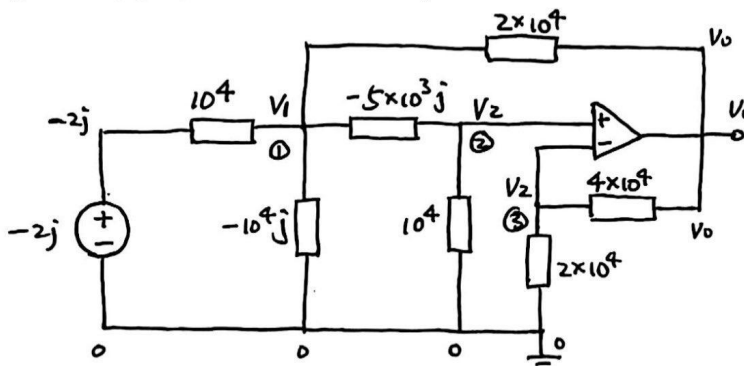Exercise 5.4 (15%) First, we transform the circuit to \bar{z} -Domain, $\omega = 400 \text{ rad/s}$



$$\bar{z}(0.25\mu\text{F}) = -\frac{1}{0.25 \times 10^{-6} \times 400} j = -10^4j (\Omega)$$

$$\bar{z}(0.5\mu\text{F}) = -\frac{1}{0.5 \times 10^{-6} \times 400} j = -5 \times 10^3j (\Omega)$$

$$\text{node ①: } \frac{V_1 + 2j}{10^4} + \frac{V_1}{-10^4j} + \frac{V_1 - V_2}{-5 \times 10^3j} + \frac{V_1 - V_0}{2 \times 10^4} = 0$$

$$\text{node ②: } \frac{V_2 - V_1}{-5 \times 10^3j} + \frac{V_2}{10^4} = 0$$

$$\text{node ③: } \frac{V_2}{2 \times 10^4} + \frac{V_2 - V_0}{4 \times 10^4} = 0$$

$$\Rightarrow \begin{cases} V_0 = -\frac{24}{37} - \frac{144}{37}j (\text{V}) \\ V_1 = -\frac{32}{37} - \frac{44}{37}j (\text{V}) \\ V_2 = -\frac{8}{37} - \frac{48}{37}j (\text{V}) \end{cases}$$

Back to time Domain, $\hat{V}_0 \approx 3.95 \angle -99.46^\circ$, $V_0 = 3.95 \cos(400t - 99.46^\circ) (\text{V})$