


Due time: 23:59, Nov. 18th, 2025

In order to get full marks, you shall write all the intermediate steps of calculation or proof unless otherwise indicated. This assignment covers content from chapters 6 to 8.

Exercise 3.1

The switch in the picture has been in position *A* for a long time. At $t = 0$, the switch moves from position *A* to *B*. The switch is a make-before-break type so that there is no interruption in the inductor current. Find:

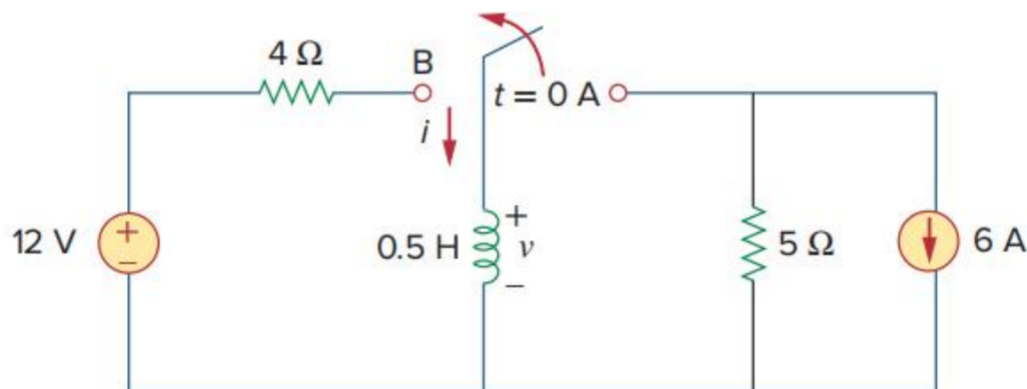
- (a) $i(t)$ for $t > 0$,
- (b) v just after the switch has been moved to position *B*,
- (c) $v(t)$ long after the switch is in position *B*.



- (a) $i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$
- (b) $v = 12 - 4i(0) = \mathbf{36\text{ V}}$
- (c) $v = \mathbf{0\text{ V}}$

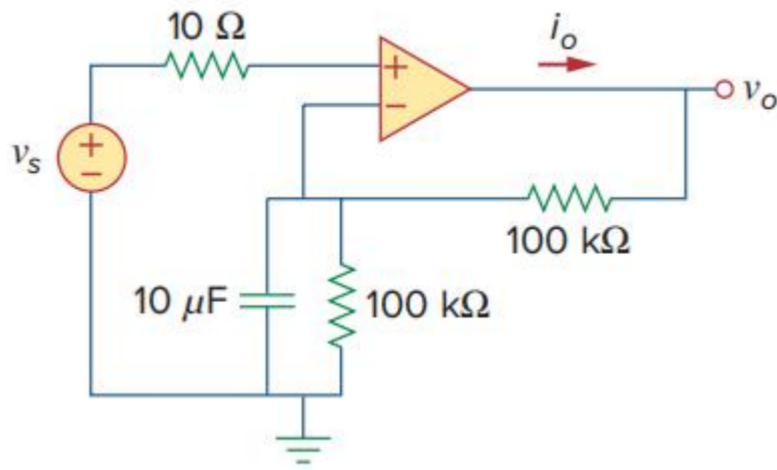Exercise 3.2

Given $V_s = 10[1 - e^{-t}]u(t)$ V, find V_o and i_o .



$$V_o = (20 - 10e^{-t})u(t) \text{ V}$$


$$i_o = 0.1u(t) \text{ mA}$$

Exercise 3.3

The neon lamp fires when its voltage reaches 75 V and turns off when its voltage drops to 30 V. Its resistance is $120\ \Omega$ when on and infinitely high when off.

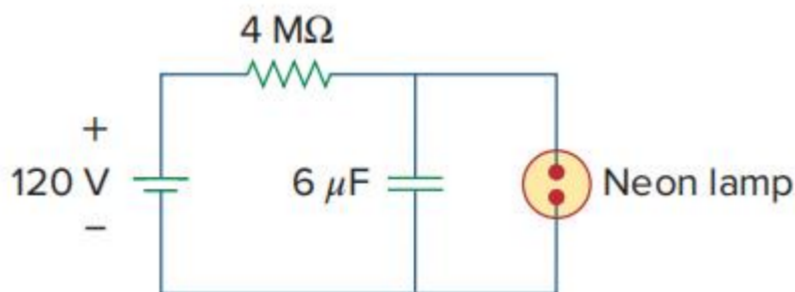- (a) For how long is the lamp on each time the capacitor discharges?
- (b) What is the time interval between light flashes?

Hint: $4\text{M} \gg 120$, when the capacitor discharges, you can consider it as charging the lamp only. And the same as charging process.




(a) **659.7 μs**

(b) **16.636 s**

Exercise 3.4


Determine the time it takes the voltage across the igniter to reach its first peak after switching from A to B . Let $R = 3\Omega$, $C = \frac{1}{30}\text{F}$, and $L = 60\text{mH}$.

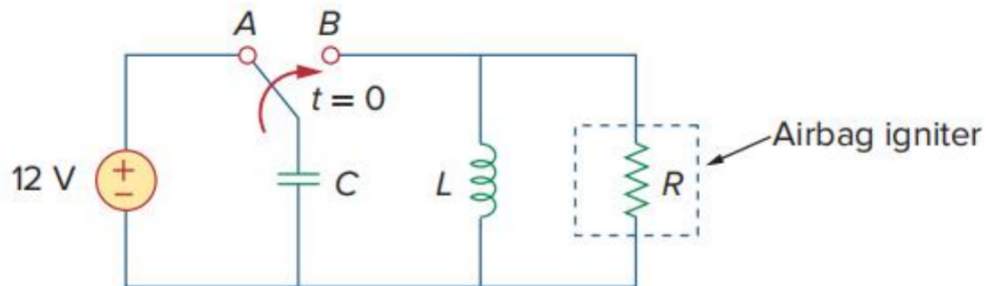



Exercise 3.5

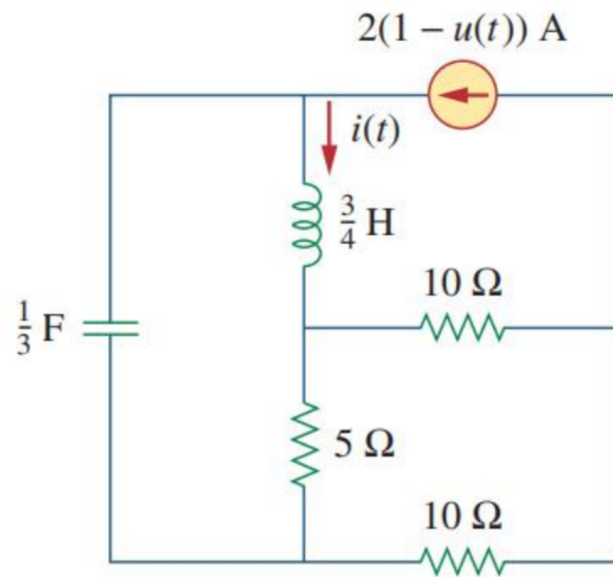- (a) When $t = 0$, what's the energy stored in the capacitor?
- (b) Calculate $i(t)$ for $t > 0$.



(a) $W = 8/3 \text{ J}$

(b) $i(t) = [e^{-4.431t} + e^{-0.903t}] \text{ A}$