



JOINT INSTITUTE
交大密西根学院

ECE2150J Introduction to Circuits

Chapter 14. Frequency Response

Yuljae Cho, PhD
Associate Professor
UM-SJTU Joint Institute, SJTU



14.1 Introduction

$$V_i = A \angle \phi$$
$$\cos \omega t$$
$$V_o = B \angle \phi'$$


Frequency response: Amplitude and phase angle of the sinusoidal source remain constant and **vary the frequency** – $f(\omega)$.

Previously, we have learned how to find voltages and currents at a **constant frequency**.

The sinusoidal steady-state (frequency responses) of circuits are of significance in many applications, especially in **communications and control systems**.

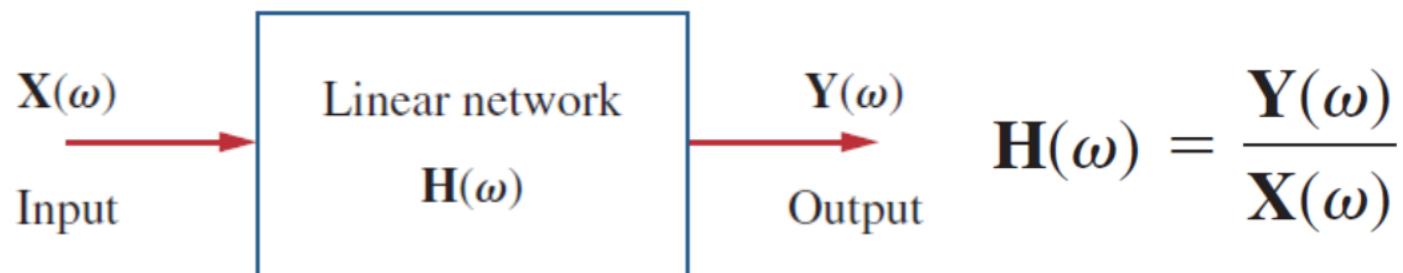14.2 Frequency Response

The frequency response of a circuit is the plot of the circuit's transfer function $H(\omega)$ versus ω .



The transfer function $H(\omega)$ of a circuit is the frequency-dependent ratio of a phasor output $Y(\omega)$ (an element voltage or current) to a phasor input $X(\omega)$ (source voltage or current).

There are four possible transfer functions:

$$\mathbf{H}(\omega) = \text{Voltage gain} = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Current gain} = \frac{\mathbf{I}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Transfer Impedance} = \frac{\mathbf{V}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Transfer Admittance} = \frac{\mathbf{I}_o(\omega)}{\mathbf{V}_i(\omega)}$$

We can obtain the frequency response of the circuit by **plotting the magnitude and phase of the transfer function as the frequency varies.**

The transfer function $H(\omega)$ can be expressed in terms of its numerator $N(\omega)$ polynomial and denominator $D(\omega)$ polynomial as

$$H(\omega) = \frac{N(\omega)}{D(\omega)}$$

N(ω) → zero
D(ω) → pole

- (i) **zeros**: values that result in a zero value of the function
- (ii) **Poles**: values for which the function is infinite


Being a complex quantity, $H(\omega)$ has a **magnitude** and a **phase**: $H\angle\phi$.
The plot of H versus ω is called the **magnitude frequency response**.
The plot of ϕ versus ω is called the **phase frequency response**.

$$H(j\omega) = H(\omega)\angle\phi(\omega)$$

$H(\omega)$: magnitude frequency response

$\phi(\omega)$: phase frequency response

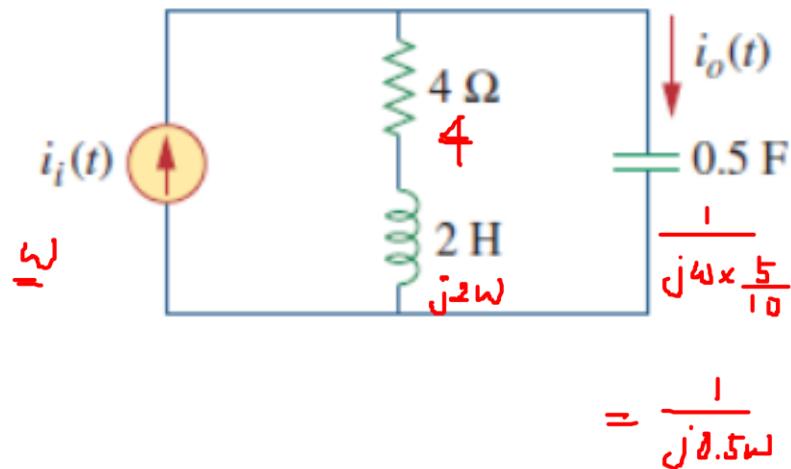Example 1. Find gain i_o/i_i , poles and zeros.



$$\begin{aligned} \frac{i_o}{i_i} &= \frac{(4+j2\omega) \times j0.5\omega}{4+j2\omega + \frac{1}{j0.5\omega}} \times j0.5\omega \\ &= \frac{j2\omega + (j\omega)^2}{j^2\omega + (j\omega)^2 + 1} \Rightarrow \frac{s^2 + 2s}{s^2 + 2s + 1} \\ j\omega &= s \end{aligned}$$

For the circuit in Fig. 14.6, calculate the gain $\mathbf{I}_o(\omega)/\mathbf{I}_i(\omega)$ and its poles and zeros.

Example 14.2

Solution:

By current division,

$$\mathbf{I}_o(\omega) = \frac{4 + j2\omega}{4 + j2\omega + 1/j0.5\omega} \mathbf{I}_i(\omega)$$

or

$$\frac{\mathbf{I}_o(\omega)}{\mathbf{I}_i(\omega)} = \frac{j0.5\omega(4 + j2\omega)}{1 + j2\omega + (j\omega)^2} = \frac{s(s + 2)}{s^2 + 2s + 1}, \quad s = j\omega$$

The zeros are at

$$s(s + 2) = 0 \quad \Rightarrow \quad z_1 = 0, z_2 = -2$$

The poles are at

$$s^2 + 2s + 1 = (s + 1)^2 = 0$$

Thus, there is a repeated pole (or double pole) at $p = -1$.

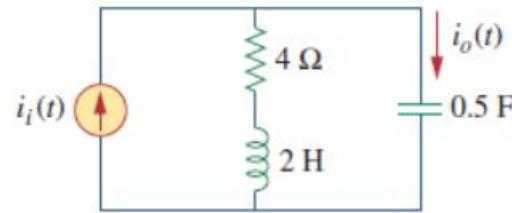



Figure 14.6

For Example 14.2.


Example 14.1 For the RC circuit in Fig.

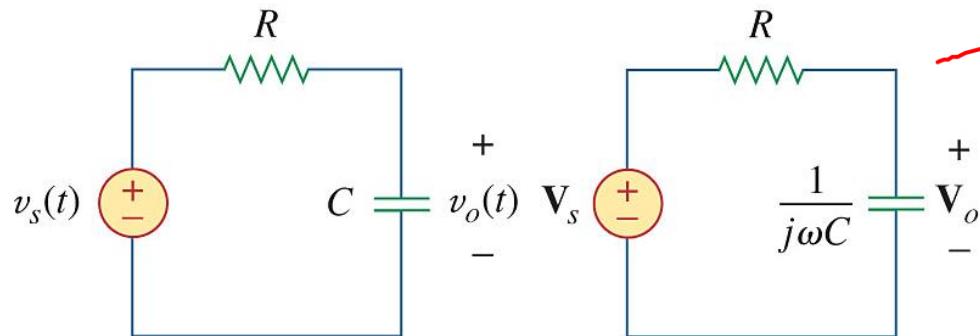14.2(a), obtain the frequency response

$\tilde{V}_o(\omega) / \tilde{V}_s(\omega)$. Let $v_s = V_m \cos \omega t$.


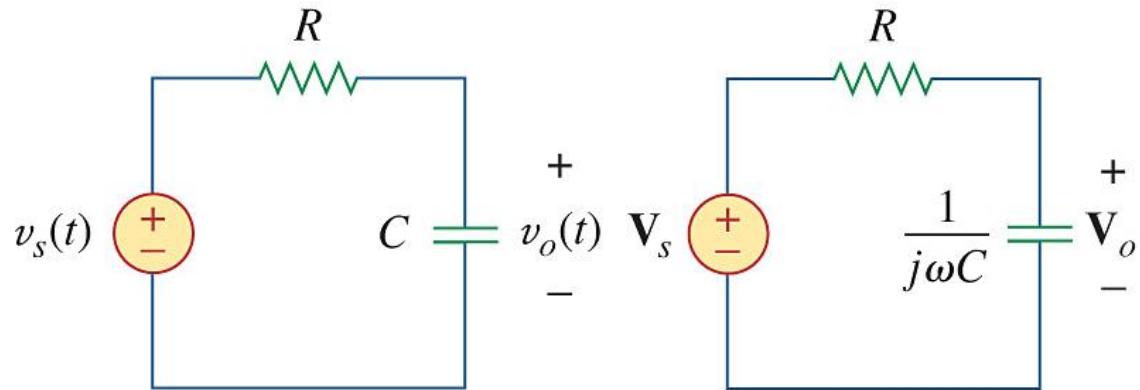
$$\begin{aligned} V_o &= \frac{\frac{1}{j\omega C} \times j\omega C}{R + \frac{1}{j\omega C} \times j\omega C} \times V_s \\ &= \frac{1}{j\omega RC + 1} V_s \quad \frac{1}{RC} = \omega_0 \\ &= \frac{1}{\frac{j\omega}{\omega_0} + 1} \times V_s \end{aligned}$$



Solution :

$$H(j\omega) = \frac{\tilde{V}_o(j\omega)}{\tilde{V}_s(j\omega)} = \frac{1/(j\omega C)}{R + 1/(j\omega C)}$$

$$= \frac{1}{1 + j\omega RC}$$


magnitude $H = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (\omega / \omega_0)^2}}$

phase $\phi = -\tan^{-1}(\omega RC) = -\tan^{-1}(\omega / \omega_0)$


where $\omega_0 = \frac{1}{RC}$

Finds some critical points to plot the responses


magnitude	$\frac{1}{\sqrt{1 + (\omega / \omega_0)^2}}$
phase	$-\tan^{-1}(\omega / \omega_0)$

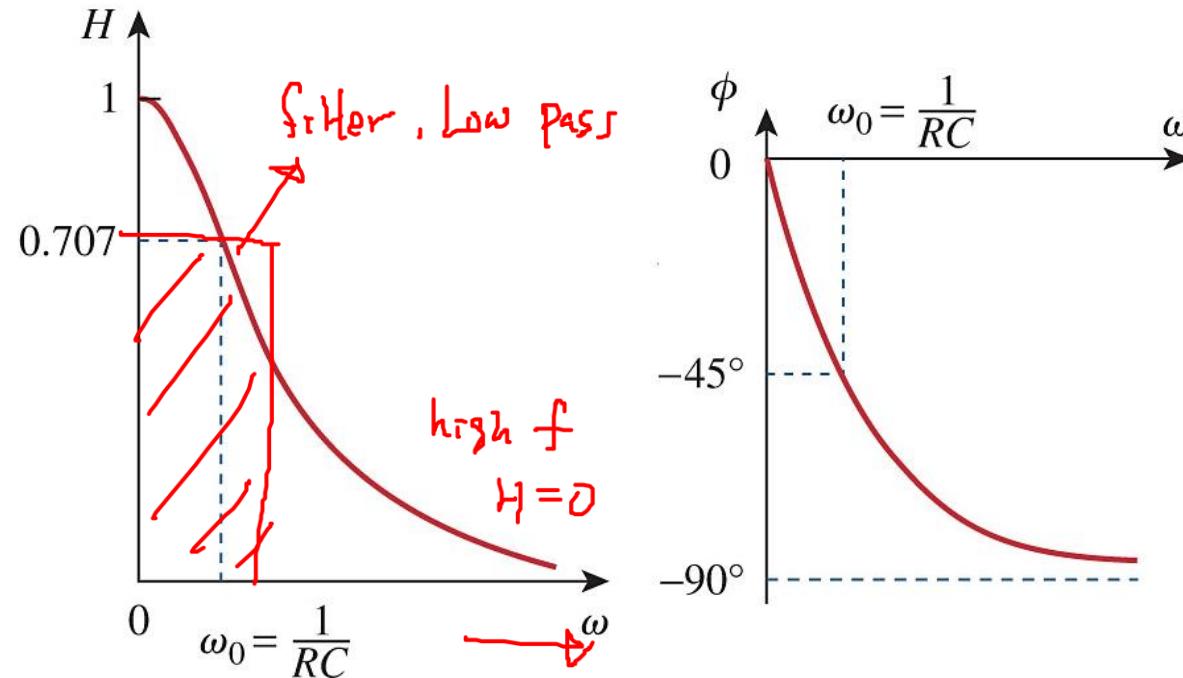

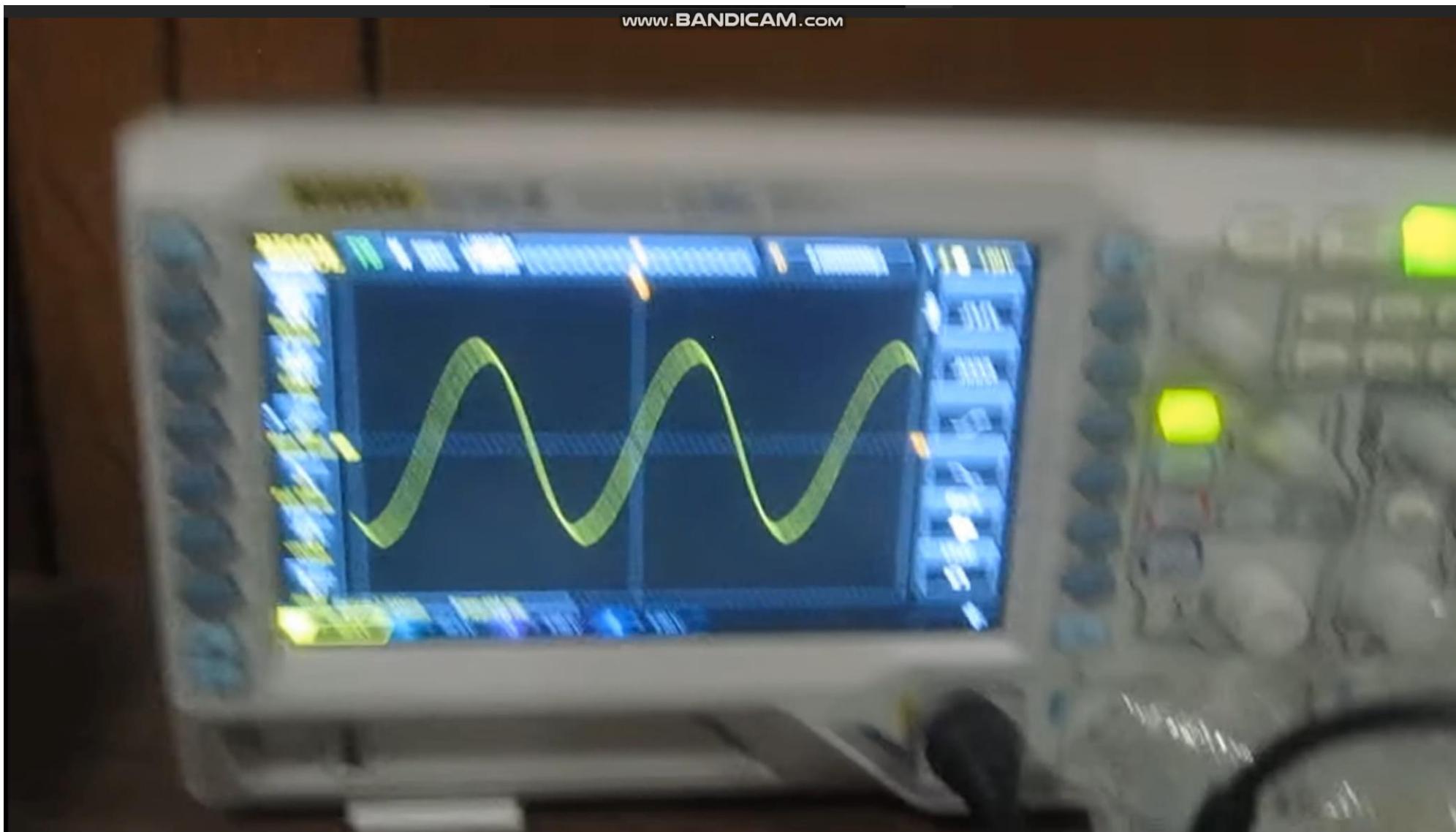When frequency increases magnitude and phase decrease



*Filters

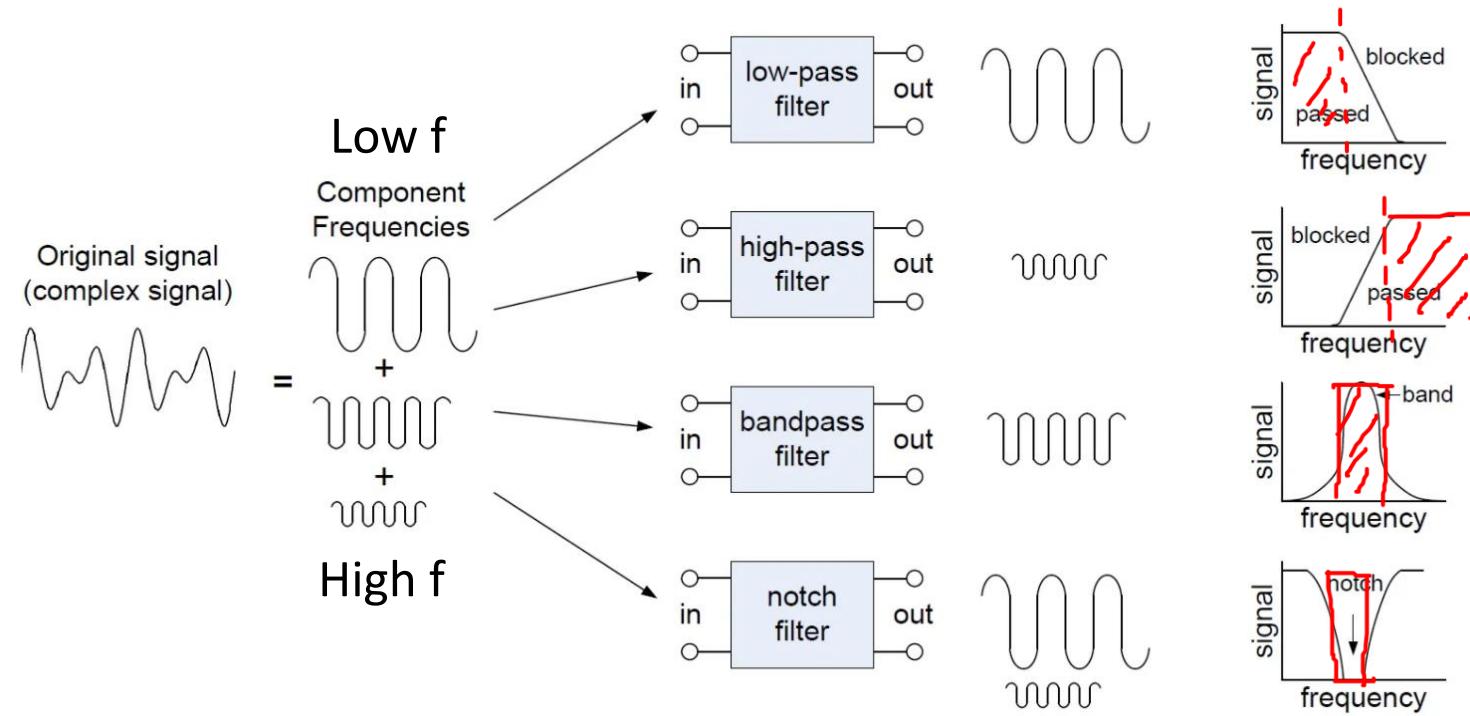

<https://www.allaboutcircuits.com/technical-articles/an-introduction-to-filters/>

Terms "low" and "high" do not refer to any absolute values of frequency, but rather they are **relative values** with respect to the cutoff frequency.

14.3 The Decibel Scale

It is not always easy to get a quick plot of the magnitude and phase of the transfer function. A more **systematic way of obtaining the frequency response is to use Bode plots.**

To use Bode plots, we should take care of two important issues:

- (i) Logarithms
- (ii) Decibels

bel: the ratio of two levels of **power** or power gain G

$$G = \text{Number of bels} = \log_{10} \frac{P_2}{P_1}$$

$10^{G_{\text{bel}}} = \text{linear scale} = 10$
E.g., $10^{\frac{1}{10}} = 100$

0 bel \Leftrightarrow 1 time
1 bel \Leftrightarrow 10 times
2 bels \Leftrightarrow 100 times
...

$\frac{1}{10}^{\text{th}}$


Decibel provides us with a unit of less magnitude. It is $1/10^{\text{th}}$ of a bel and is given by

$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1}$$

$10^{G_{\text{dB}/10}} = \text{linear scale} = 10^{\frac{1}{10}}$

E.g.,
0 dB \Leftrightarrow 1 time
10 dB \Leftrightarrow 10 times
20 dB \Leftrightarrow 100 times
...

$10^1 = 10$

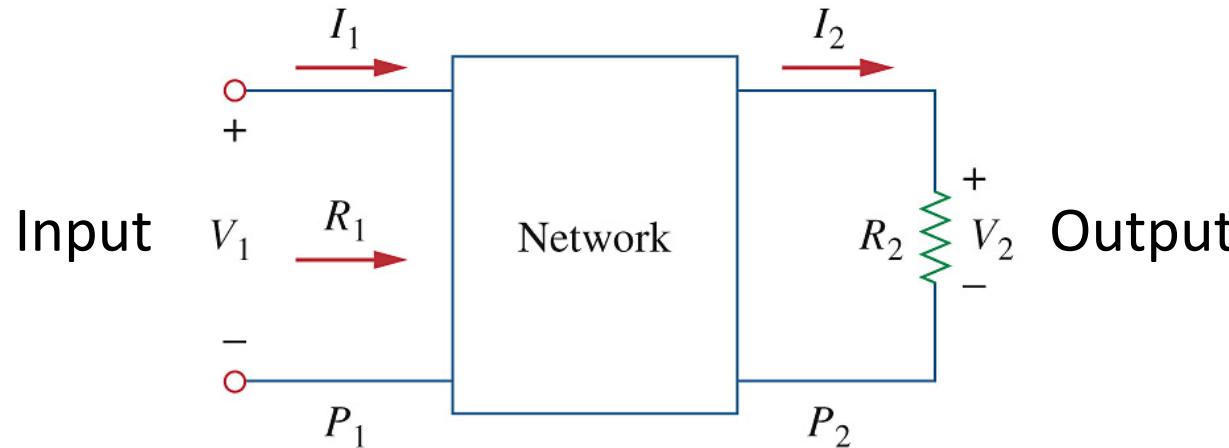

$$G_{dB} = 10 \log_{10} \frac{P_2}{P_1} = 10 \log_{10} \frac{V_2^2/R_2}{V_1^2/R_1}$$

$$= 20 \log_{10} \frac{V_2}{V_1} - 10 \log_{10} \frac{R_2}{R_1}$$

When $R_1 = R_2$

$$G_{dB} = 10 \log_{10} \left(\frac{V_2}{V_1} \right)^2 = 20 \log_{10} \frac{V_2}{V_1}$$

Similarly, for $R_1 = R_2$,

$$G_{dB} = 20 \log_{10} \frac{I_2}{I_1}$$

Transfer functions in dB scale:

The dB value is a logarithmic measurement of the *ratio* of one variable to another of **the same type**. Therefore, it applies in expressing **the transfer function H with the same type** (dimensionless quantities).

For these transfer functions

$$\mathbf{H}(\omega) = \text{Voltage gain} = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} \quad G_{dB} = 10 \log_{10} \left(\frac{V_2}{V_1} \right)^2 = 20 \log_{10} \frac{V_2}{V_1}$$

$$\mathbf{H}(\omega) = \text{Current gain} = \frac{\mathbf{I}_o(\omega)}{\mathbf{I}_i(\omega)} \quad G_{dB} = 20 \log_{10} \frac{I_2}{I_1}$$

Not for those transfer functions

$$\mathbf{H}(\omega) = \text{Transfer Impedance} = \frac{\mathbf{V}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Transfer Admittance} = \frac{\mathbf{I}_o(\omega)}{\mathbf{V}_i(\omega)}$$

Comparisons between power and amplitude in dB scale:

For power (amplitude²)

$10^{\text{G_dB}/10}$ = linear scale

E.g.,

0 dB $\Leftrightarrow P_2/P_1=1$ time

10 dB $\Leftrightarrow P_2/P_1=10$ times

20 dB $\Leftrightarrow P_2/P_1=100$ times

...

For amplitude (voltage and current)

$10^{\text{G_dB}/20}$ = linear scale

E.g.,

0 dB $\Leftrightarrow V_2/V_1=1$ time

10 dB $\Leftrightarrow V_2/V_1=(10)^{0.5}$ time = 3.16 times

20 dB $\Leftrightarrow V_2/V_1=10$ times

...

When we are talking about dB, we do not need to specify power or amplitude.

e.g.,


(i) 10 dB: 10 times in power; 3.16 times in amplitude

(ii) -3 dB: 0.5 times in power; approx. 0.7 times in amplitude

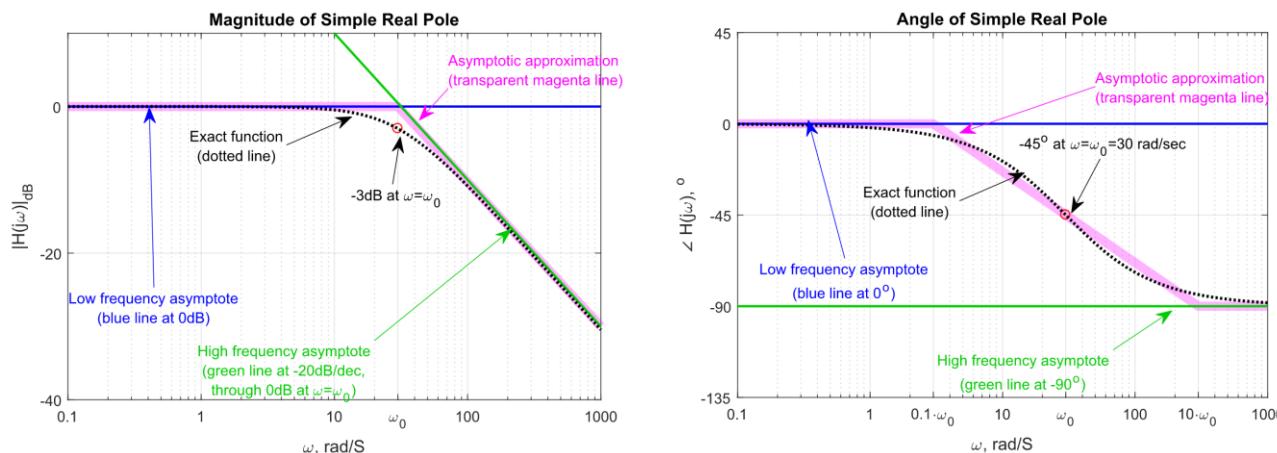14.4 Bode Plots

A more systematic way of locating the important features of the magnitude and phase plots of the transfer function is required.


Bode plots are semi-log plots of the magnitude (in decibels) and phase (in degrees) of a transfer function vs frequency. **Bode plots have become the industry standard.**



Bode plot of the transfer function $H = H\angle\phi$


- The **magnitude**: $H_{dB} = 20 \log_{10} H$
- The **phase**: $\angle H(\omega)$

e.g. RLC system

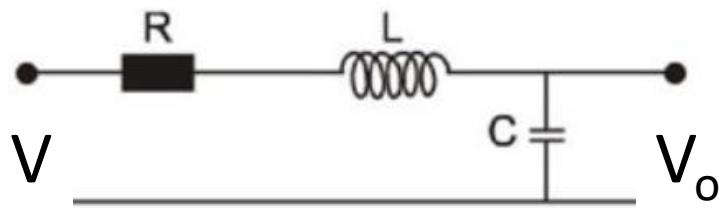

$$\underline{V_o} = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C} V$$
x j\omega C.
x j\omega C.
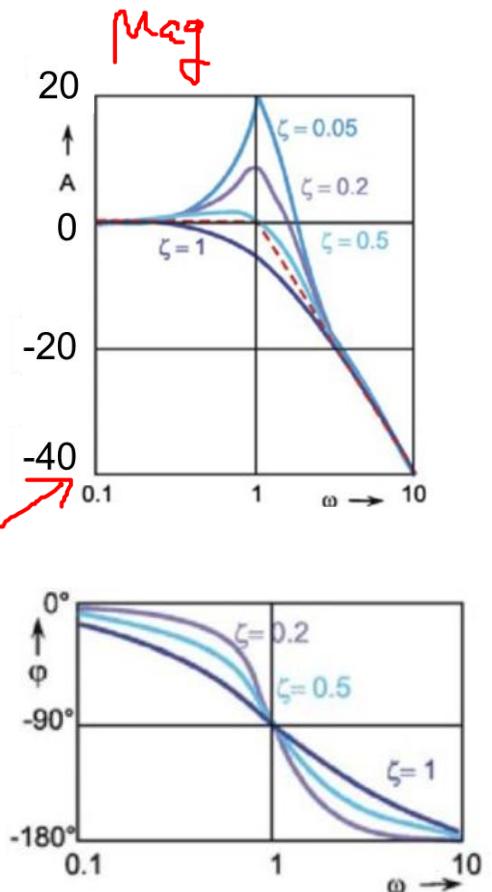
$$H(\omega) = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C} = \frac{1}{(j\omega)^2 + j\omega R/L + 1/LC}$$



Transfer function $\mathbf{H} = H\angle\theta$

- The **magnitude**: $H_{\text{dB}} = 20 \log_{10} H$
- The **phase**: $\angle H(\omega)$

Standard form of $H(\omega)$

$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2] \cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2] \cdots}$$

$H(\omega)$ has **zeros** (z_1, z_2, \dots) and **poles** (p_1, p_2, \dots) and real and imaginary numbers

General form of $H(\omega)$ is

Complex conjugate


$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1) [1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2] \cdots}{(j\omega) (1 + j\omega/p_1) [1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2] \cdots}$$

And, we can have **seven types of different factors**

- { 1. A gain K
- 2. A pole $(j\omega)^{-1}$ or zero $(j\omega)$ at the origin
- 3. A simple pole $1/(1+j\omega/p_1)$ or zero $(1+j\omega/z_1)$
- 4. A quadratic pole $1/[1+j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]$ or zero $[1+j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]$

In constructing a Bode plot, **we plot each factor separately** and then **add them graphically**, i.e. factors can be considered one at a time and then combined additively.

(i) Gain K

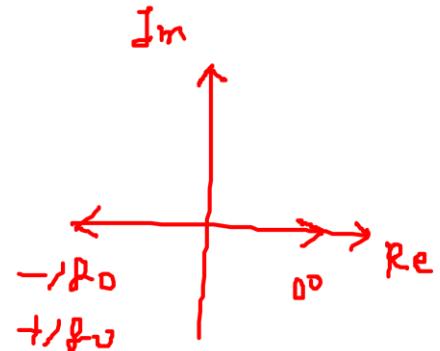


$$1/P_0 = 2^{-50},$$

$$1D \approx 2^0$$

$$H_{dB} = 20 \log_{10} |K| \quad \leftarrow \quad H_{dB} = 20 \log_{10} H$$


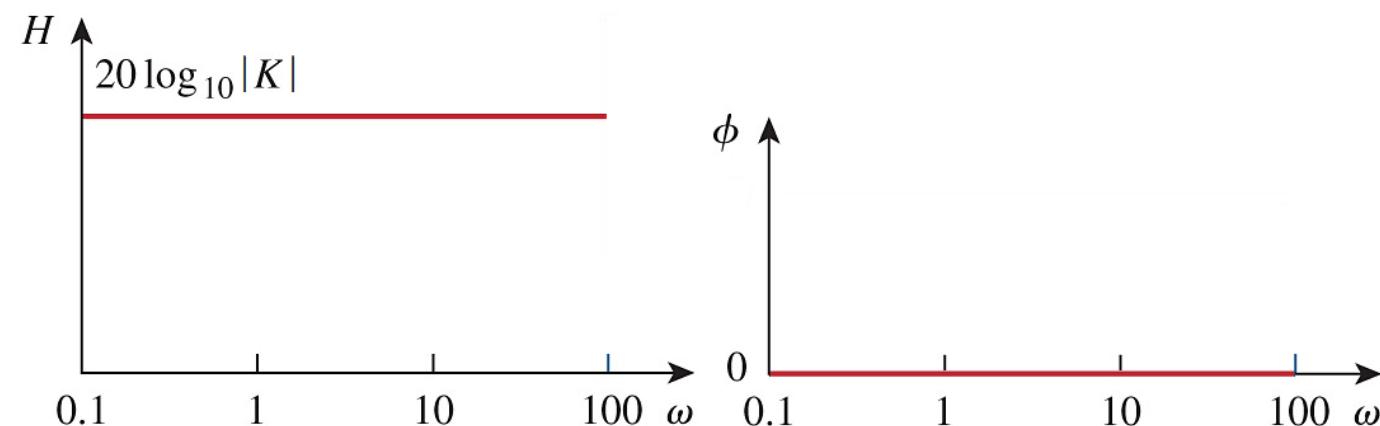
$$\phi = \begin{cases} 0^\circ, & K > 0 \\ \pm 180^\circ & K < 0 \end{cases}$$



(ii) Pole/zero at the origin

A pole $(j\omega)^{-1}$ or zero $(j\omega)$ at the origin

$$\text{zero. } \left\{ \begin{array}{l} H_{dB} = 20 \log_{10} |j\omega| = 20 \log_{10} \sqrt{\omega^2} \\ \phi = 90^\circ \end{array} \right. \xrightarrow{\quad \ln e^{j\phi} \quad} \left\{ \begin{array}{l} \text{i) } \omega = 0.1, H_{dB} = -20 \\ \text{ii) } \omega = 1, H_{dB} = 0 \\ \text{iii) } \omega = 10, H_{dB} = 20 \end{array} \right.$$

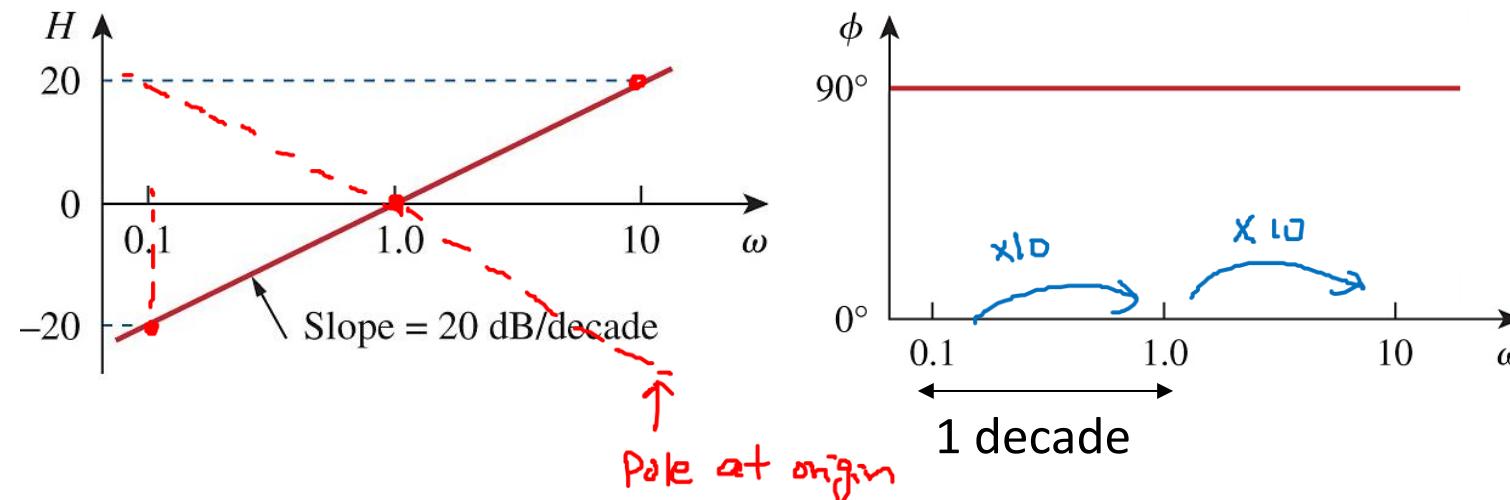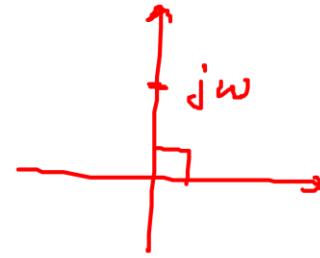

The slope of the magnitude plot is **20 dB/decade**, where decade means a group or series of ten.

(ii) Pole/zero at the origin – other cases

- $(j\omega)^{-1}$

$$-20 \log_{10} |j\omega|$$

$$H_{dB} = 20 \log_{10} |(j\omega)^{-1}| = -20 \log_{10} \omega$$

Angle of $(j\omega)^{-1} = -90^\circ$

i) $\omega = 0.1, H_{dB} = 20$

ii) $\omega = 1, H_{dB} = 0$

iii) $\omega = 10, H_{dB} = -20$

- $(j\omega)^n$ or $(j\omega)^{-n}$ cases

\rightarrow slope is diff. shape same.

$$-20N \log_{10} \omega$$


$$H_{dB} = 20 \log_{10} |(j\omega)^N| = 20N \log_{10} \omega$$

Angle of $(j\omega)^N = j + j + \dots = 90N^\circ$

i) $\omega = 0.1, H_{dB} = 20 \cdot N$

ii) $\omega = 1, H_{dB} = 0$

iii) $\omega = 10, H_{dB} = -20 \cdot N$

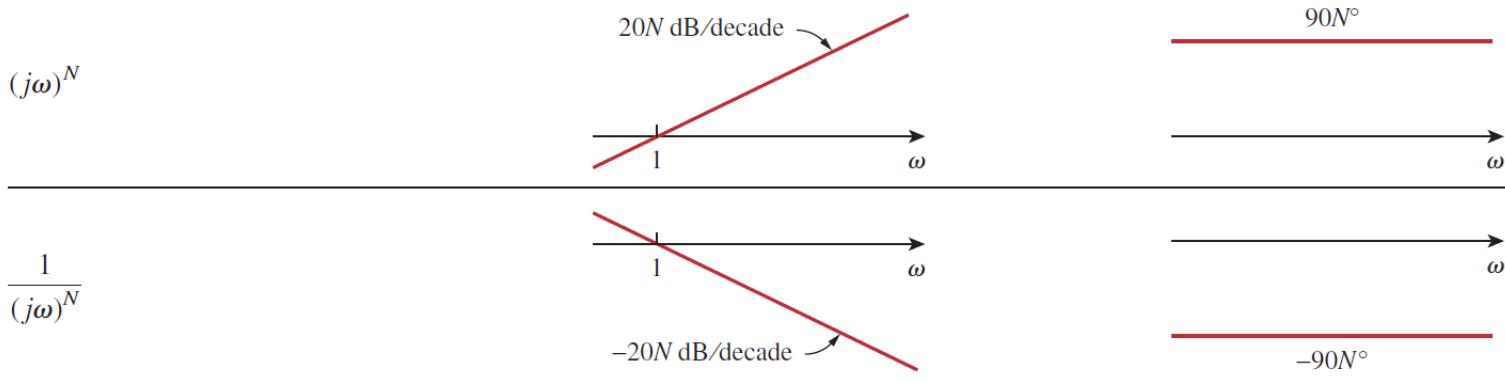

(iii) Simple pole/zero

A simple zero ($1+j\omega/z_1$)




$$H_{dB} = 20 \log_{10} \left| 1 + j\omega / z_1 \right| \rightarrow a+jb \rightarrow \tan^{-1} \frac{b}{a}$$

$$\begin{aligned} & 0.1z_1 \quad z_1 \quad 10z_1 \\ & \sqrt{1^2 + \left(\frac{\omega}{z_1}\right)^2} \quad \sqrt{1^2 + 1^2} \end{aligned}$$

- i) $\omega = 0.1z_1, H_{dB} = 20 \log(1) = 0$
- ii) $\omega = z_1, H_{dB} = 20 \log(\sqrt{2}) = 3 \text{ dB} \approx 0$
- iii) $\omega = 10z_1, H_{dB} = 20 \log 10 = 20$

- i) $\omega = 0.1z_1, \phi = 5.71^\circ \approx 0$
- ii) $\omega = z_1, \phi = 45^\circ$
- iii) $\omega = 10z_1, \phi = 84^\circ \approx 90^\circ$

$\tan^{-1} 0.1$

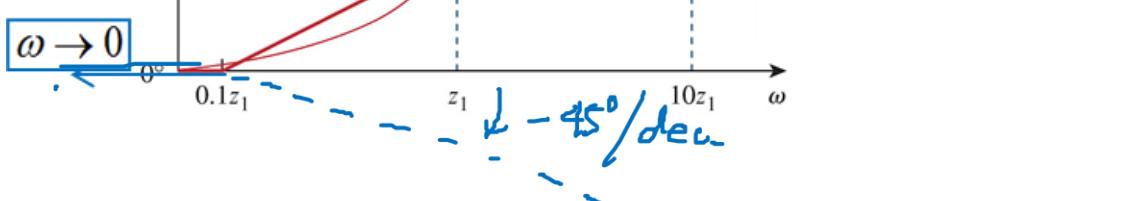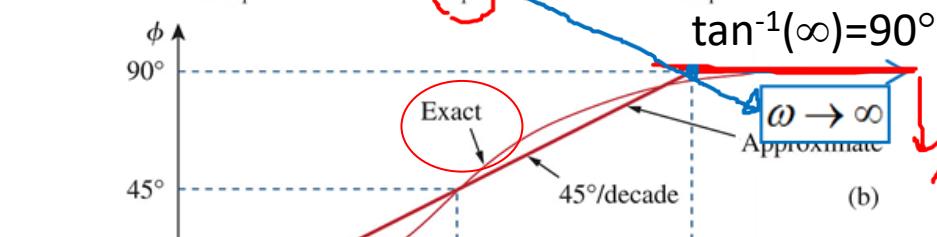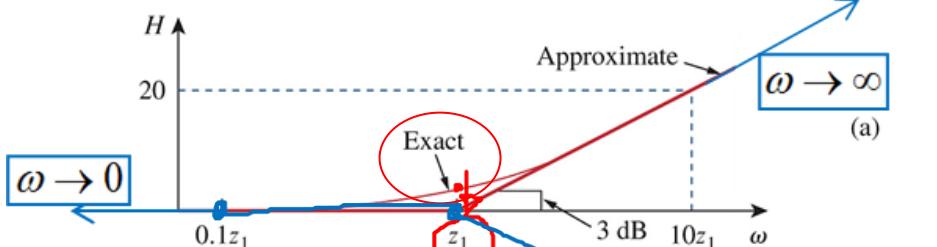


Straight-line approximation

z_1 : corner frequency or break frequency


$\max 90^\circ$

(iii) Simple pole/zero – other cases

pole $1/(1+j\omega/p_1)$

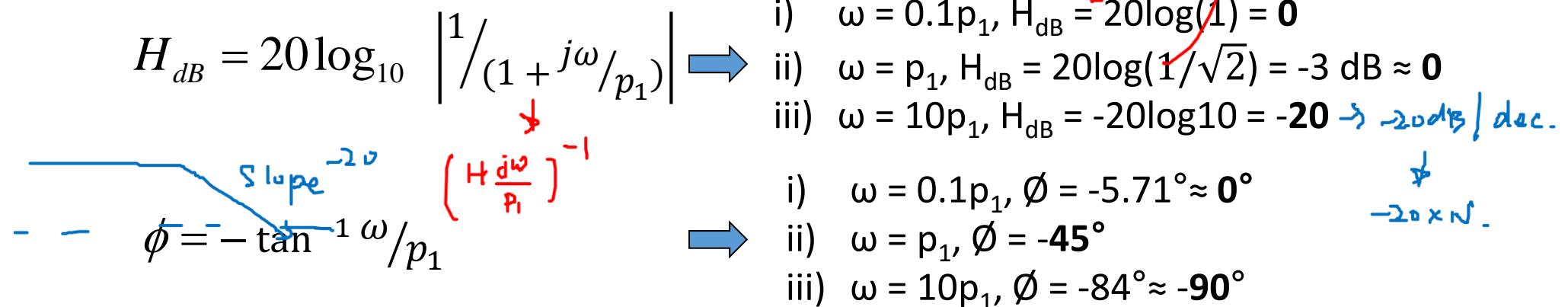

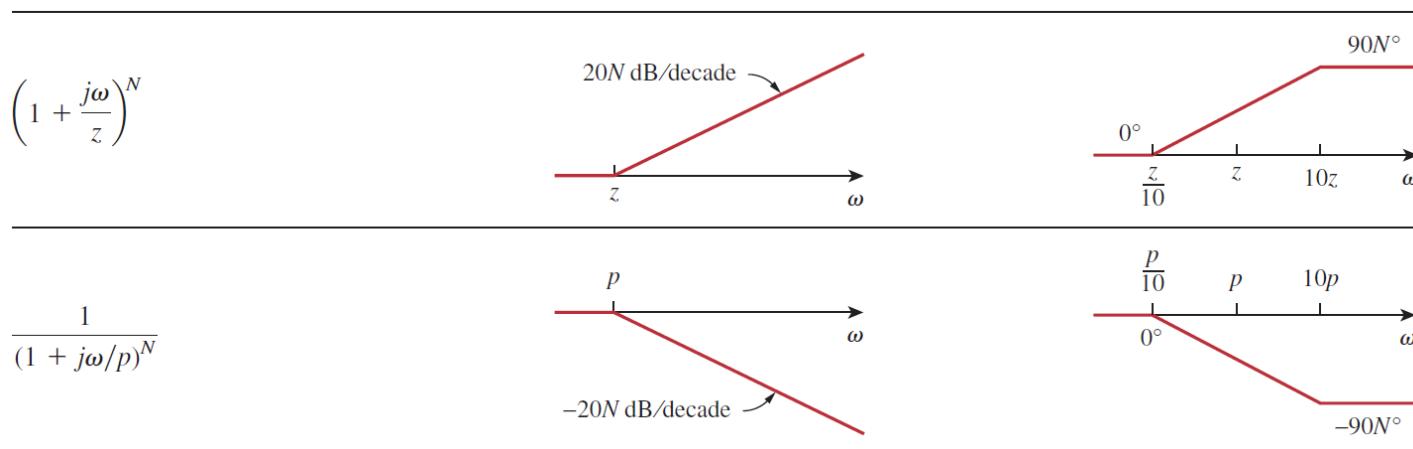In general, for $(1+j\omega/z_1)^N$, where N is an integer → Multiply N to H_{dB} and ϕ



(iv) Quadratic pole/zero

+ something

Pole: $1/(1+j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2)$


$$H_{dB} = -20 \log_{10} \left| 1 + 2\zeta_2(j\omega/\omega_n) + (j\omega/\omega_n)^2 \right|$$

$$-20 \log_{10} \left| \left[1 - \frac{\omega^2}{\omega_n^2} \right] + j2\zeta_2 \frac{\omega}{\omega_n} \right|$$

$$\zeta < 0.707$$

$$= -20 \log_{10} \sqrt{\left[1 - \frac{\omega^2}{\omega_n^2} \right]^2 + 4\zeta_2^2 \left(\frac{\omega}{\omega_n} \right)^2}$$

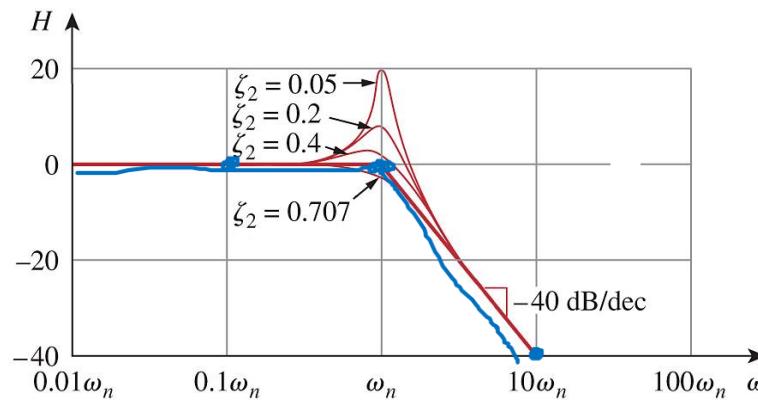- i) $\omega = 0.1\omega_n, H_{dB} = -20 \log_{10} 1 = 0$
- ii) $\omega = \omega_n, H_{dB} = -20 \log(\sqrt{4}) = -6 \text{ dB} \approx 0$
- iii) $\omega = 10\omega_n \rightarrow \left[1 - \frac{\omega^2}{\omega_n^2} \right] > j2\zeta_2 \frac{\omega}{\omega_n} \rightarrow$
 $H_{dB} = -20 \log_{10} \sqrt{\left[1 - \frac{\omega^2}{\omega_n^2} \right]^2} = -40 \text{ dB.}$



(iv) Quadratic pole/zero




Pole: $1/[1+j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2]$

$$\phi = -\tan^{-1}\left(\frac{2\zeta_2\omega/\omega_n}{1-\omega^2/\omega_n^2}\right) \quad -\frac{\omega^2}{\omega_n^2}$$

i) $\omega = 0.1\omega_n, \phi = -11.31^\circ = 0^\circ$

ii) $\omega = \omega_n, \phi = -90^\circ$

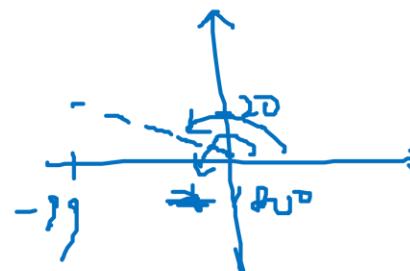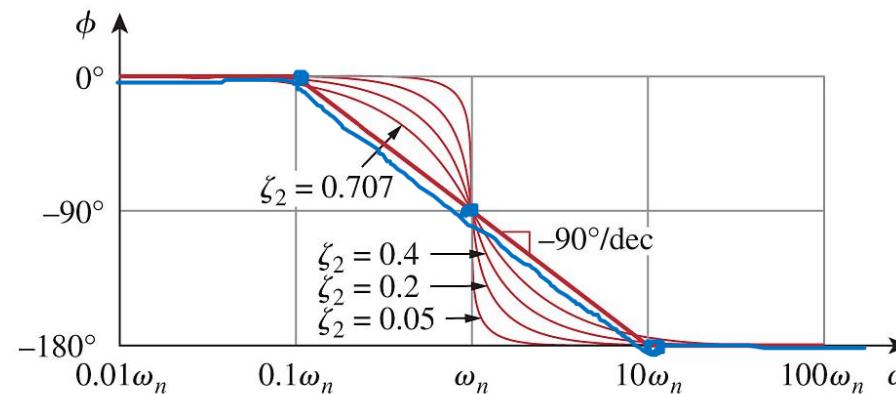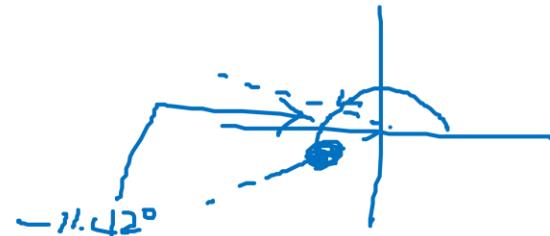iii) $\omega = 10\omega_n \rightarrow 1/(-99+j20) \rightarrow \phi = -180^\circ$



(iv) Quadratic pole/zero – other cases

Zero $[1+j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2]$

i) $\omega = 0.1\omega_n, H_{dB} = 20\log_{10} 1 = 0$

ii) $\omega = \omega_n, H_{dB} = 20\log(\sqrt{4}) = 6 \text{ dB} \approx 0$

iii) $\omega = 10\omega_n \rightarrow \left[1 - \frac{\omega^2}{\omega_n^2}\right] > j2\zeta_2 \frac{\omega}{\omega_n} \rightarrow$


$$H_{dB} = 20\log_{10} \sqrt{\left[\left[1 - \frac{\omega^2}{\omega_n^2} \right] \right]^2} = +40$$

i) $\omega = 0.1\omega_n, \phi = +11.31^\circ = 0^\circ$

ii) $\omega = \omega_n, \phi = 90^\circ$

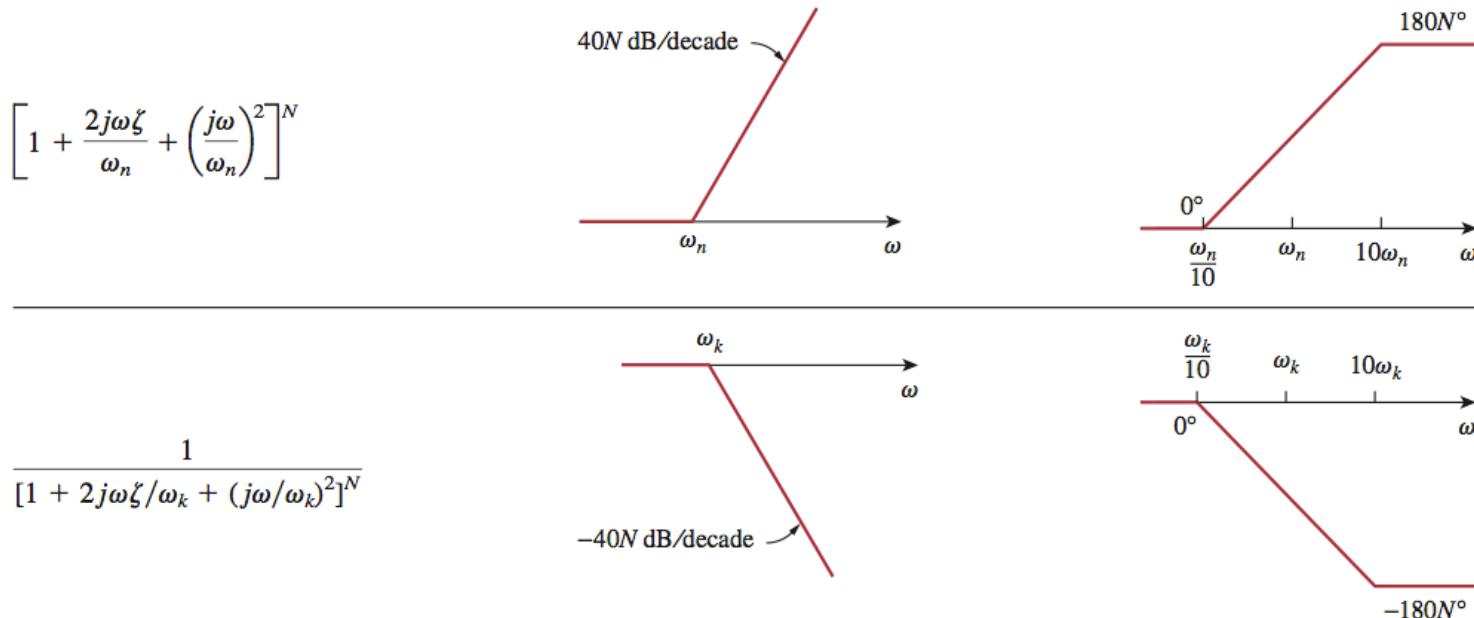iii) $\omega = 10\omega_n \rightarrow -99+j20 \rightarrow \phi = 180^\circ$








In general, for quadratic pole and zero to the power of N
→ Multiply N to the output H_{dB} and ϕ



Summary



Zeros: upward turn

Poles: downward turn

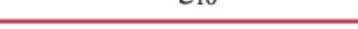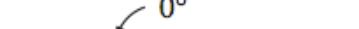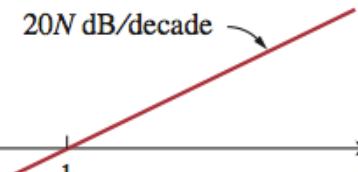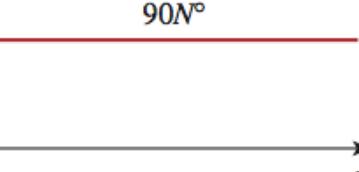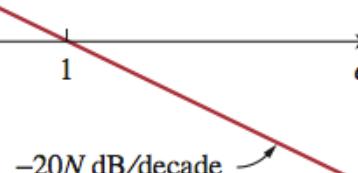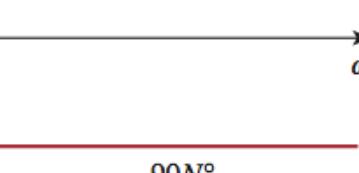
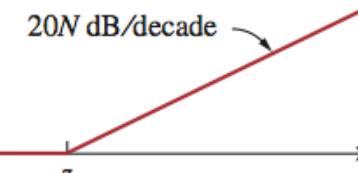
Factor	Magnitude	Phase
K	$20 \log_{10} K$ 	
$(j\omega)^N$	$20N$ dB/decade 	$90N^\circ$ 
$\frac{1}{(j\omega)^N}$	$-20N$ dB/decade 	$-90N^\circ$ 
$\left(1 + \frac{j\omega}{z}\right)^N$	$20N$ dB/decade 	0° at $\omega = \frac{z}{10}$, then increasing to $90N^\circ$ at $\omega = 10z$ 

Zeros: upward turn
Poles: downward turn



$$\frac{1}{(1 + j\omega/p)^N}$$

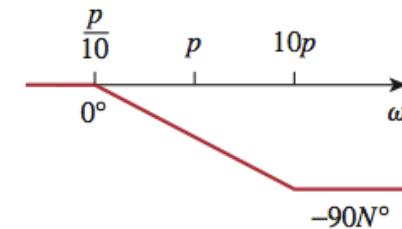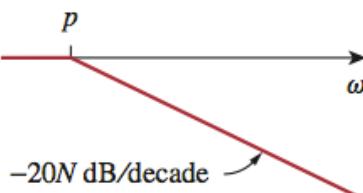
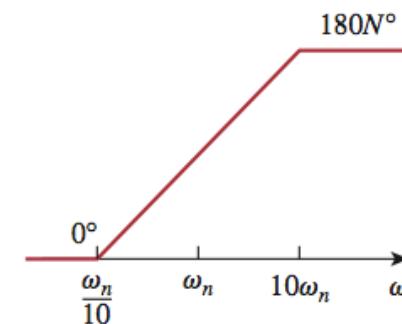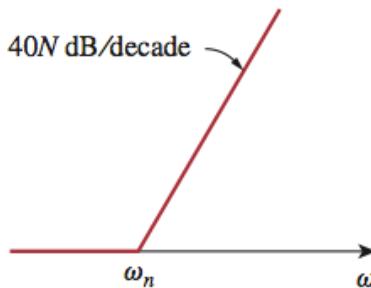
$$\left[1 + \frac{2j\omega\xi}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2 \right]^N$$



$$\frac{1}{[1 + 2j\omega\xi/\omega_k + (j\omega/\omega_k)^2]^N}$$

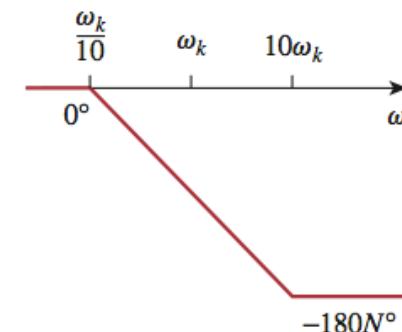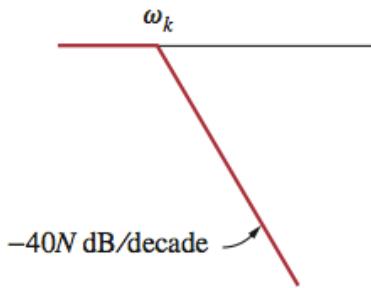

Example 14.4 Obtain the Bode plots for

$$H(j\omega) = \frac{j\omega + 10}{j\omega(j\omega + 5)^2} \rightarrow \frac{10 \left(1 + \frac{j\omega}{10}\right)}{25 j\omega \left(1 + \frac{j\omega}{5}\right)^2} = 0.4 \frac{\left(1 + \frac{j\omega}{10}\right)}{j\omega \left(1 + \frac{j\omega}{5}\right)^2}$$

Change the form

$$H(\omega) = \frac{K(j\omega)^{\pm 1} (1 + j\omega/z_1)[1 + j2\zeta_1\omega/\omega_k + (j\omega/\omega_k)^2] \cdots}{(1 + j\omega/p_1)[1 + j2\zeta_2\omega/\omega_n + (j\omega/\omega_n)^2] \cdots}$$

Magnitude


$$H(j\omega) = \frac{0.4(1 + j\omega/10)}{j\omega(1 + j\omega/5)^2}$$

$$H_{dB} = 20 \log_{10} \left| \frac{0.4(1 + j\omega/10)}{j\omega(1 + j\omega/5)^2} \right|$$

Four terms:

- (i) 0.4
- (ii) $(1+j\omega/10)$
- (iii) $(j\omega)^{-1}$
- (iv) $(1+j\omega/5)^{-2}$

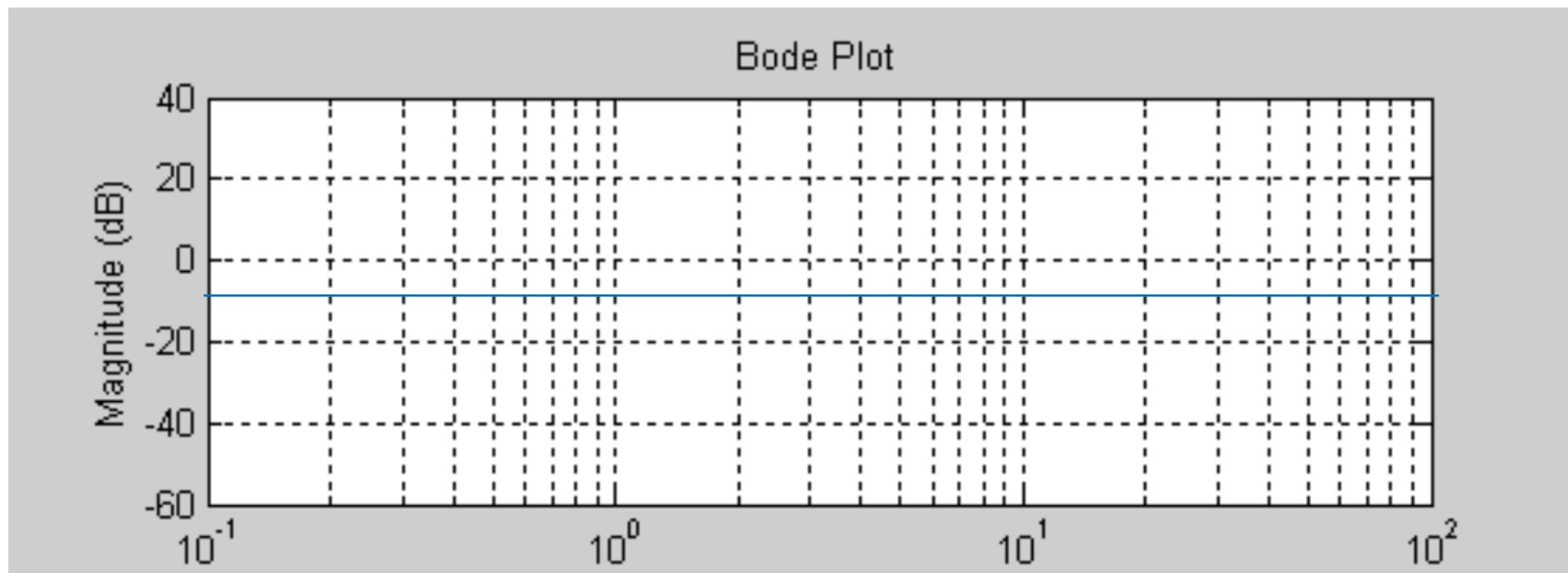(i) $0.4 \rightarrow 20 \log 0.4 = -8 \text{ dB}$




$$H(j\omega) = \frac{0.4(1+j\omega/10)}{j\omega(1+j\omega/5)^2}$$

$$H_{dB} = 20 \log_{10} \left| \frac{0.4(1+j\omega/10)}{j\omega(1+j\omega/5)^2} \right|$$

- (i) $\omega = 1, H_{dB} = 0 \text{ dB}$
- (ii) $\omega = 10, H_{dB} = 3 \text{ dB} = 0$
- (iii) $\omega = 100, H_{dB} = 20 \text{ dB}$

(ii) $(1+j\omega/10) \rightarrow 20 \log |1+j\omega/10|$

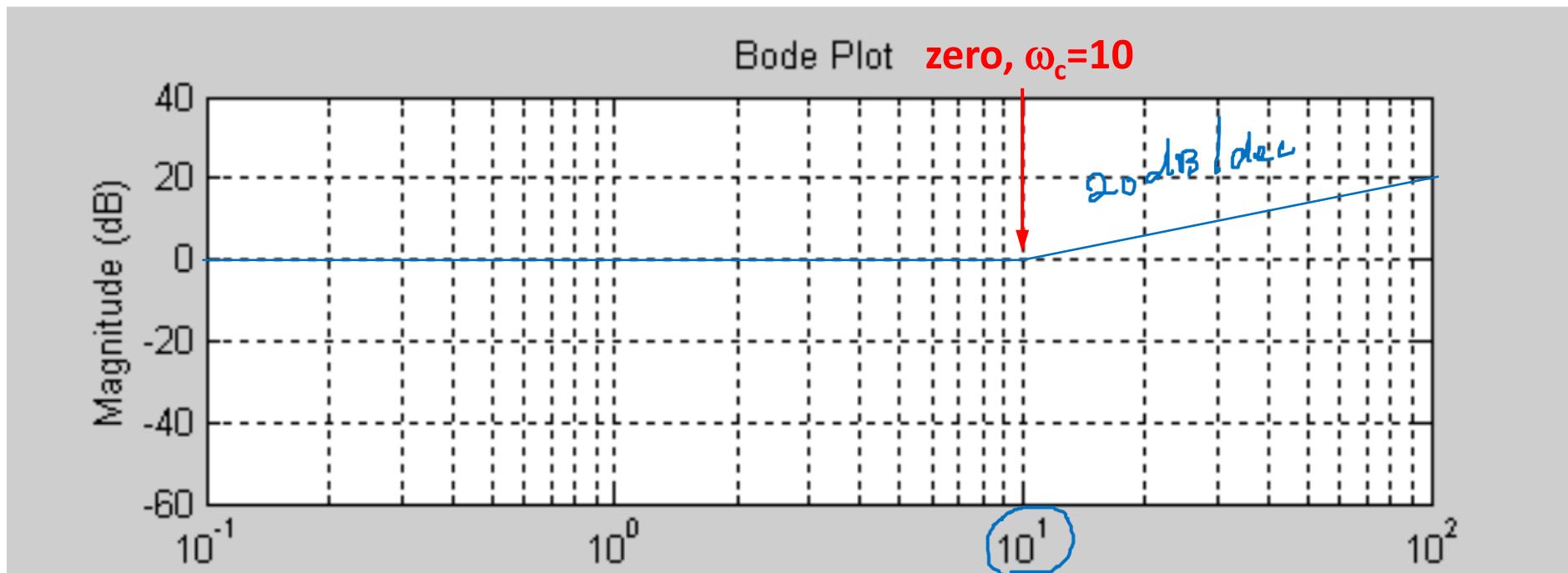

$$H(j\omega) = \frac{0.4(1+j\omega/10)}{j\omega(1+j\omega/5)^2}$$


$$H_{dB} = 20 \log_{10} \left| \frac{0.4(1+j\omega/10)}{j\omega(1+j\omega/5)^2} \right|$$

(iii) $(j\omega)^{-1} \rightarrow -20 \log |j\omega|$

(i) $\omega = 0.1, H_{dB} = 20 \text{ dB}$

(ii) $\omega = 10, H_{dB} = -20 \text{ dB}$

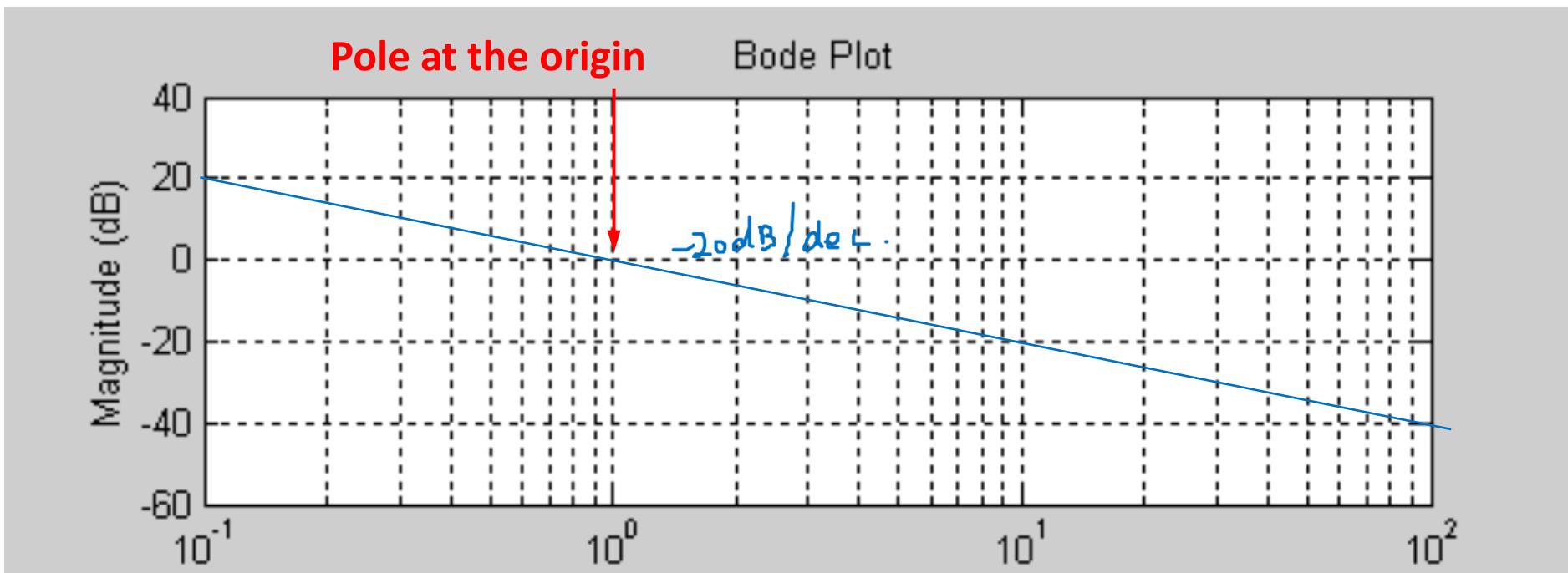(iii) $\omega = 100, H_{dB} = -40 \text{ dB}$




$$H(j\omega) = \frac{0.4(1+j\omega/10)}{j\omega(1+j\omega/5)^2}$$

$$H_{dB} = 20 \log_{10} \left| \frac{0.4(1+j\omega/10)}{j\omega(1+j\omega/5)^2} \right|$$

$-20 \log(1+\omega/5)$

(iv) $(1+j\omega/5)^{-2} \rightarrow -40 \log |1+j\omega/5|$

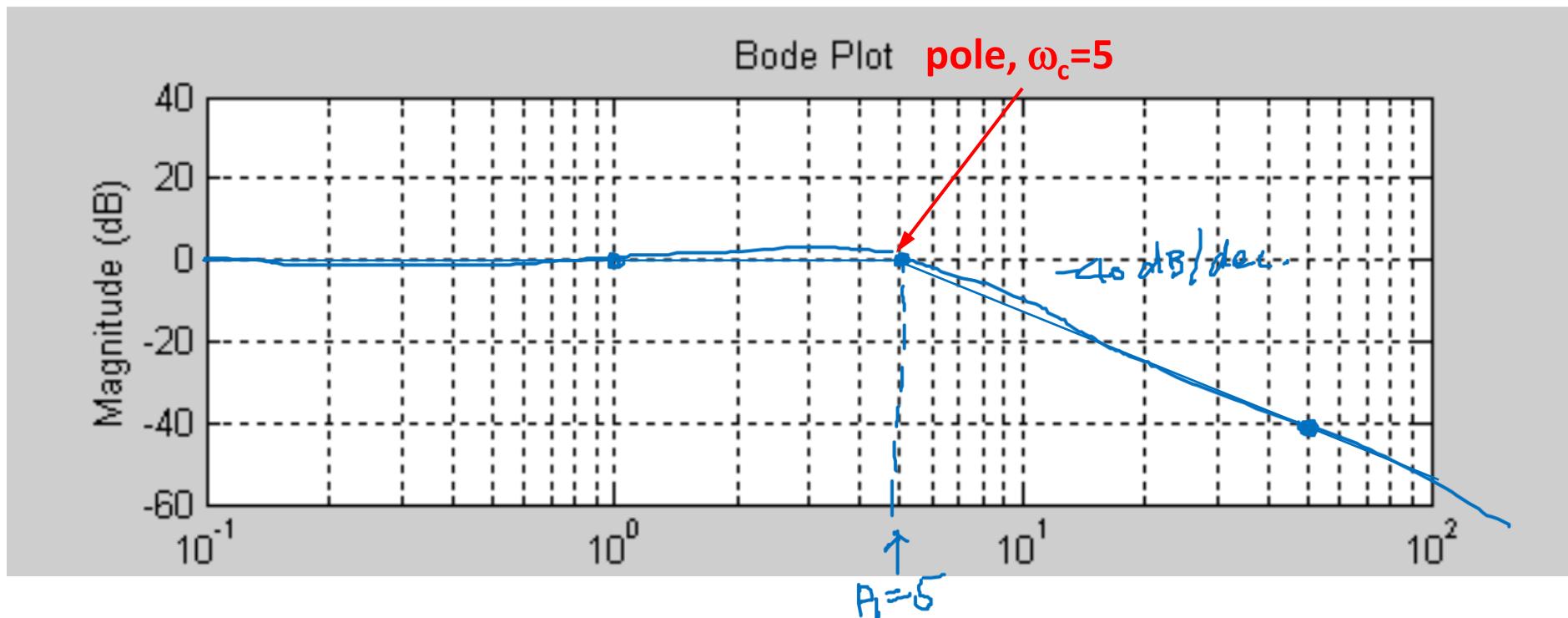- (i) $\omega = 0.5, H_{dB} = 0 \text{ dB}$
- (ii) $\omega = 5, H_{dB} = -6 \text{ dB} = 0 \text{ dB}$
- (iii) $\omega = 50, H_{dB} = -40 \text{ dB}$




$$H(j\omega) = \frac{0.4(1+j\omega/10)}{j\omega(1+j\omega/5)^2}$$

$$H_{dB} = 20 \log_{10} \left| \frac{0.4(1+j\omega/10)}{j\omega(1+j\omega/5)^2} \right|$$

Draw all of the four terms

$$= 20 \log_{10} 0.4 + 20 \log_{10} |1+j\omega/10| - 20 \log_{10} |j\omega| - 40 \log_{10} |1+j\omega/5|$$

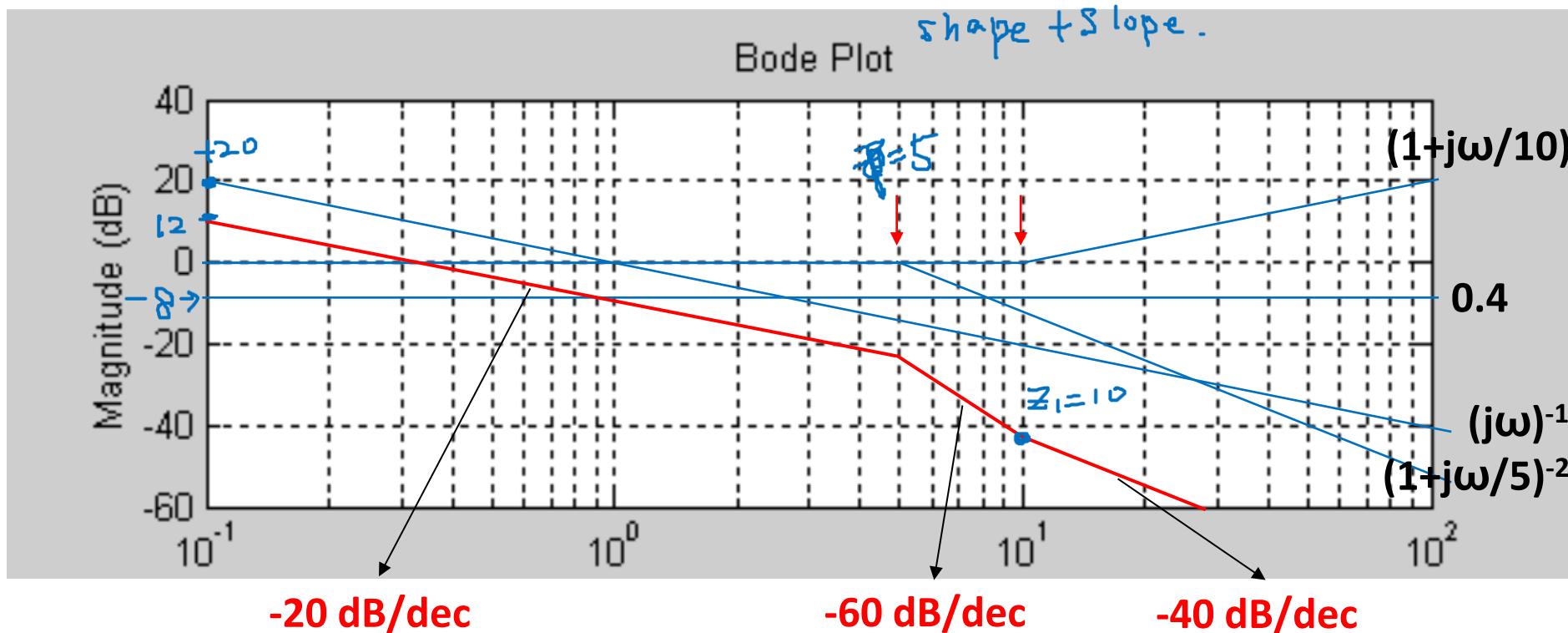

Phase

$$H(j\omega) = \frac{0.4(1+j\omega/10)}{j\omega(1+j\omega/5)^2}$$

Four terms:

- (i) $0.4 \rightarrow 0^\circ$
- (ii) $(1+j\omega/10)$
- (iii) $(j\omega)^{-1}$
- (iv) $(1+j\omega/5)^{-2}$


$$(ii) (1+j\omega/10) \rightarrow \angle \tan^{-1}(\omega/10)$$

$$(i) \quad \omega = 1, \Phi = 5.7 = 0^\circ$$

$$(ii) \quad \omega = 10, \Phi = 45^\circ$$

$$(iii) \quad \omega = 100, \Phi = 84 = 90^\circ$$

zero, $\omega_c=10$

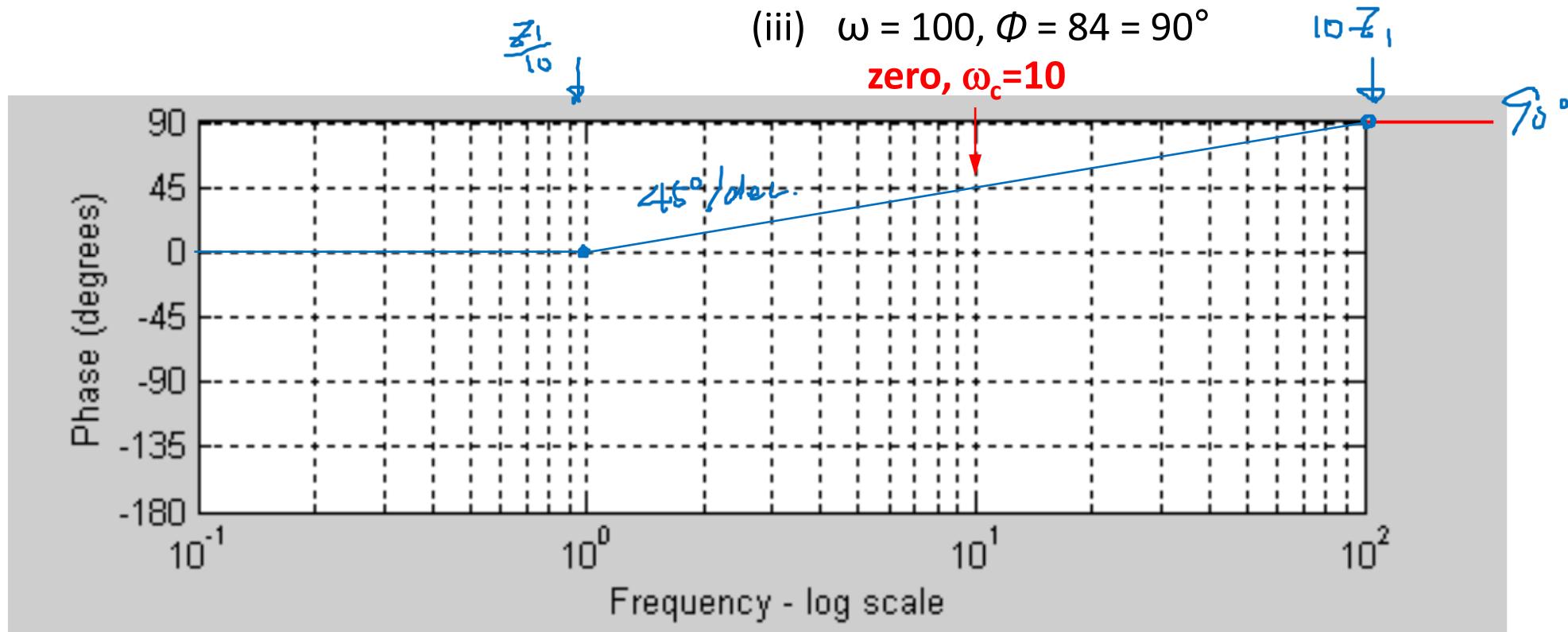

Phase


$$H(j\omega) = \frac{0.4(1 + j\omega/10)}{j\omega(1 + j\omega/5)^2}$$

Four terms:

- (i) $0.4 \rightarrow 0^\circ$
- (ii) $(1+j\omega/10)$
- (iii) $(j\omega)^{-1}$
- (iv) $(1+j\omega/5)^{-2}$

(iii) $(j\omega)^{-1} \rightarrow -90^\circ \Rightarrow -j\omega \Rightarrow -j$

Pole at the origin

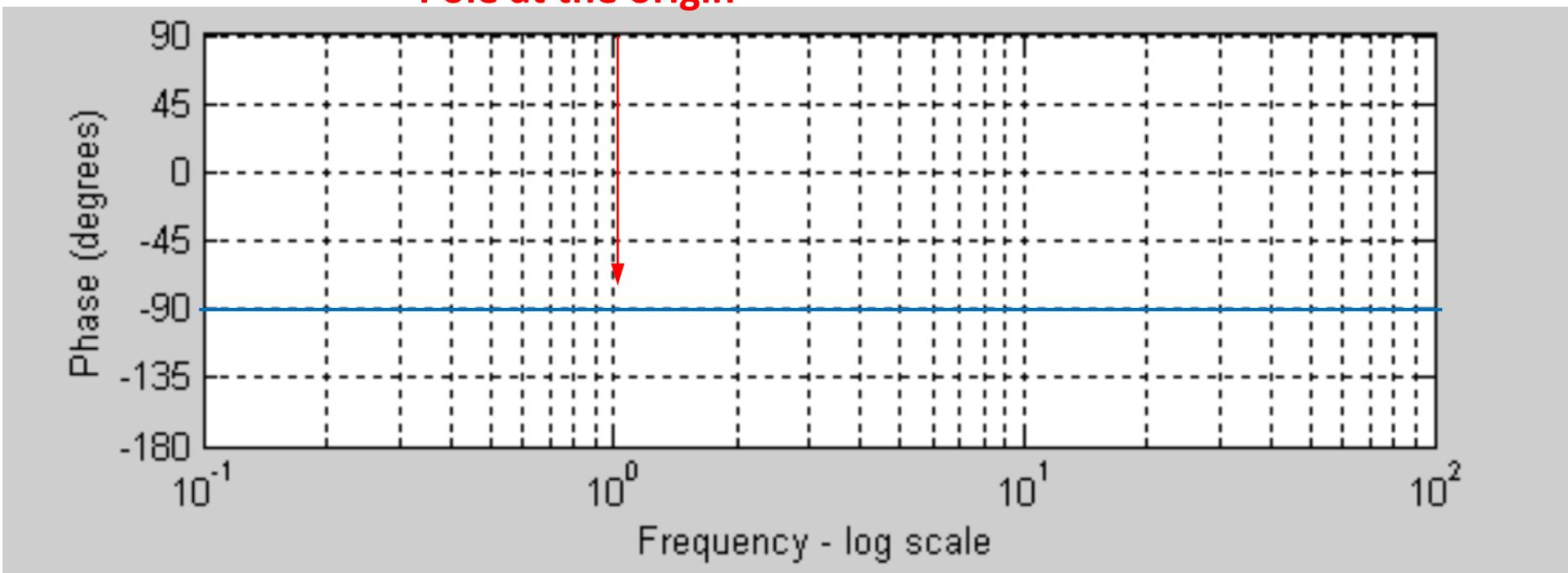

Phase

$$H(j\omega) = \frac{0.4(1+j\omega/10)}{j\omega(1+j\omega/5)^2}$$

Four terms:

- (i) $0.4 \rightarrow 0^\circ$
- (ii) $(1+j\omega/10)$
- (iii) $(j\omega)^{-1}$
- (iv) $(1+j\omega/5)^{-2}$

$$(iv) (1+j\omega/5)^{-2} \rightarrow -2 * \angle \tan^{-1}(\omega/5)$$


$$\text{H}_d(j\omega) \rightarrow -45^\circ/\text{dec.} \times 2.$$

$$(i) \quad \omega = 0.5, \Phi = -2 * 5.7 = -11.42 = 0^\circ$$

$$(ii) \quad \omega = 5, \Phi = -90^\circ$$

$$(iii) \quad \omega = 50, \Phi = -2 * 84 = -168 = -180^\circ$$

pole, $\omega_c=5$

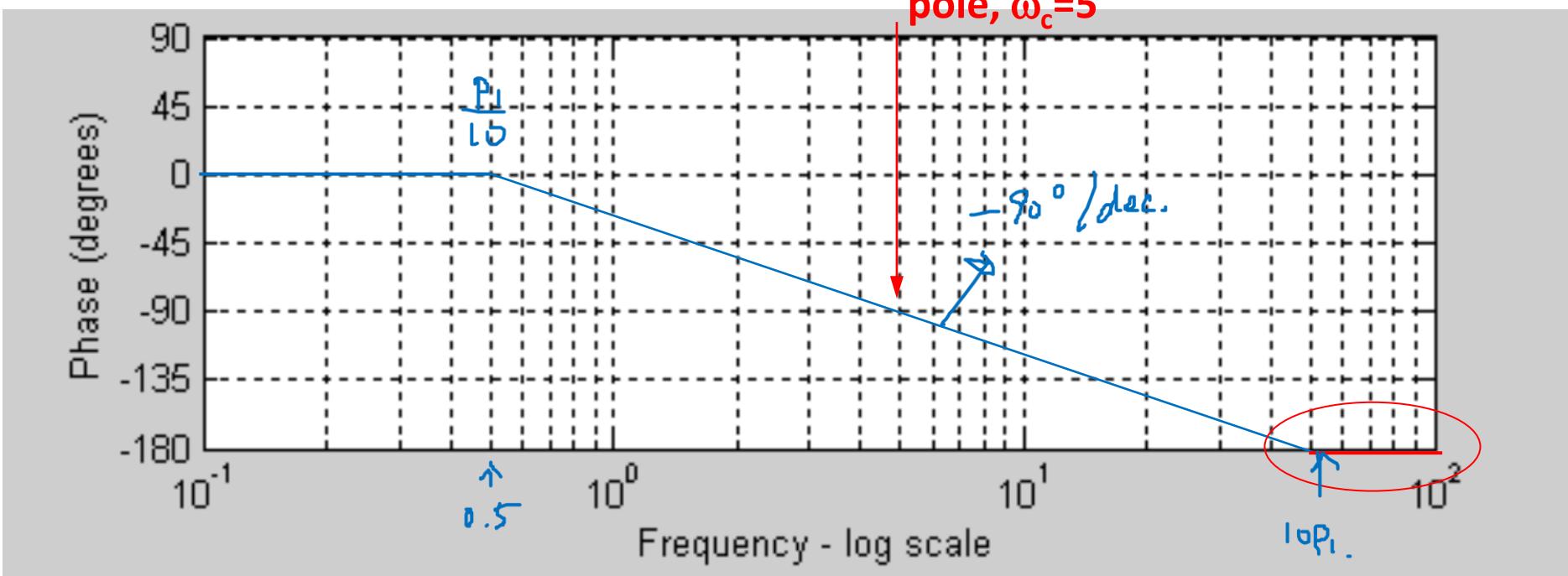

Phase


$$H(j\omega) = \frac{0.4(1 + j\omega/10)}{j\omega(1 + j\omega/5)^2}$$

Four terms:

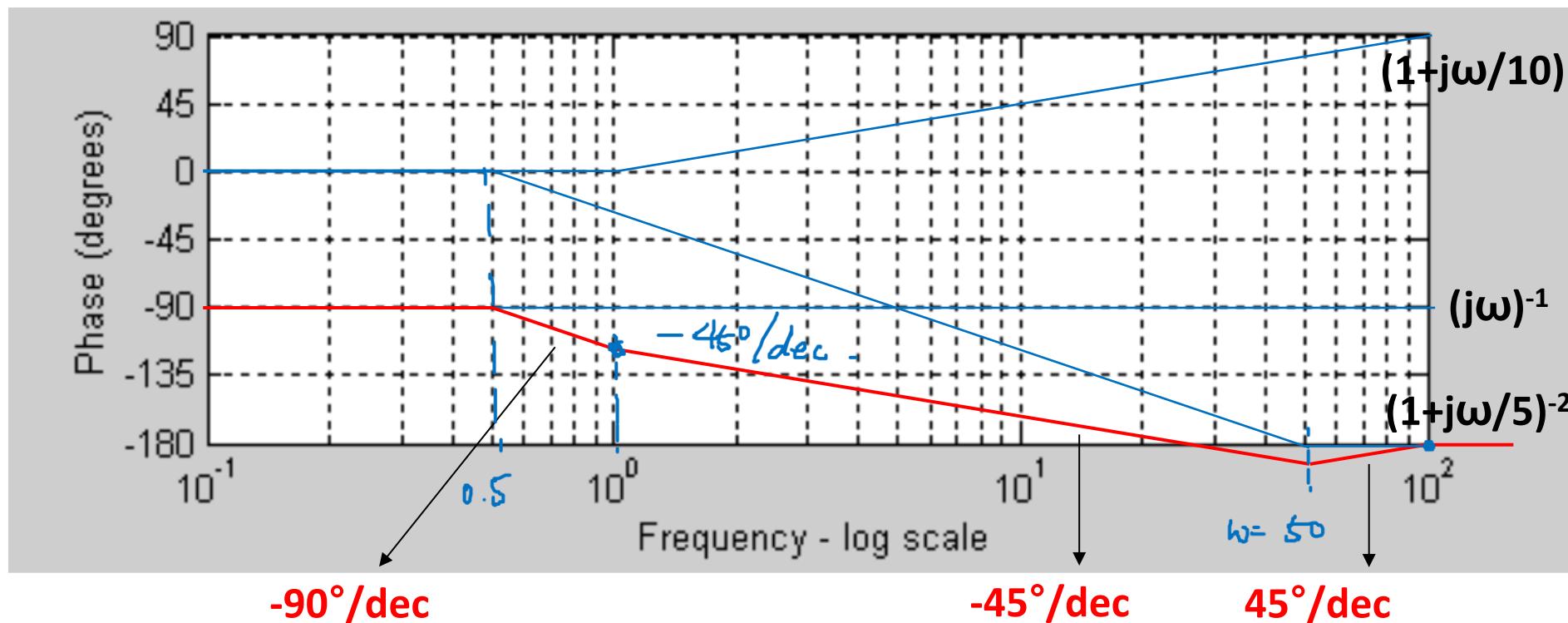
- (i) $0.4 \rightarrow 0^\circ$
- (ii) $(1+j\omega/10)$
- (iii) $(j\omega)^{-1}$
- (iv) $(1+j\omega/5)^{-2}$

Draw all of the four terms

$$\phi = 0^\circ + \tan^{-1}(\omega/10) - 90^\circ - 2 \tan^{-1}(\omega/5)$$



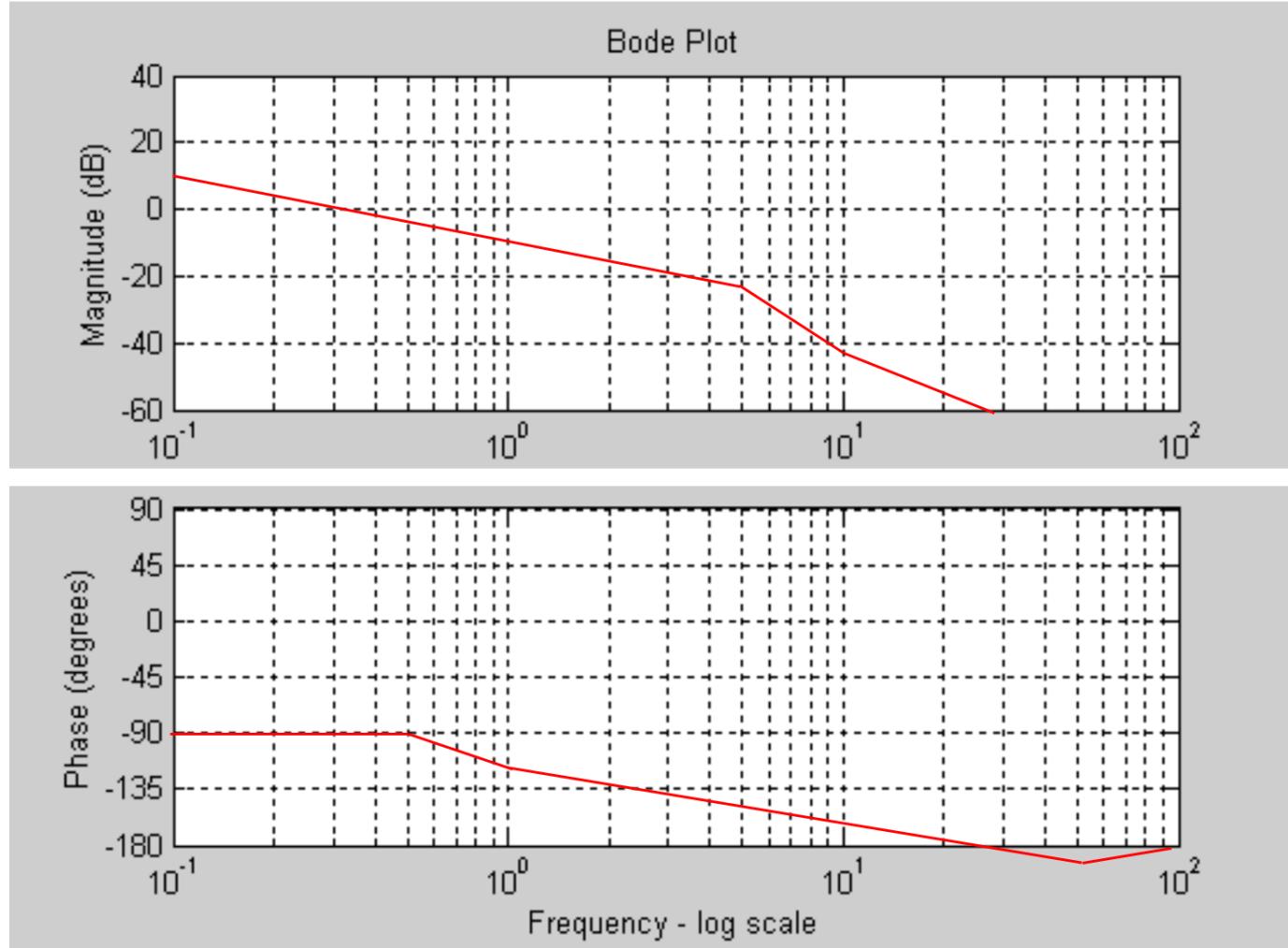Bode plot of the transfer function: $H(j\omega) = \frac{j\omega + 10}{j\omega(j\omega + 5)^2}$



Practice Problem 14.3 Draw the Bode plots for


$$H(j\omega) = \frac{5(j\omega + 2)}{j\omega(j\omega + 10)}$$

$$H_{dB} = 20 \log_{10} \left| \frac{(1 + j\omega/2)}{j\omega(1 + j\omega/10)} \right| = 20 \log_{10} |1 + j\omega/2| - 20 \log_{10} |j\omega| - 20 \log_{10} |1 + j\omega/10|$$

$20 \log_{10} |1 + j\omega/2|$ **Green line**


$-20 \log_{10} |j\omega|$ **Blue line**

$-20 \log_{10} |1 + j\omega/10|$ **Yellow line**

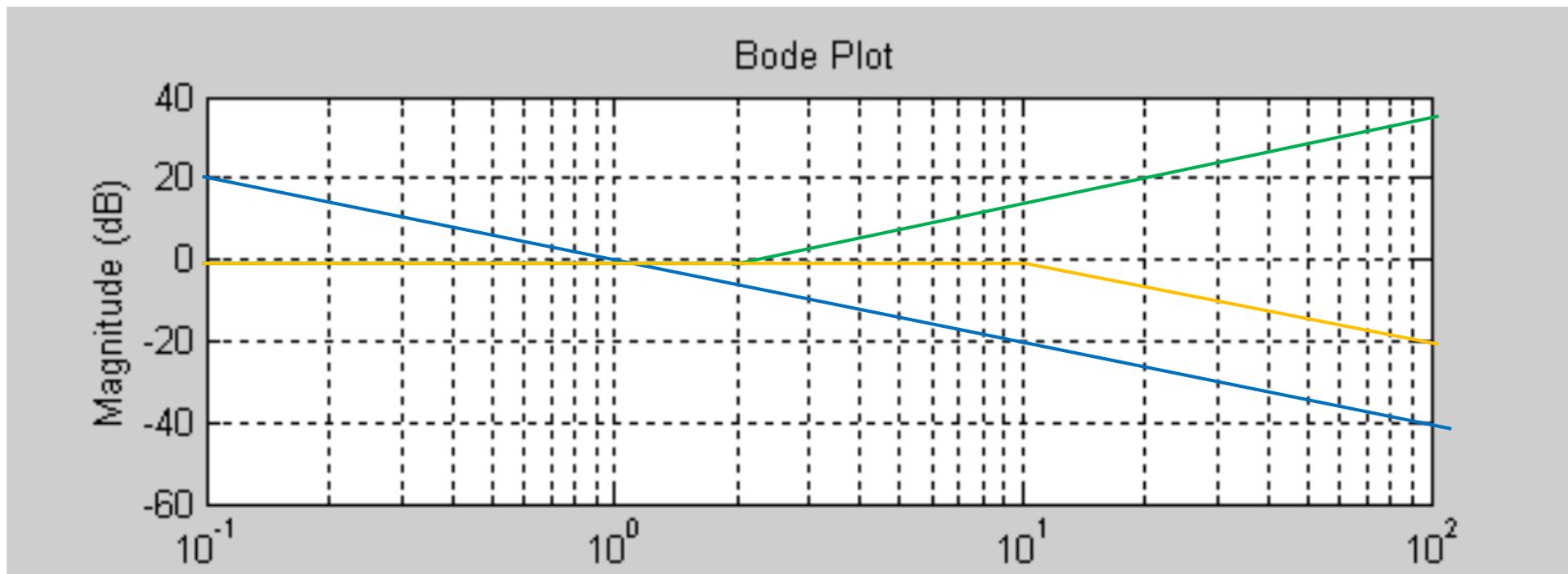

$$H_{dB} = 20 \log_{10} \left| \frac{(1+j\omega/2)}{j\omega(1+j\omega/10)} \right| = 20 \log_{10} |1+j\omega/2| - 20 \log_{10} |j\omega| - 20 \log_{10} |1+j\omega/10|$$

Combined in red line

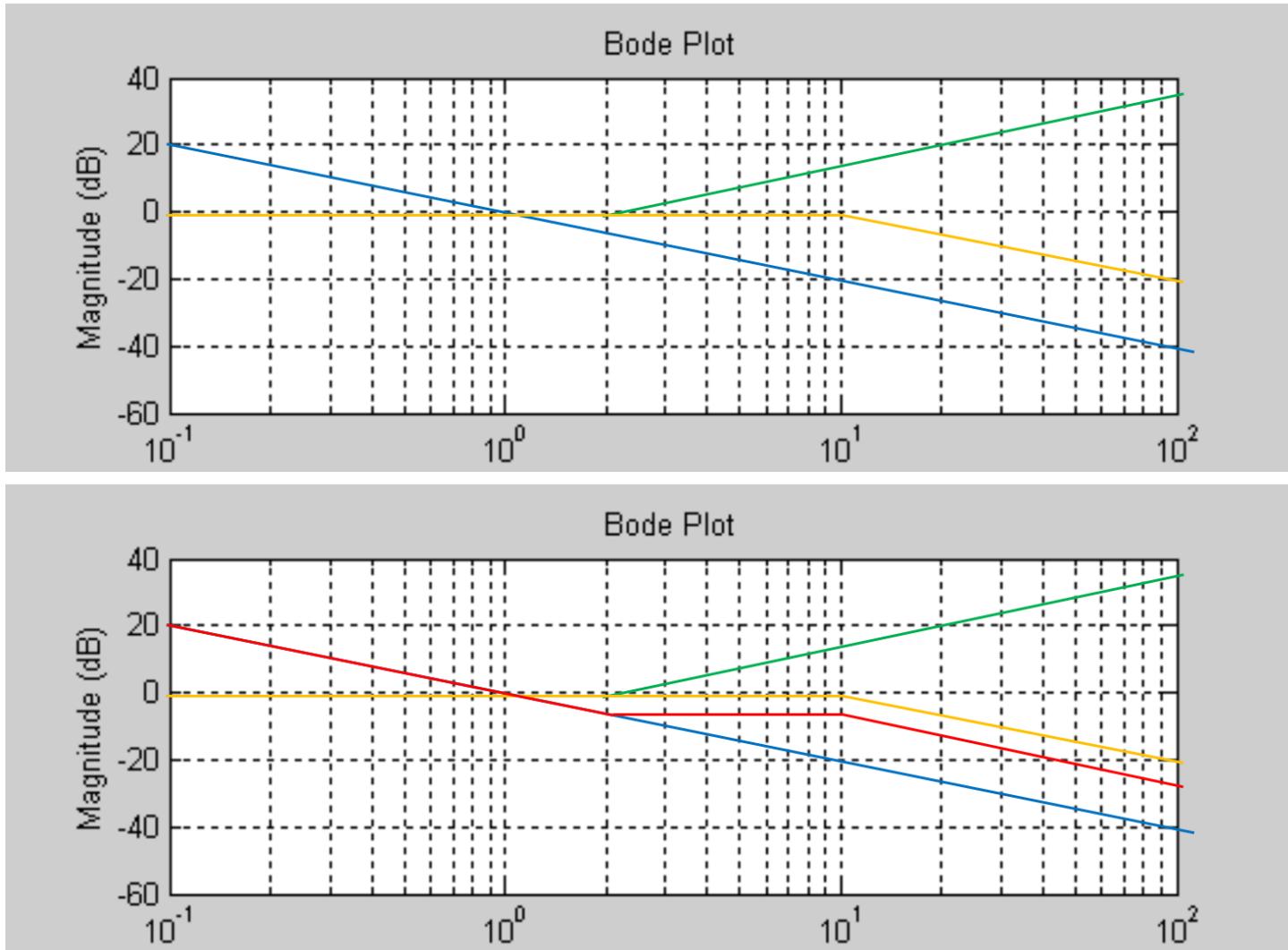


$$H(j\omega) = \frac{(1 + j\omega/2)}{j\omega(1 + j\omega/10)}$$

$$\phi = \tan^{-1}(\omega/2) - 90^\circ - \tan^{-1}(\omega/10)$$



Green line

Blue line

Yellow line

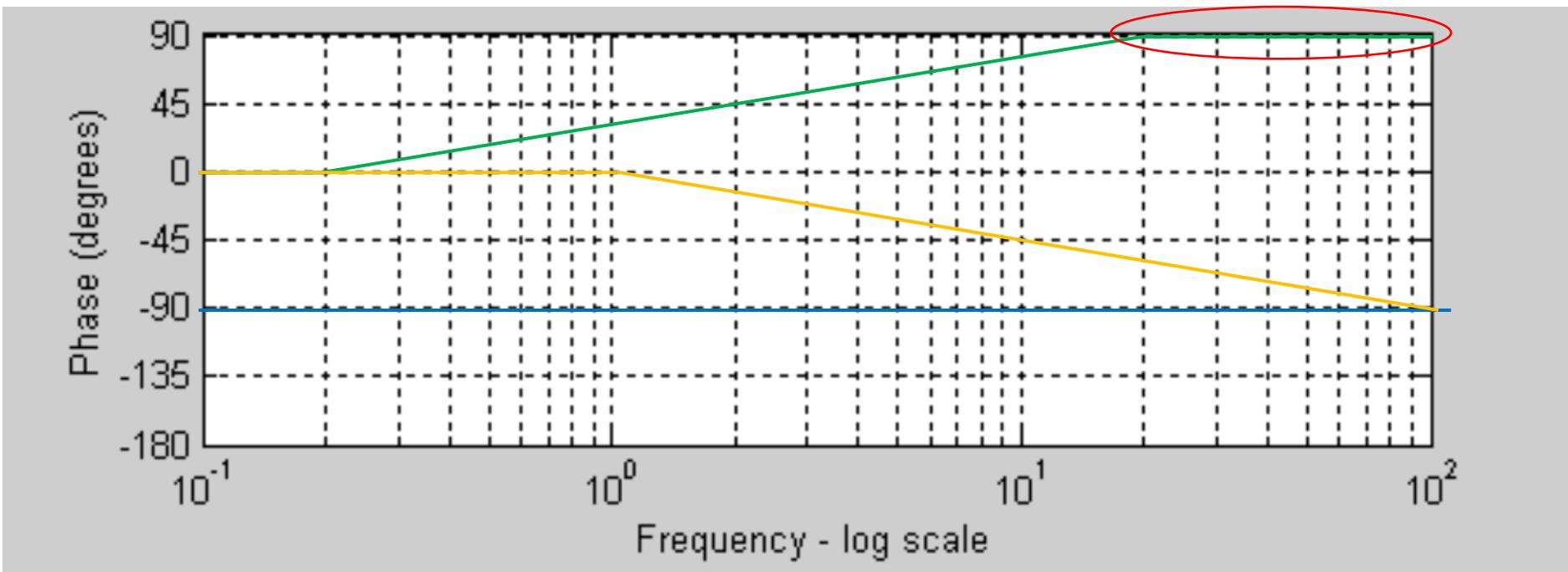
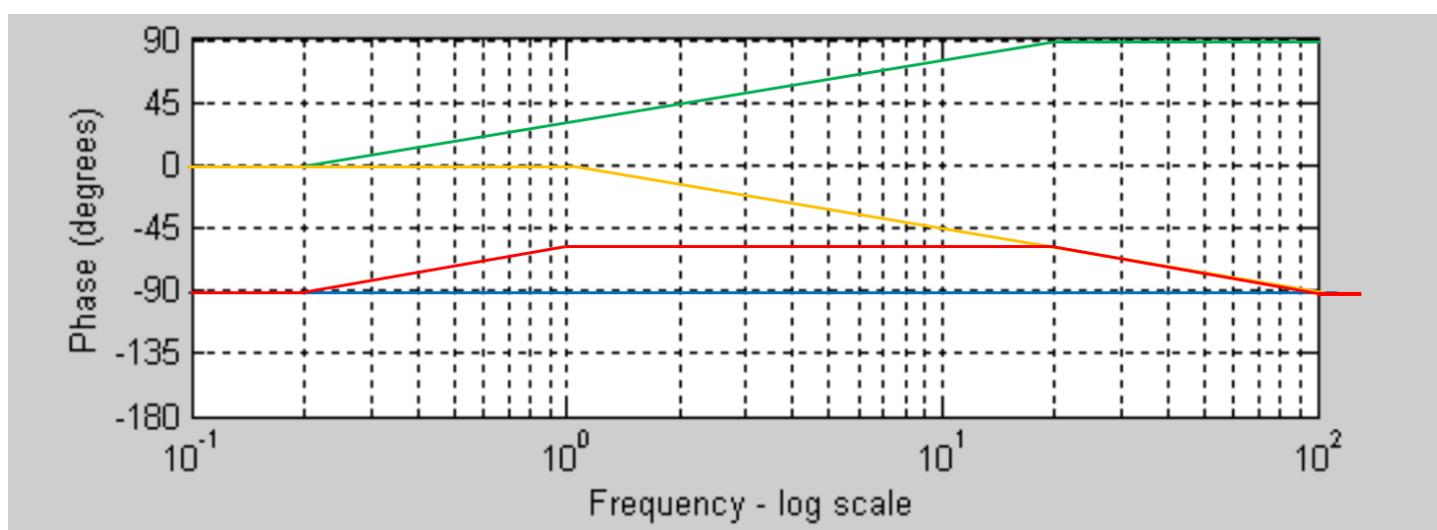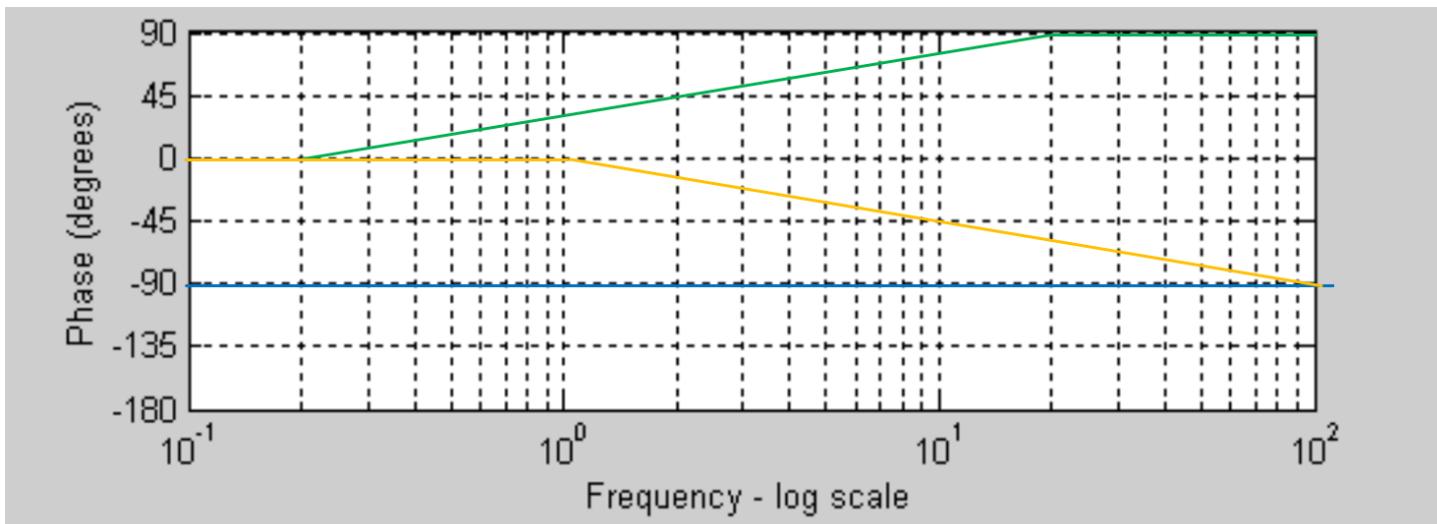
$$\phi = \tan^{-1}(\omega/2) - 90^\circ - \tan^{-1}(\omega/10) \quad \text{Combined in red line}$$



$$H(j\omega) = \frac{(1 + j\omega/2)}{j\omega(1 + j\omega/10)}$$

$$H_{dB} = 20 \log_{10} \left| \frac{(1 + j\omega/2)}{j\omega(1 + j\omega/10)} \right|$$

Pole at the origin
Simple pole



$$= 20 \log_{10} |1 + j\omega/2| + 20 \log_{10} \frac{1}{|j\omega|}$$

$$+ 20 \log_{10} \frac{1}{|1 + j\omega/10|}$$

$$= 20 \log_{10} |1 + j\omega/2| - 20 \log_{10} |j\omega|$$

$$- 20 \log_{10} |1 + j\omega/10|$$

$$\phi = \tan^{-1}(\omega/2) - 90^\circ - \tan^{-1}(\omega/10)$$

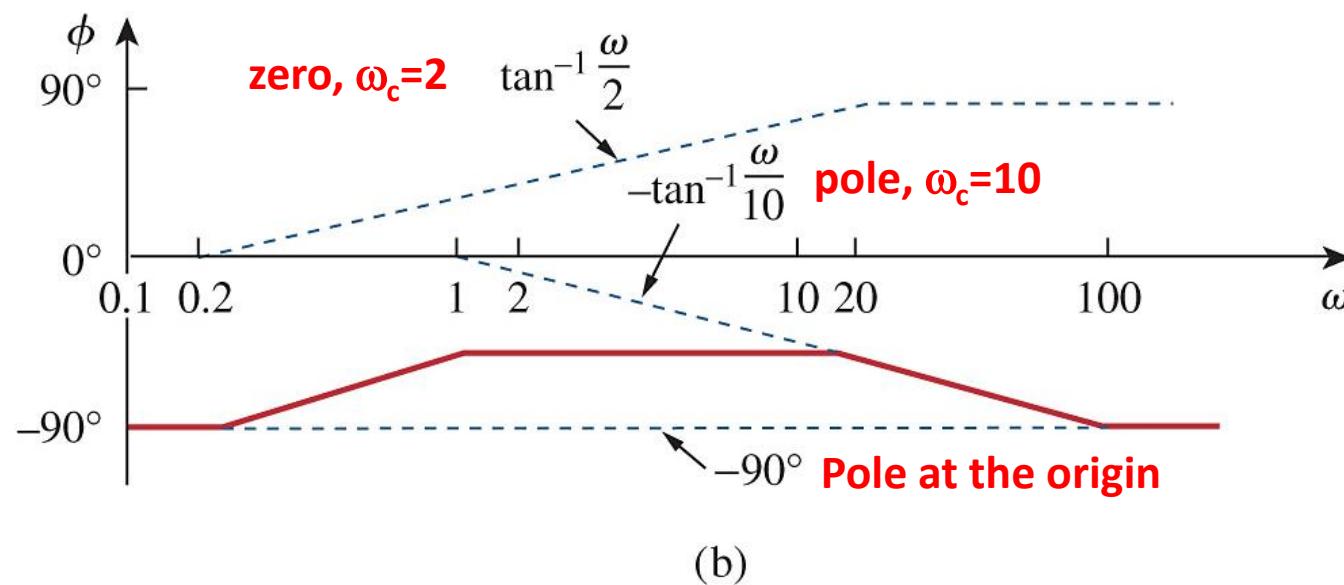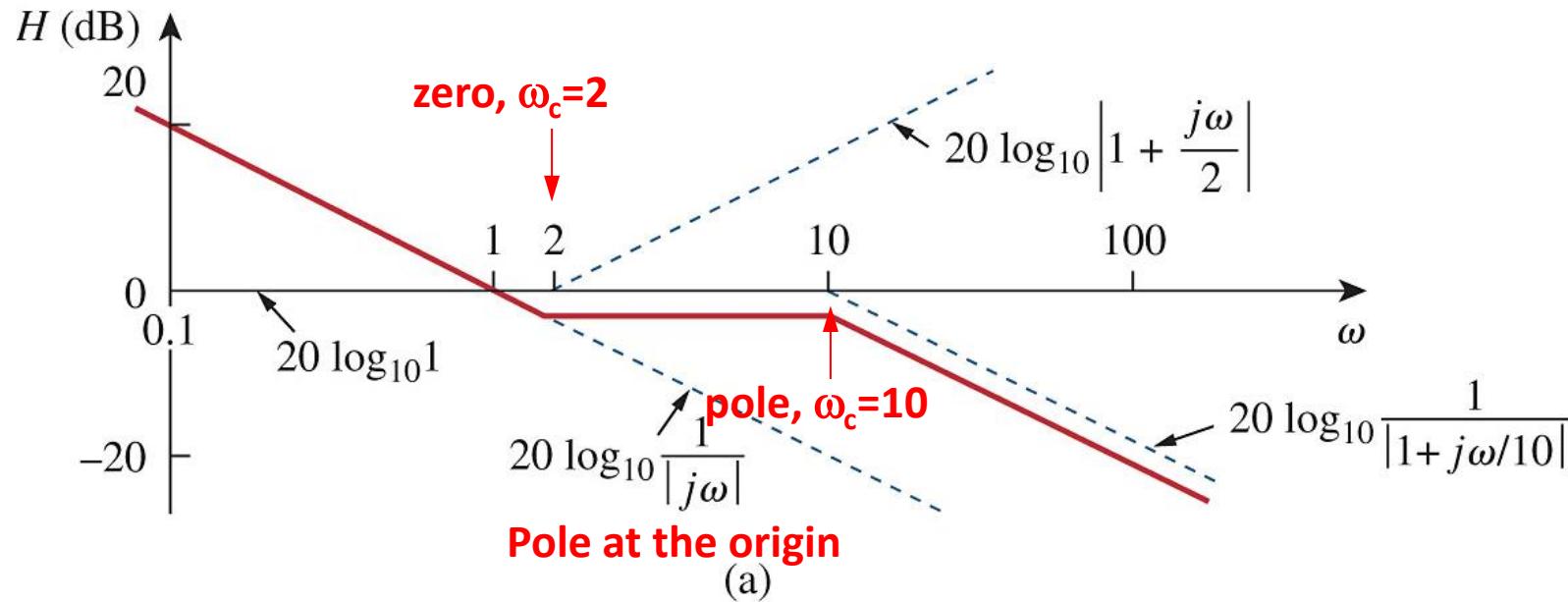

Example 14.5 Draw the Bode plots for

$$H(j\omega) = \frac{j\omega + 1}{(j\omega)^2 + 12(j\omega) + 100} \Rightarrow$$

$$100 \left(1 + \frac{1^2}{100} j\omega + \left(\frac{j\omega}{10}\right)^2 \right)$$

$$H(j\omega) = \frac{1}{100} \frac{(1+j\omega)}{\left[1 + 2 \times 0.6 \left(\frac{j\omega}{10}\right) + \left(\frac{j\omega}{10}\right)^2 \right]}$$

$$100 \left(1 + 2 \times 0.6 \left(\frac{j\omega}{10}\right) + \left(\frac{j\omega}{10}\right)^2 \right)$$

Example 14.5 Draw the Bode plots for

$$H(j\omega) = \frac{j\omega + 1}{(j\omega)^2 + 12(j\omega) + 100}$$

$$\begin{aligned} H(j\omega) &= \frac{0.01(1 + j\omega/1)}{1 + 0.12(j\omega) + (j\omega/10)^2} \\ &= \frac{0.01(1 + j\omega/1)}{1 + 2 \times 0.6(j\omega/10) + (j\omega/10)^2} \end{aligned}$$

$$\begin{aligned} H_{dB} &= 20 \log_{10} \left| \frac{0.01(1 + j\omega/1)}{1 + 2 \times 0.6(j\omega/10) + (j\omega/10)^2} \right| \\ &= 20 \log_{10} 0.01 + 20 \log_{10} |1 + j\omega/1| \\ &\quad - 20 \log_{10} |1 + 2 \times 0.6(j\omega/10) + (j\omega/10)^2| \end{aligned}$$

$$\phi = 0^\circ + \tan^{-1}(\omega/1) - \tan^{-1} \left[\frac{2 \times 0.6(\omega/10)}{1 - (\omega/10)^2} \right]$$


$$H_{dB} = 20 \log_{10} \left| \frac{0.01(1+j\omega/1)}{1+2\times 0.6(j\omega/10)+(j\omega/10)^2} \right|$$

$$= 20 \log_{10} 0.01 \quad \text{-40 dB Green line}$$

$$+ 20 \log_{10} |1 + j\omega/1| \quad \text{Blue line}$$


$$-20 \log_{10} |1 + 2 \times 0.6(j\omega/10) + (j\omega/10)^2| \quad \text{Yellow line}$$

$\omega_K = 10$

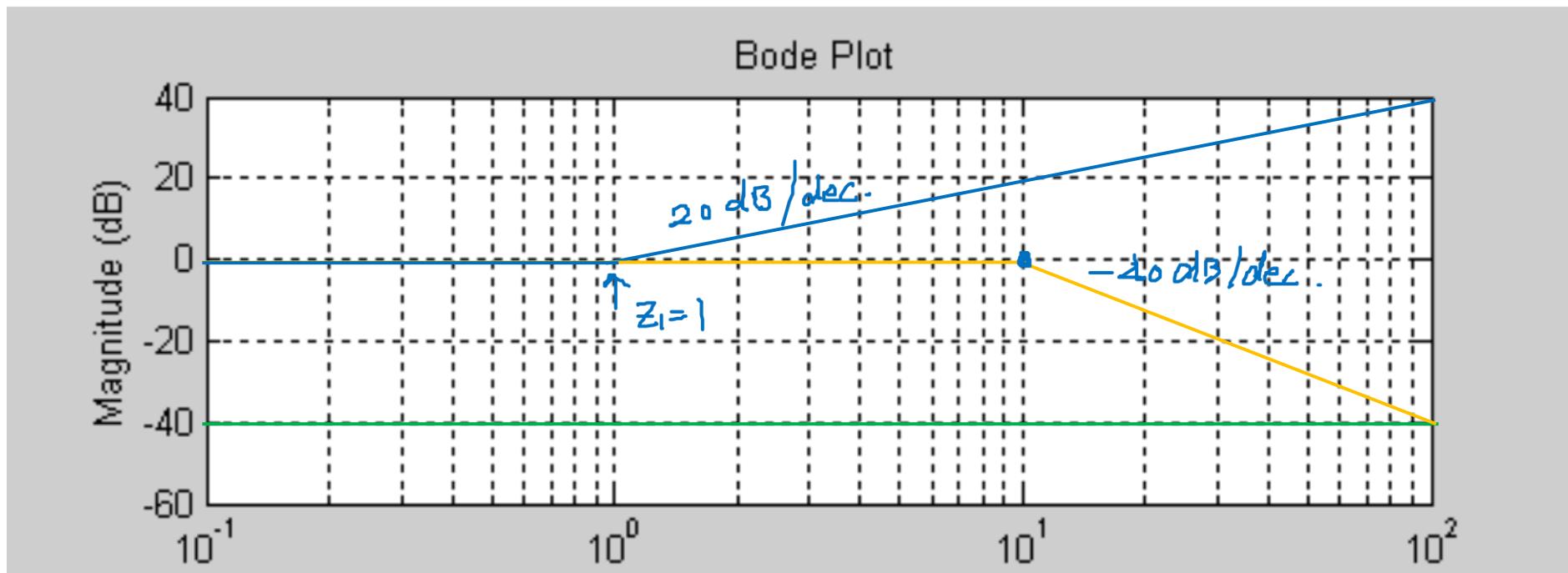

$$H_{dB} = 20 \log_{10} \left| \frac{0.01(1 + j\omega/1)}{1 + 2 \times 0.6(j\omega/10) + (j\omega/10)^2} \right|$$

Combined in red line

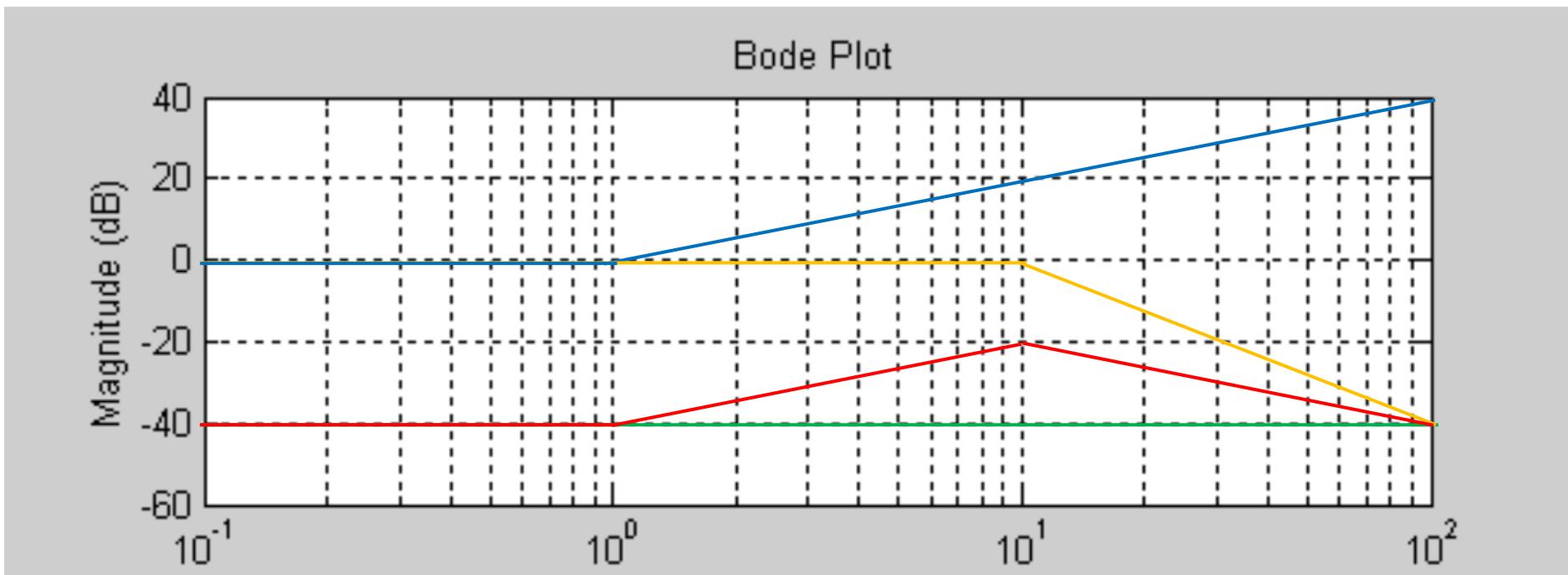


$$H(j\omega) = \frac{0.01(1+j\omega/1)}{1+0.12(j\omega)+(j\omega/10)^2}$$

$$= \frac{0.01(1+j\omega/1)}{1+2\times 0.6(j\omega/10)+(j\omega/10)^2}$$

$$\phi = 0^\circ + \tan^{-1}(\omega/1) - \tan^{-1} \left[\frac{2 \times 0.6(\omega/10)}{1 - (\omega/10)^2} \right]$$


Const. **Green line** **Blue line**


$\omega_0 = 1$ $\omega_K = 10$

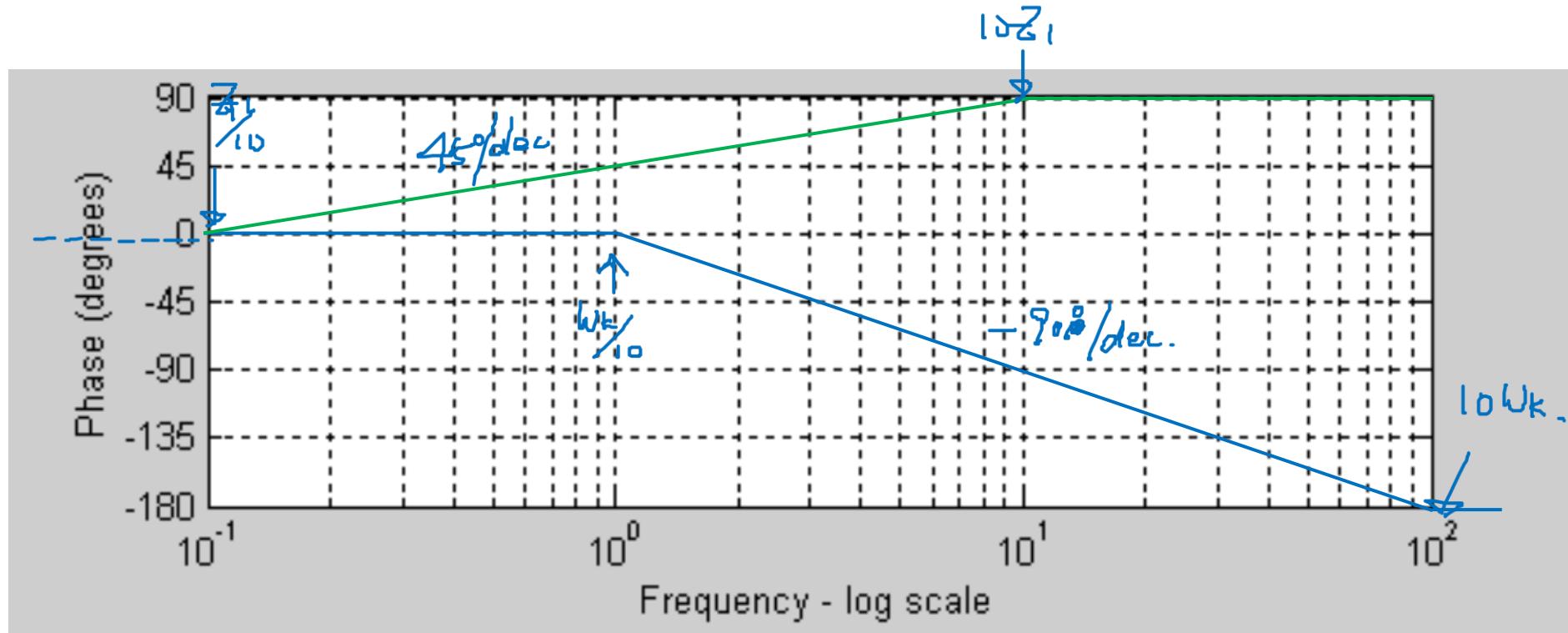

$$\phi = 0^\circ + \tan^{-1}(\omega/1) - \tan^{-1} \left[\frac{2 \times 0.6(\omega/10)}{1 - (\omega/10)^2} \right]$$

Combined in red line

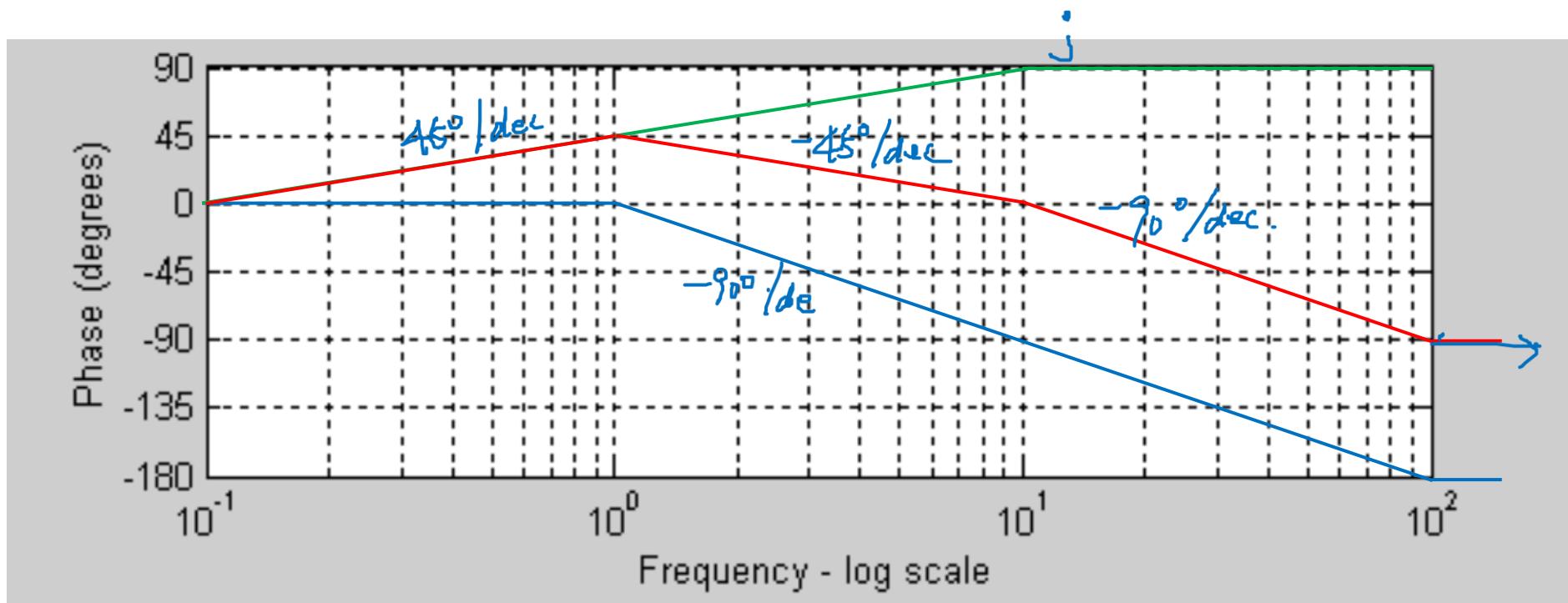

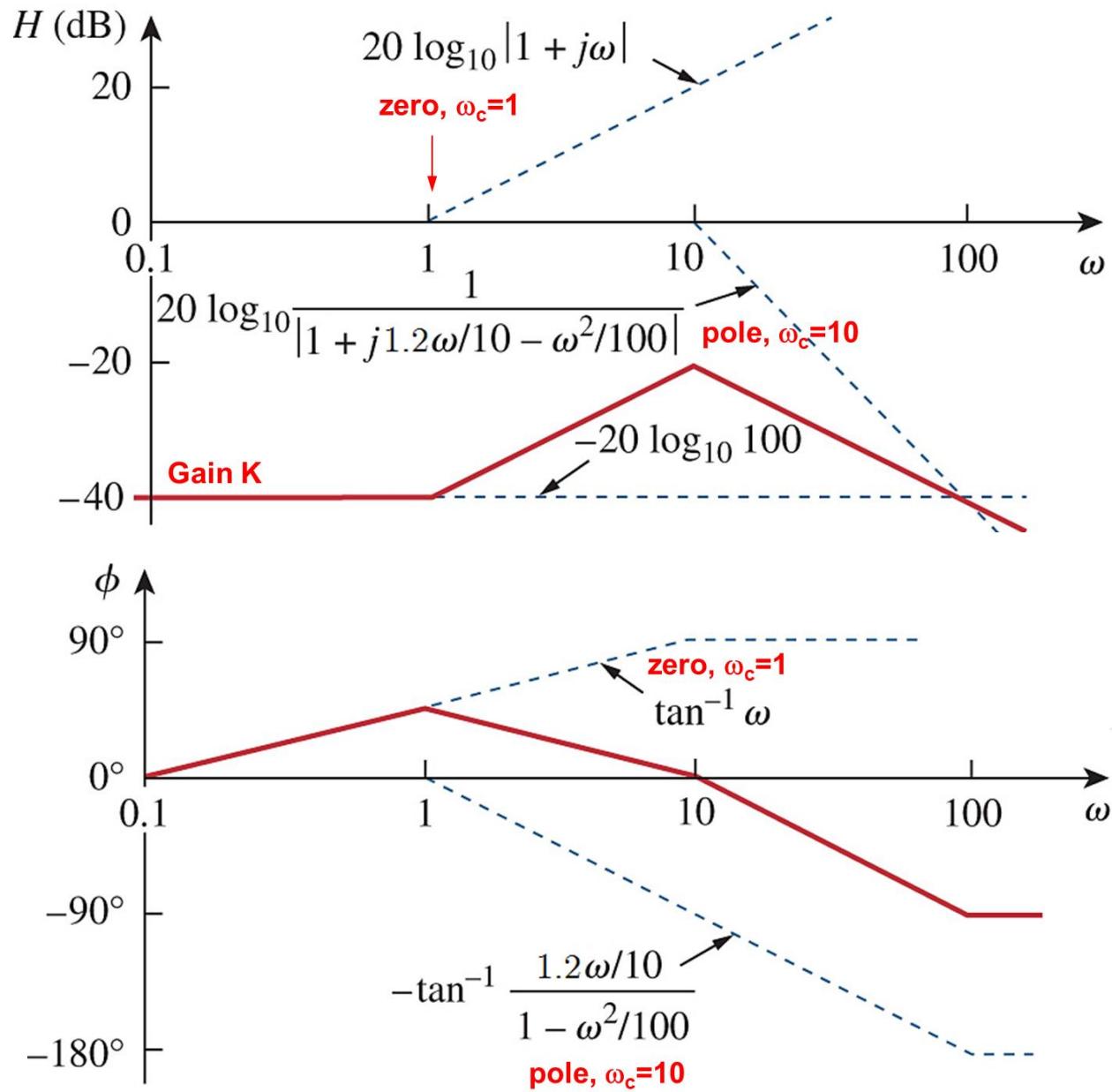


*Filters


A filter is a circuit that is designed to pass signals with desired frequencies and reject or attenuate others, i.e. a **frequency-selective device**.

Passive filter: consists of only passive elements R, L, and C

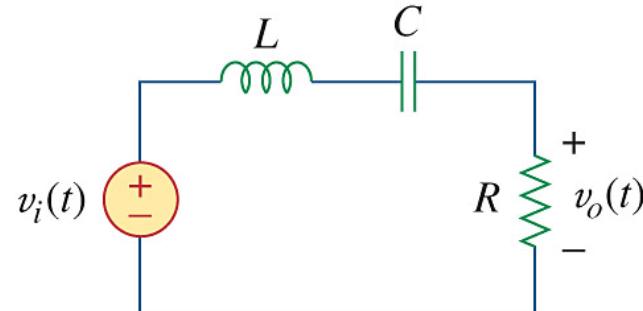
Active filter: consists of active elements, such as, transistors and op amps in addition to RLC.



Passive bandpass filter

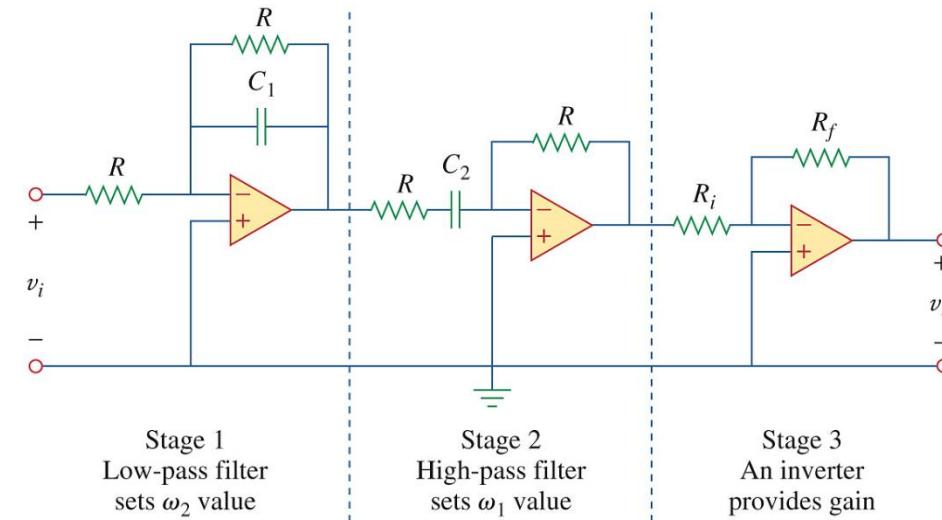


Active bandpass filter

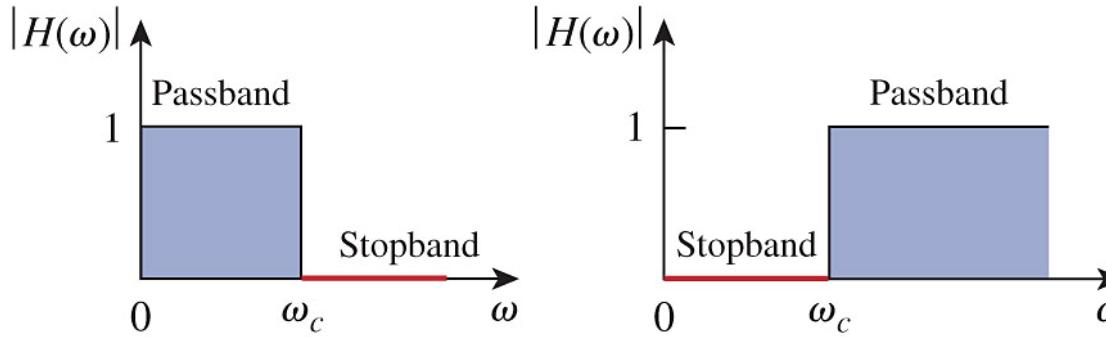

Lowpass filter passes low frequencies and stops high frequencies.

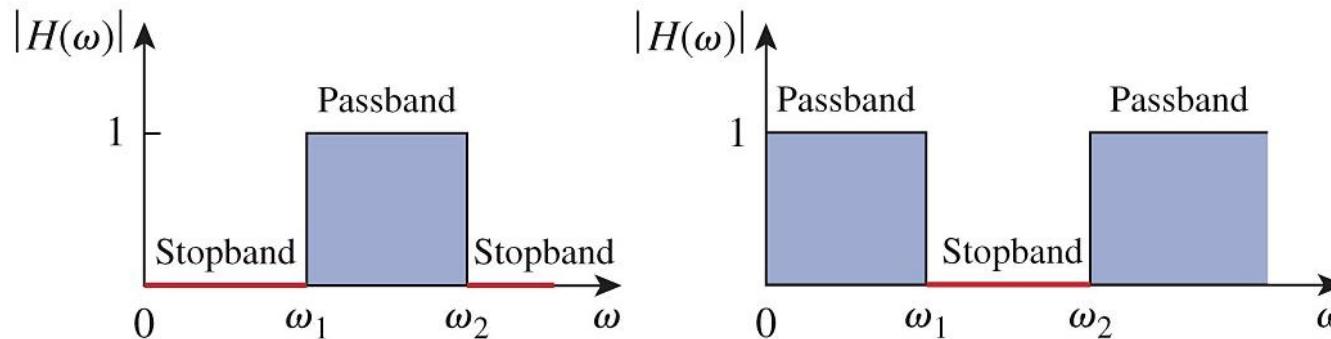Highpass filter passes high frequencies and rejects low frequencies.



Bandpass filter passes frequencies within a frequency band and blocks or attenuates frequencies outside the band.

Bandstop filter passes frequencies outside a frequency band and blocks or attenuates frequencies within the band.