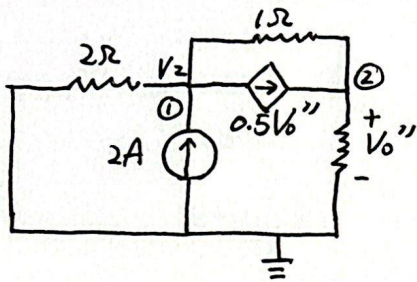


### Exercise 2.1 (15%)


First, we shut off the 10V independent Voltage Source:



$$\begin{cases} \frac{V_2}{2} + 0.5V_0'' + \frac{V_2 - V_0''}{1} = 2 & \text{node ①} \\ \frac{V_0''}{4} + \frac{V_0'' - V_2}{1} = 0.5V_0'' & \text{node ②} \end{cases}$$

$$\Rightarrow \begin{cases} -0.5V_0'' + 1.5V_2 = 2 \\ 0.75V_0'' - V_2 = 0 \end{cases} \Rightarrow \begin{cases} V_0'' = 3.2V \\ V_2 = 2.4V \end{cases}$$

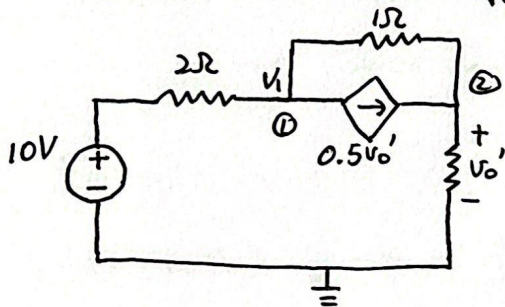Second, we shut off the 2A independent Current Source:



$$\begin{cases} \frac{V_1 - 10}{2} + 0.5V_0' + \frac{V_1 - V_0'}{1} = 0 & \text{node ①} \\ \frac{V_0'}{4} + \frac{V_0' - V_1}{1} = 0.5V_0' & \text{node ②} \end{cases}$$

$$\Rightarrow \begin{cases} -0.5V_0' + 1.5V_1 = 5 \\ 0.75V_0' - V_1 = 0 \end{cases} \Rightarrow \begin{cases} V_0' = 8V \\ V_1 = 6V \end{cases}$$

So, by superposition Thm.  $V_0 = V_0' + V_0'' = 8 + 3.2 = \boxed{11.2V}$

### Exercise 2.2 (15%)

First, we transform the independent Current Source 3A parallel with 10Ω to an independent voltage Source  $V = 3 \times 10 = 30V$ , also, transform the independent Voltage Source 15V series with 3Ω to an independent Current Source  $I = \frac{15}{3} = 5A$ : show in FIG 1.

Next, we combine two parallel resistor 3Ω and 6Ω equivalent to  $\frac{6 \times 3}{6 + 3} = 2Ω$ .

show in FIG 2

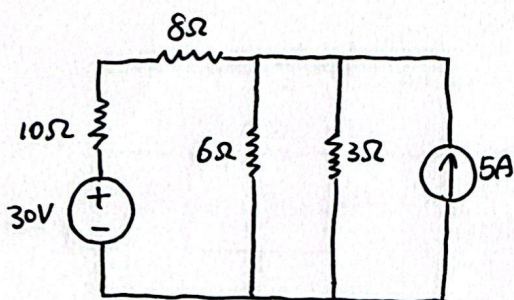


FIG 1



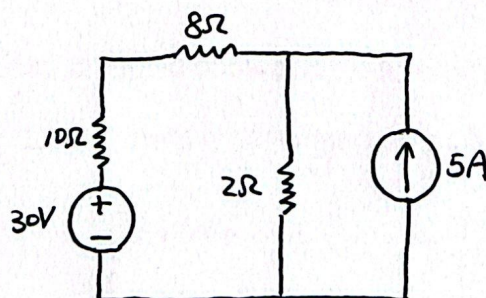


FIG 2

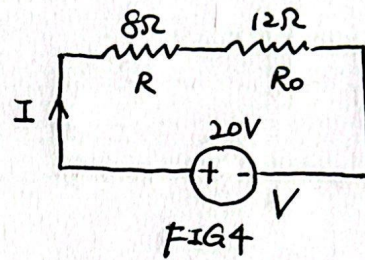



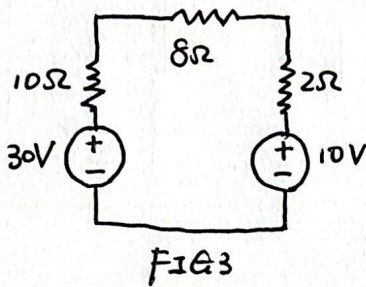
Then, we transform the independent current source  $5A$  parallel with  $2\Omega$  in FIG2 to an independent Voltage Source  $V = 5 \times 2 = 10V$ . Show in FIG3.  
Combine two series resistors  $2\Omega$  and  $10\Omega$ , two Voltage Sources  $10V$  and  $30V$  in FIG3, show in FIG4.



Finally, the current absorbed by  $8\Omega$  resistor is  $I = \frac{V}{R+R_0} = \frac{20}{8+12} = \boxed{1A}$   
the power absorbed by  $8\Omega$  resistor is  $P = VI = I^2R = \boxed{8W}$

### Exercise 2.3 (25%)

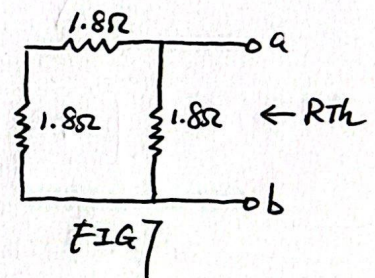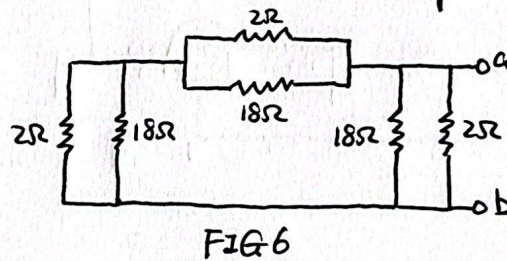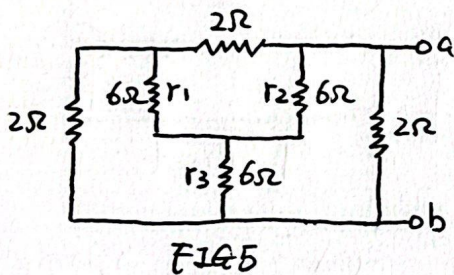(a) (20%) First, we find  $R_{Th}$ . Shut off all independent source: show FIG5



using  $Y-\Delta$  transformation, turn  $Y(r_1, r_2, r_3)$  into  $\Delta(R_1, R_2, R_3)$ :


$$R_1 = \frac{r_1 r_2 + r_2 r_3 + r_3 r_1}{r_1} = 18\Omega. \quad \text{Similarly, } R_2 = R_3 = 18\Omega \text{ (symmetry)}$$

the circuit is equivalent to FIG6. Combine parallel resistor. FIG7

$$2\Omega \parallel 18\Omega = \frac{2 \times 18}{2+18} = 1.8\Omega$$

$$\text{So, } R_{Th} = 1.8 \parallel (1.8 + 1.8) = 1.8 \parallel 3.6 = \frac{1.8 \times 3.6}{1.8+3.6} = 1.2\Omega$$

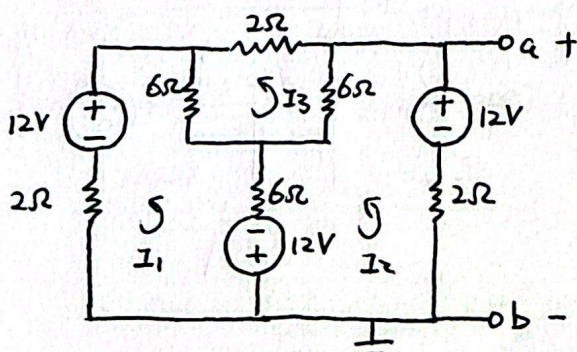Next, we find  $V_{Th}$ , let a-b become a open circuit,  $V_{ab} = V_{Th}$ .



mesh analysis by inspection:

$$\begin{bmatrix} 2+6+6 & -6 & -6 \\ -6 & 2+6+6 & -6 \\ -6 & -6 & 2+6+6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} -24 \\ 24 \\ 0 \end{bmatrix}$$


$\Delta = 800$   
 $\Delta_1 = -960$   
 $\Delta_2 = 960$   
 $\Delta_3 = 0$



$$\text{So, } I_1 = \frac{\Delta_1}{\Delta} = -1.2A, I_2 = \frac{\Delta_2}{\Delta} = 1.2A, I_3 = \frac{\Delta_3}{\Delta} = 0A.$$

$$\frac{V_{ab}-12}{2} = -I_2, \text{ so, } V_{Th} = V_{ab} = 12 - 2I_2 = 9.6V. \text{ Thevenin equivalent circuit is shown in FIG8.}$$

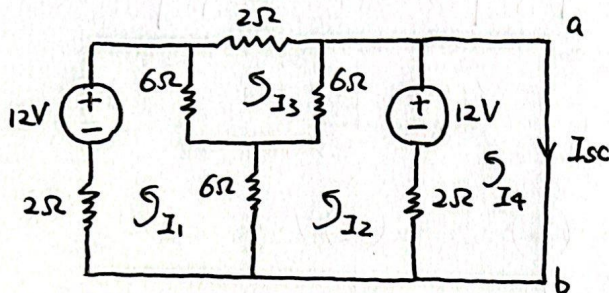Then, we find  $I_N$ , let a-b become an short circuit. ( $R_N = R_{Th} = 1.2\Omega$ ).



mesh analysis by inspection:

$$\begin{bmatrix} 2+6+6 & -6 & -6 & 0 \\ -6 & 2+6+6 & -6 & -2 \\ -6 & -6 & 2+6+6 & 0 \\ 0 & -2 & 0 & 2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \end{bmatrix} = \begin{bmatrix} -24 \\ 24 \\ 0 \\ -12 \end{bmatrix}$$



$$\begin{aligned} \Delta &= 960 \\ \Delta_1 &= -3456 \\ \Delta_2 &= -1920 \\ \Delta_3 &= -2304 \\ \Delta_4 &= -7680 \end{aligned}$$

$$\text{So, } I_1 = \frac{\Delta_1}{\Delta} = -3.6A, I_2 = \frac{\Delta_2}{\Delta} = -2A, I_3 = \frac{\Delta_3}{\Delta} = -2.4A, I_4 = \frac{\Delta_4}{\Delta} = -8A.$$

$I_N = I_{sc} = -I_4 = 8A$ . Norton equivalent circuit is shown in FIG9.

Also,  $R_N$  and  $I_N$  can be derived from  $R_{Th}$  and  $V_{Th}$  (Source transformation).

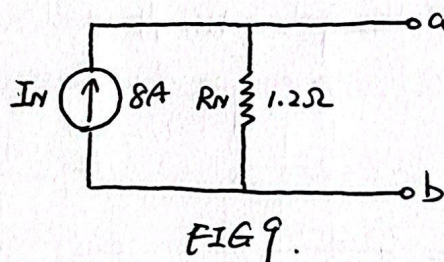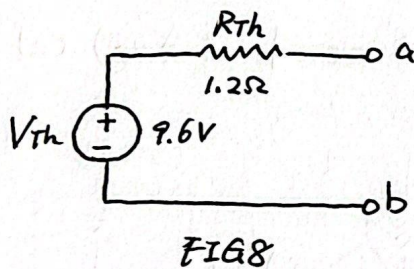
$$R_N = R_{Th}, I_N = \frac{V_{Th}}{R_{Th}}.$$



$$(b) (5\%) P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{9.6^2}{4 \times 1.2} = 19.2W \text{ when } R = R_{Th} = 1.2\Omega$$

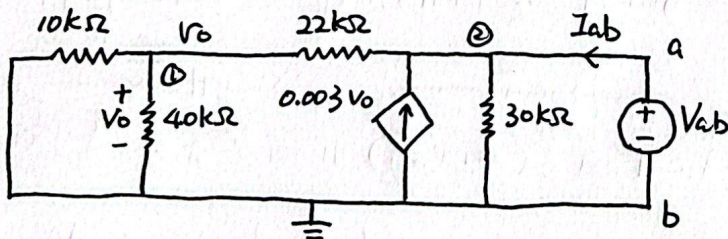Exercise 2.4 (20%).

We first use Thevenin's Thm to find the equivalent circuit: for  $R_{Th}$ :



we connect an independent voltage source  $V_{ab}$  between a and b, the current is  $I_{ab}$ , then  $R_{Th} = \frac{V_{ab}}{I_{ab}}$

$$\frac{V_0}{40} + \frac{V_0}{10} + \frac{V_0 - V_{ab}}{22} = 0, \text{ node ①} \Rightarrow V_0 = \frac{4}{15} V_{ab}$$


$$\frac{V_{ab}}{30} + \frac{V_{ab} - V_0}{22} = 3V_0 + 1000I_{ab} \text{ node ②}$$

$$\Rightarrow I_{ab} = \left( \frac{1}{30} + \frac{1 - \frac{4}{15}}{22} - 3 \times \frac{4}{15} \right) V_{ab} = -\frac{11}{15} V_{ab}.$$

$$\Rightarrow R_{Th} = \frac{V_{ab}}{I_{ab}} = -\frac{15}{11} \times 10^3 \Omega = -\frac{15}{11} k\Omega \doteq -1.364 k\Omega$$



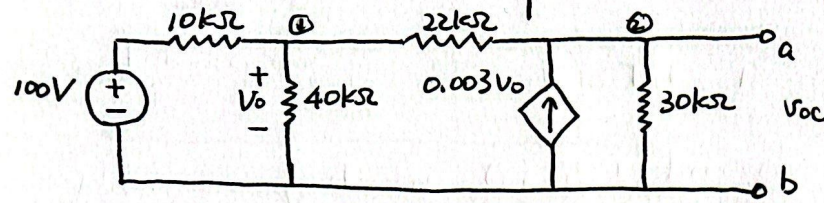
Next, we make ab an open circuit,  $V_{Th} = V_{oc}$ :



$$\begin{cases} \frac{V_o}{40} + \frac{V_o - 100}{10} + \frac{V_o - V_{oc}}{22} = 0, \text{ node ①} \\ \frac{V_{oc} - V_o}{22} + \frac{V_{oc}}{30} = 3V_o, \text{ node ②} \end{cases}$$

$$\Rightarrow \begin{cases} \frac{15}{88} V_o - \frac{1}{22} V_{oc} = 10 \\ -\frac{67}{22} V_o + \frac{13}{165} V_{oc} = 0 \end{cases} \Rightarrow \begin{cases} V_o = -\frac{208}{33} V \\ V_{oc} = -\frac{2680}{11} V \end{cases}$$

So, the equivalent circuit is:

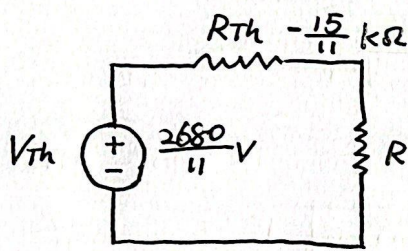


$$P = I^2 R = \frac{V_{Th}^2 R}{(R + R_{Th})^2}$$

when  $R = -R_{Th} = \frac{15}{11} k\Omega \doteq 1.364 k\Omega$ ,

$P \rightarrow \infty$ . So,  $P_{max}$  doesn't not exist.

### Exercise 2.5 (25%)

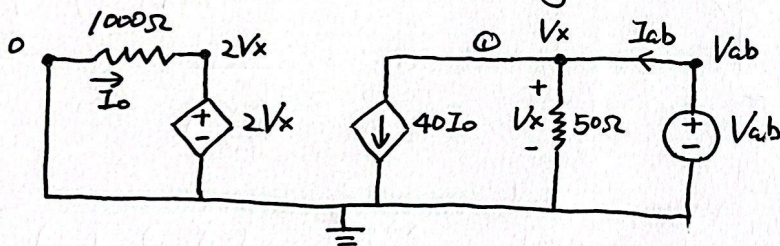
(a) (20%) First, we derive  $R_{Th}$  by shutting off all independent source and add voltage  $V_{ab}$  source between a-b.  $R_{Th} = \frac{V_{ab}}{I_{ab}}$



$$\begin{cases} V_{ab} = V_x \\ \frac{0 - 2V_x}{1000} = I_o \\ \frac{V_x}{50} + 40I_o = I_{ab}, \text{ node ①} \end{cases}$$

$$\Rightarrow \frac{V_{ab}}{50} - \frac{40 V_{ab}}{500} = I_{ab}, \quad -\frac{3}{50} V_{ab} = I_{ab}, \quad R_{ab} = -\frac{50}{3} \Omega = R_{Th}$$

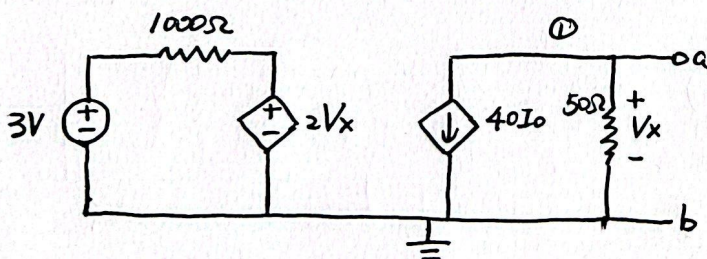Next, we derive  $V_{Th}$  by make a-b open circuit,  $V_{Th} = V_{oc} = V_x$




$$\begin{cases} I_o = \frac{3 - 2V_x}{1000} \\ \frac{V_x}{50} = -40I_o, \text{ node ①} \end{cases}$$

$$\Rightarrow V_{Th} = V_x = V_{oc} = 2V$$

So, the Thevenin equivalent circuit is shown in FIG 10, then, we derive

$I_N$  by make a-b a short circuit:





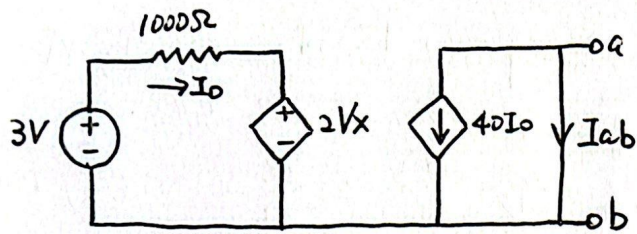

In this case,  $V_x = V_{ab} = 0$ ,  $I_N = I_{ab}$ .

$$\begin{cases} I_o = \frac{3}{1000} \\ I_{ab} = -40I_o = -40 \times \frac{3}{1000} = -0.12 \text{ A} = I_N. \end{cases}$$

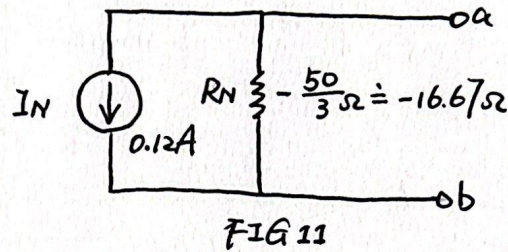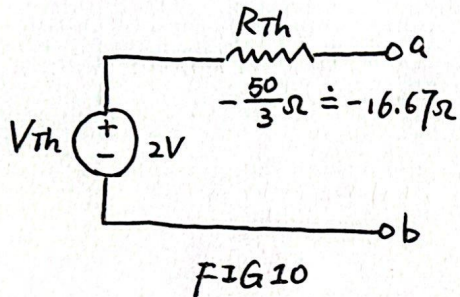So, the Norton equivalent circuit is shown in FIG 11.



(b) (5%). First, calculate the  $I$  using Norton equivalent circuit.

$$I = \frac{V}{R} = \frac{2}{10 - \frac{50}{3}} = -0.3 \text{ A}.$$

Next, calculate the power  $P = VI = I^2 R = 0.3^2 \times \frac{50}{3} = \boxed{0.9 \text{ W}}$