

VE215 Introduction to Circuits

Instructor: Rui Yang



JOINT INSTITUTE
交大密西根学院

About the instructor

- 2011.08 – 2016.05. Ph.D., Electrical Engineering, Case Western Reserve University



- 2016.07 – 2018.07. Postdoc Fellow, Electrical Engineering, Stanford University



- 2018.08 – 2022. Assistant Professor, UM-SJTU II, Shanghai Jiao Tong University, Shanghai, China
- 2022 – Now. Associate Professor, UM-SJTU II, Shanghai Jiao Tong University, Shanghai, China
 - Instructor of VE215
 - Instructor of ECE4230J
 - Instructor of VE510/ECE6209J
 - Former Instructor of VE320



Course schedule

- Lectures: Tuesday 4:00 – 5:40 pm (Beijing time)
Thursday 4:00 – 5:40 pm (Beijing time)
- Location: DZY-2-206 (at least weeks 1-6)
- My office hours: Tuesday 1-3pm. Or ping me on Feishu or Piazza anytime if you have questions.
- Recitation: TBD
- TA:
 - Mingnan Yao (姚明楠) , Email: yao_mn@sjtu.edu.cn
 - Jingyu Liu (刘璟昱) , Email: liujingyu@sjtu.edu.cn

My contact

- Office location:
Rm. 434, UM-SJTU JI Building (You can discuss with me online through Feishu, email or Piazza)
- Office tel:
3420-8540 ext. 4341
- Email:
rui.yang@sjtu.edu.cn

Feishu group



ECE2150J Summer 20...

上海交通大学



仅限企业内部成员加入


该二维码 1 年内 (2026/4/29前)有效

Course expectation and requirement


- Pre-requisites: VV156 or VV186, VG101
- Co-requisites: VP240 or VP260
- Basic college math and physics
 - Scalar & Vector
 - Differentiation & Integration
 - Electric Charge
 - Current & Voltage

Textbook


Main Textbook

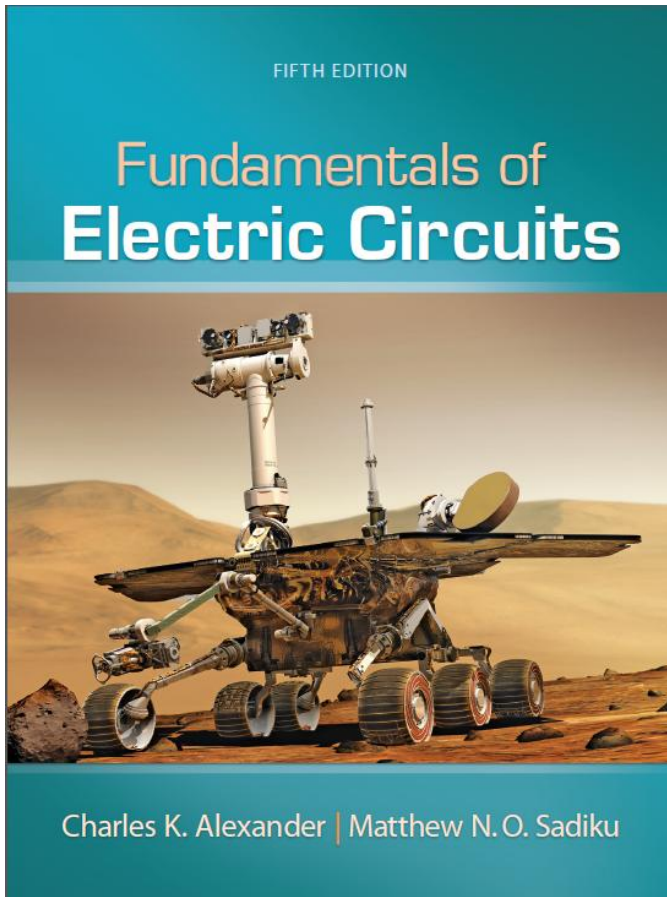

Laboratory book

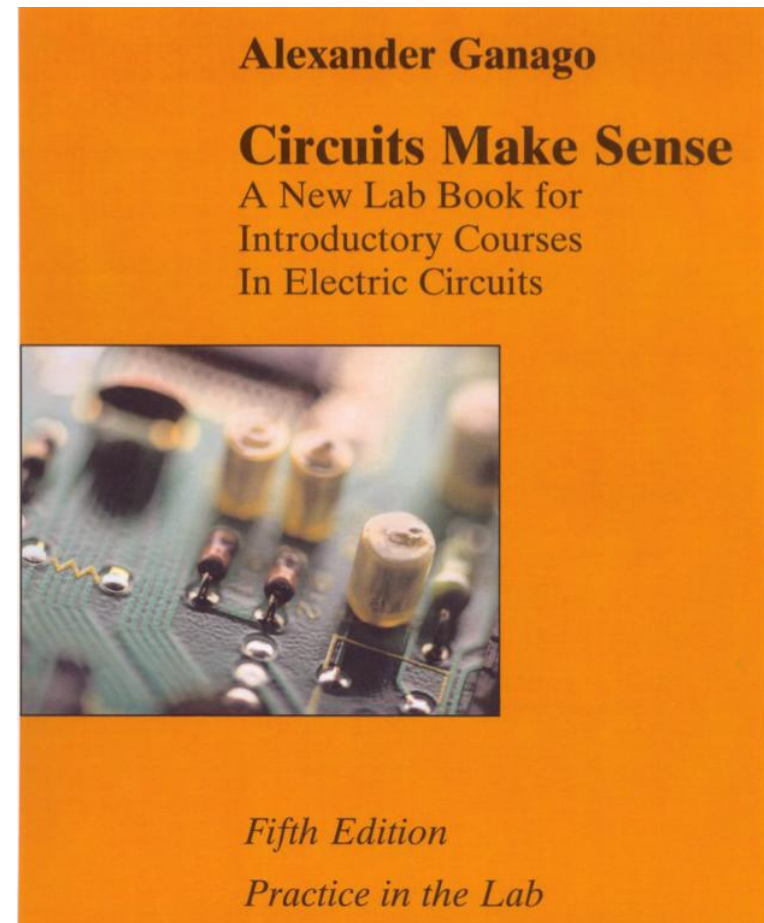

Computer Aided Design - CAD

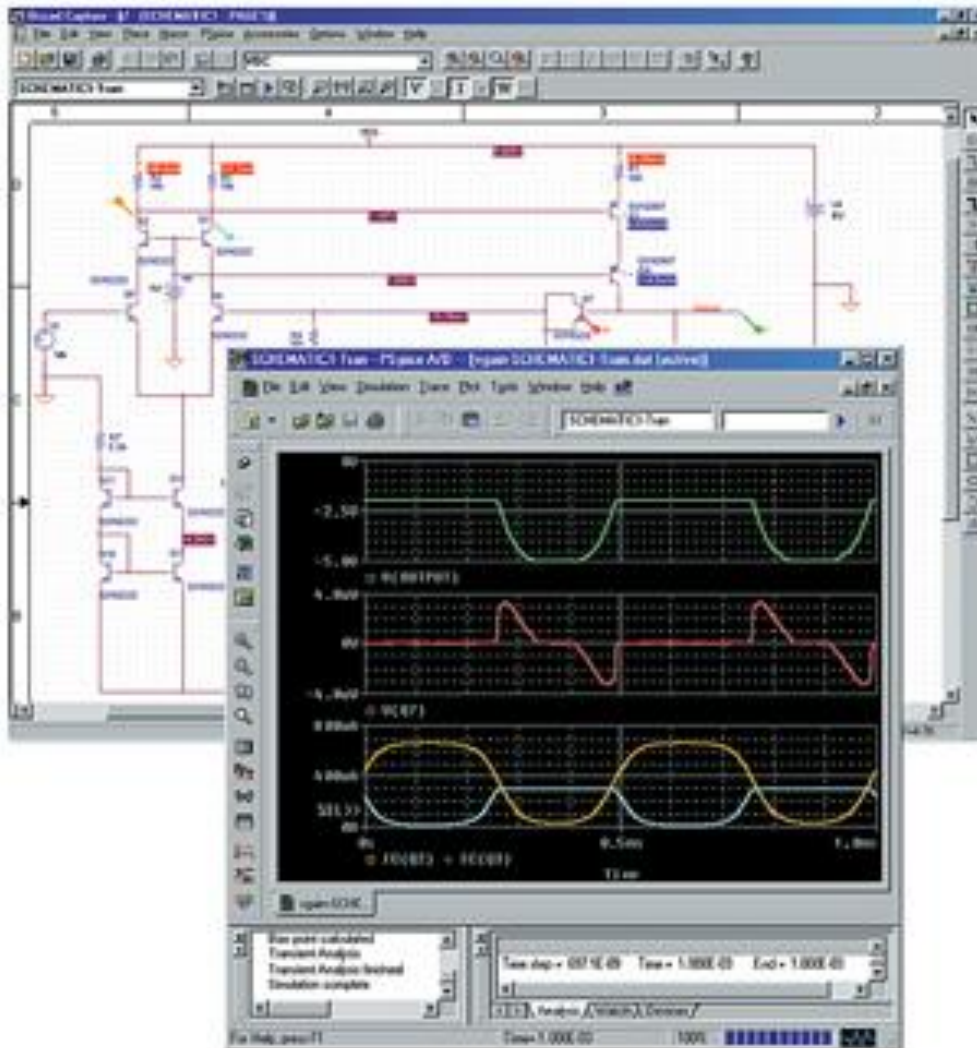

- PSpice CAD tool to simulate most analog and digital circuits.
- Demo version available online for free.
<https://www.orcad.com/pspice-free-trial>
- Download link of PSpice will also be posted on Canvas for convenience.
- Some tutorial posted on Canvas.
- Also check online tutorials, such as <https://www.bilibili.com/video/BV1Wb41177J1>

Lab

- 9 labs in total, ~3 hours each
- Time: will be announced
- Change in the policy of report:

Previous: pre-lab and post-lab,

Now: 1 single report is enough. But make sure you read the materials carefully before the lab.

- Try to finish the lab report during the lab sessions. If you cannot finish it within the lab session, notify the TAs and send to them asap.
- Lab: You are recommended to get familiar with PSPICE before the lab sessions.

Grading policy

- Ve215 has about 8 problem sets (homework assignments), random in-class quizzes (also for checking attendance), 9 labs, and 2 exams:
- In-class Quizzes: 10%
- Problem Sets: 10%
- Labs: 15%
- Exam 1 (Midterm Exam): 30%
- Exam 2 (Final Exam): 35%

The JI Honor Code

- Personal integrity as students and professionals.
- Respect other people and their work.
- Respect yourself and your own efforts.
- Applicable to all your academic activities here, including homework, quizzes, lab reports, projects and exams.
- Violations will be reported to the Honor Council.
 - Copy other student's homework, quizzes, lab reports, exams.
 - Illegal copy of online resource and academic literatures.
 - Helping others on the abovementioned activities.
 - Fake ID for exams.

Class rules

- Please do not come in late and do not get up to leave until the class is dismissed.
- You are responsible for all material covered in class, whether or not it is in the book.

Homework rules

- Homework will be assigned online at Canvas as scheduled. They are usually due one week later or specified otherwise. One day automatic grace period. Second day late penalty - 25%, later no credit.
- Students should complete the homework independently. Copy of others' homework is not allowed and is a violation to the Honor Code.
- Students on campus should hand in the homework in person. Students outside of China can take a photo of the homework or type them electronically, and then upload on Canvas.
- Solutions will be posted on Canvas about two days after the due date.

Quiz

- We will have random quizzes.
- Open book, open discussion.
- We will not focus on whether your final answer is correct but we will mainly check your solution process, *i.e.*, You need to write your thinking steps related to the question. Do not simply write the answer, or simply copy the textbook equations without your thoughts.
- Also for checking attendance.
- No make-up quizzes are allowed.
- Handing in the quiz deserves half of the total points automatically (blank page doesn't count).

Exam rules

- There will be one midterm exam and one final exam.
- Each lasts 100 minutes, will be conducted offline.
- Students should complete the exam independently. No talk and collaboration are allowed.
- Closed book, cheat sheet may be allowed.
- No electronic devices except basic calculators will be allowed to use.

Tentative schedule: (subject to change)

Week	Date	Lecture Topics	Homework: main content; may vary slightly	Labs
1	May 13	Introduction to Ve215, Ch1. Basic concepts		
	May 15	Ch2. Basic laws		
2	May 20	Ch3. Methods of analysis		
	May 22	Ch3. Methods of analysis	HW1: Chaps. 1-3	
3	May 27	Ch4. Circuit theorems		Lab1
	May 29	Ch5. Operational amplifiers	HW2: Chap. 4	
4	Jun 3	Ch5. Operational amplifiers		Lab2
	Jun 5	Ch6. Capacitors and inductors	HW3: Chaps. 5,6	
5	Jun 10	Ch7. First-order circuits		Lab3
	Jun 12	Ch8. Second-order circuits		
6	Jun 17	Ch8. Second-order circuits	HW4: Chaps. 7,8	Lab4
	Jun 19	Ch9. Sinusoids and phasors		
7	Jun 24	No lecture, Midterm Exam		
	Jun 26	Ch9. Sinusoids and phasors		
8	Jul 1	Ch10. Sinusoidal steady-state analysis	HW5: Chaps. 9,10	Lab5
	Jul 3	Ch11. AC power analysis		
9	Jul 8	Ch11. AC power analysis		Lab6
	Jul 10	Ch12. Three-phase circuits		
10	Jul 15	Ch12. Three-phase circuits	HW6: Chaps. 11,12	Lab7
	Jul 17	Ch13. Magnetically coupled circuits		
11	Jul 22	Ch13. Magnetically coupled circuits		Lab8
	Jul 24	Ch13. Magnetically coupled circuits	HW7: Chap. 13	
12	Jul 29	Ch14. Frequency response		Lab9
	Jul 31	Ch14. Frequency response	HW8: Chap. 14	
13	Aug 4-8	No lecture, Final Exam		




What are circuits?

Circuit – Electrical Engineering


■ In electrical engineering

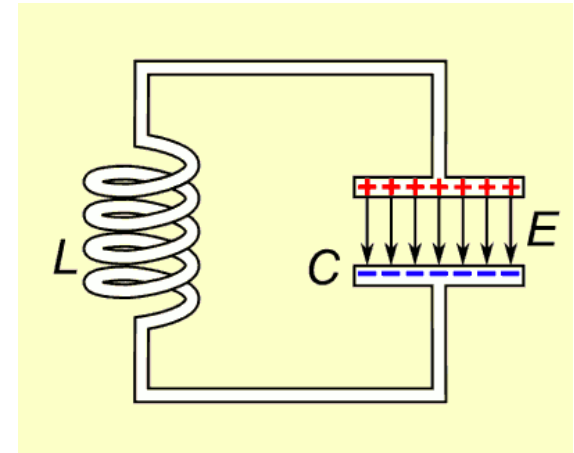- Circuit analysis
- Analog circuit or Digital circuit
- Integrated circuit
 - Mixed-signal integrated circuit
- Asynchronous circuit or Synchronous circuit
- Printed circuit board (PCB)
- Series and parallel circuits
- Telecommunication circuit
- Circuit diagram
- Balanced circuit
- LC circuit



Electrical circuit

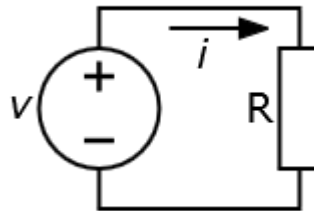
- An **electrical circuit** is a path in which electrons from a **voltage or current source** flow.
- Electric current flows in a closed path called an electric circuit.
- A simple electrical circuit. This circuit has a power source, a complete path for electrons to flow, and a resistor as the load.



Electrical circuits and electronic circuits

■ Electrical circuits

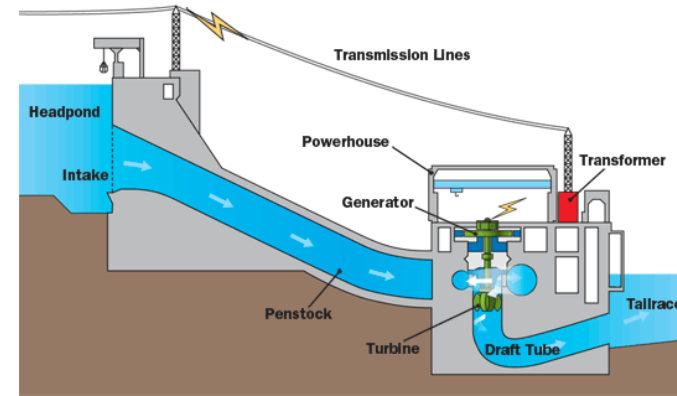- Usually use alternating current sources
- Load: refrigerators, televisions, or microwave ovens; the output of a hydroelectric power generating station.



■ Electronic circuits

- Usually use low voltage direct current sources
- Load: the flash in a digital camera; the microprocessors.

More on electronic circuit

■ Definition:

An electronic circuit is composed of individual electronic components, such as resistors, transistors, capacitors, inductors and diodes, connected by conductive wires or traces through which electric current can flow.

■ Function:

The combination of components and wires allows various simple and complex operations to be performed:

- signals can be amplified
- computations can be performed
- data can be moved from one place to another.

More on electronic circuit

■ Print circuit board (PCB):


Circuits can be constructed of discrete components connected by individual pieces of wire, but today it is much more common to create interconnections by photolithographic techniques on a laminated substrate (a printed circuit board or PCB) and solder the components to these interconnections to create a finished circuit.



More on electronic circuit

- Integrated circuit (IC)

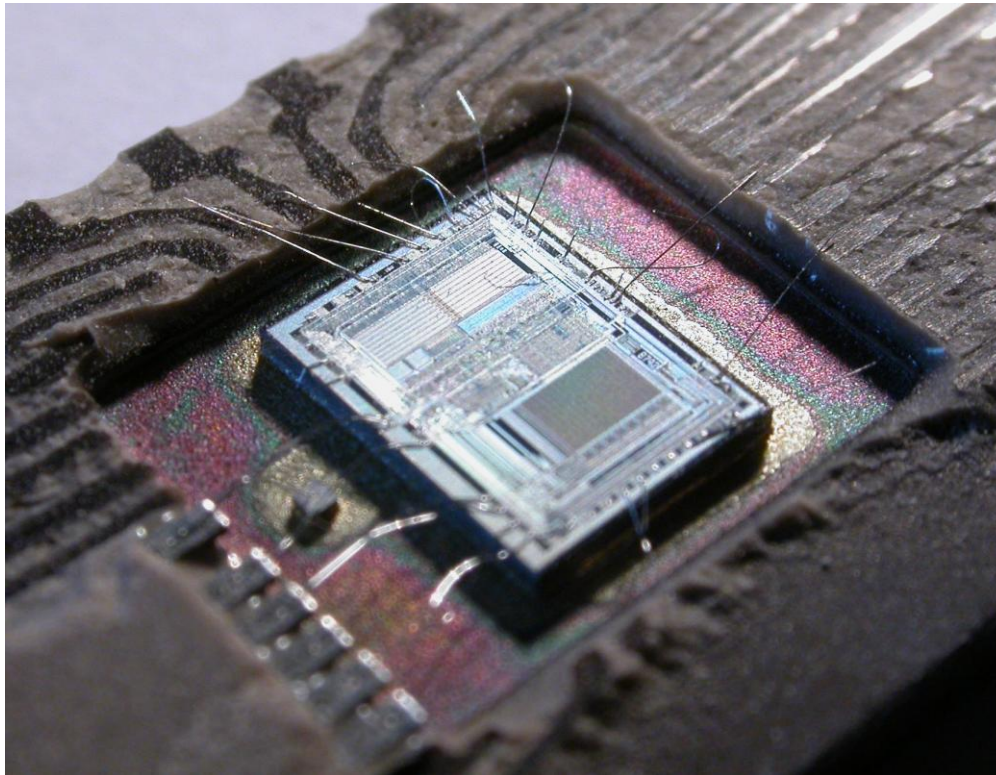In an integrated circuit or IC, the components and interconnections are formed on the same substrate, typically a semiconductor such as silicon or (less commonly) gallium arsenide.




The die from an Intel 8742, an 8-bit microcontroller that includes a CPU, 128 bytes of RAM, 2048 bytes of EPROM, and I/O in the same chip.

Categories of electronic circuit

- Analog circuits
- Digital circuits
- Mixed-signal circuits (a combination of analog circuits and digital circuits).

Analog circuits

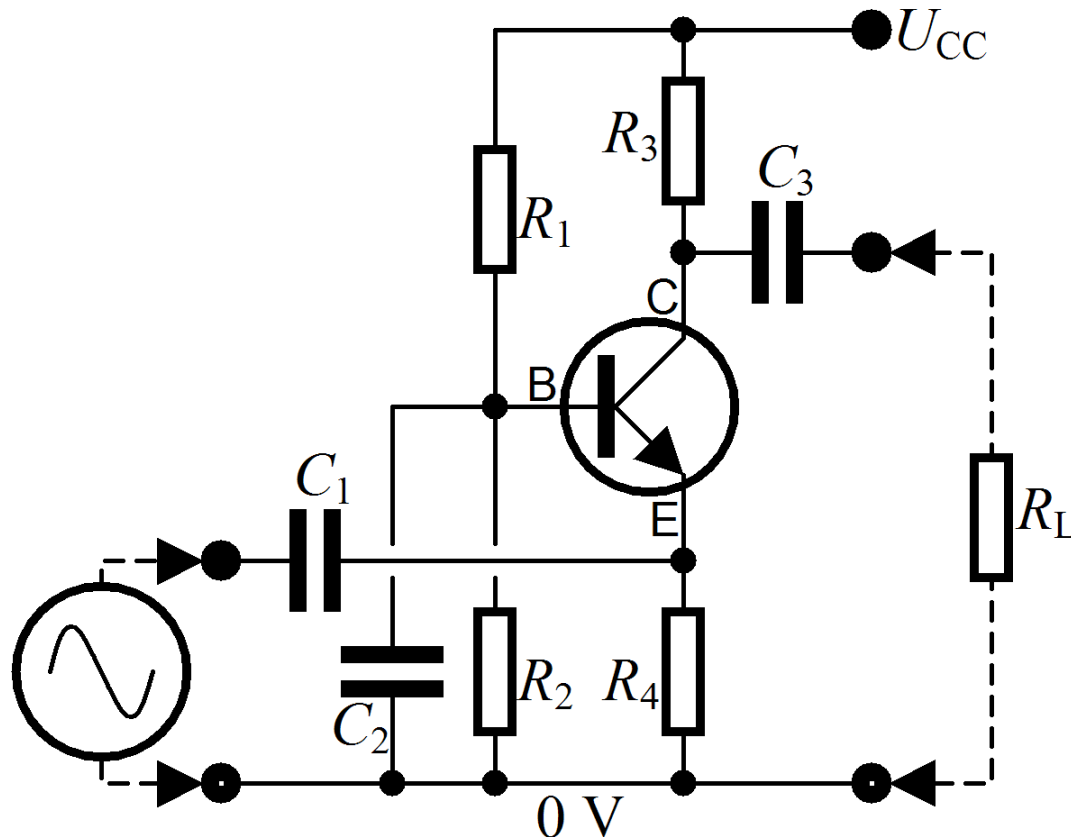- Analog electronic circuits are those in which current or voltage may vary continuously with time to correspond to the information being represented.




A circuit diagram representing an analog circuit, in this case a simple amplifier


Lumped and distributed

- A lumped system is one in which the dependent variables of interest are a function of time alone.
- A distributed system is one in which all dependent variables are functions of time and one or more spatial variables.

Distributed

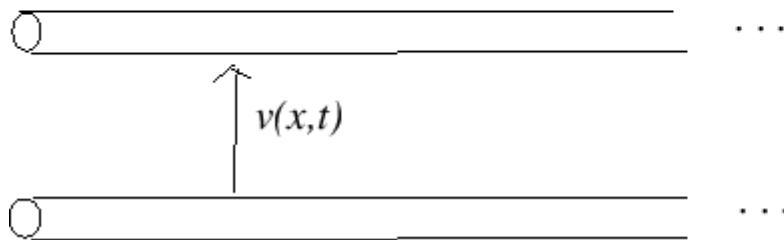

Lumped

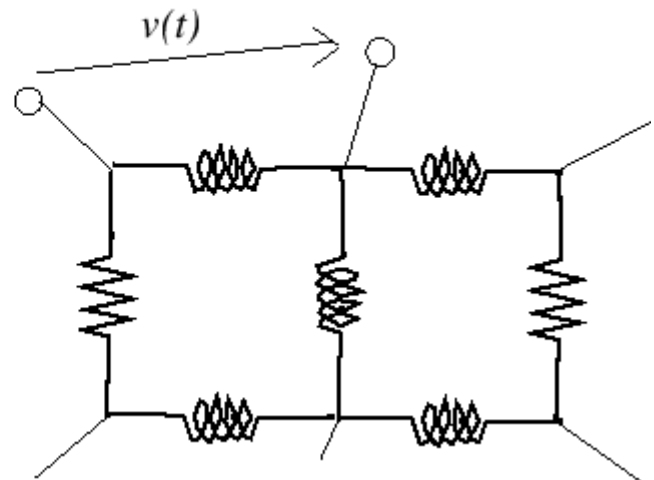

Analog circuits

- Analog circuit analysis employs Kirchhoff's circuit laws: all the currents at a node (a place where wires meet), and the voltage around a closed loop of wires is 0.
- Applicability/Validity
 - L_c : circuit's characteristic length; λ : circuit's operating wavelength
 - The lumped element model ($L_c \ll \lambda$):
 - Ignores the finite time it takes signals to propagate around a circuit.
 - The attributes of the circuit elements are **concentrated into idealized electrical components** (resistors, capacitors, and inductors, etc.) joined by a network of **perfectly conducting wires**.
 - Distributed circuit model ($L_c \sim \lambda$):
 - When the circuit size is comparable to a wavelength of the relevant signal frequency
 - Such considerations typically become important for circuit boards at frequencies above a GHz.

Digital circuits

- In digital electronic circuits, electric signals take on discrete values, to represent logical and numeric values.
- In the vast majority of cases, binary encoding is used: one voltage (typically the more positive value) represents a binary '1' and another voltage (usually a value near the ground potential, 0 V) represents a binary '0'.
- Digital circuits make extensive use of transistors, interconnected to create logic gates that provide the functions of Boolean logic: AND, NAND, OR, NOR, XOR and all possible combinations thereof.

Digital circuits

■ Advantages over analog circuits:

- Each logic gate regenerates the binary signal, so the designer need not account for distortion, gain control, offset voltages, and other concerns faced in an analog design.
- Extremely complex digital circuits (billions of logic elements integrated on a single silicon chip) can be fabricated at low cost.


■ Digital circuitry

- General purpose computing chips, such as microprocessors
- Custom-designed logic circuits, known as application-specific integrated circuit (ASICs).
- Field-programmable gate arrays (FPGAs), chips with logic circuitry whose configuration can be modified after fabrication

■ Applications

- Ubiquitous in modern electronic devices

Digital circuits-microprocessor

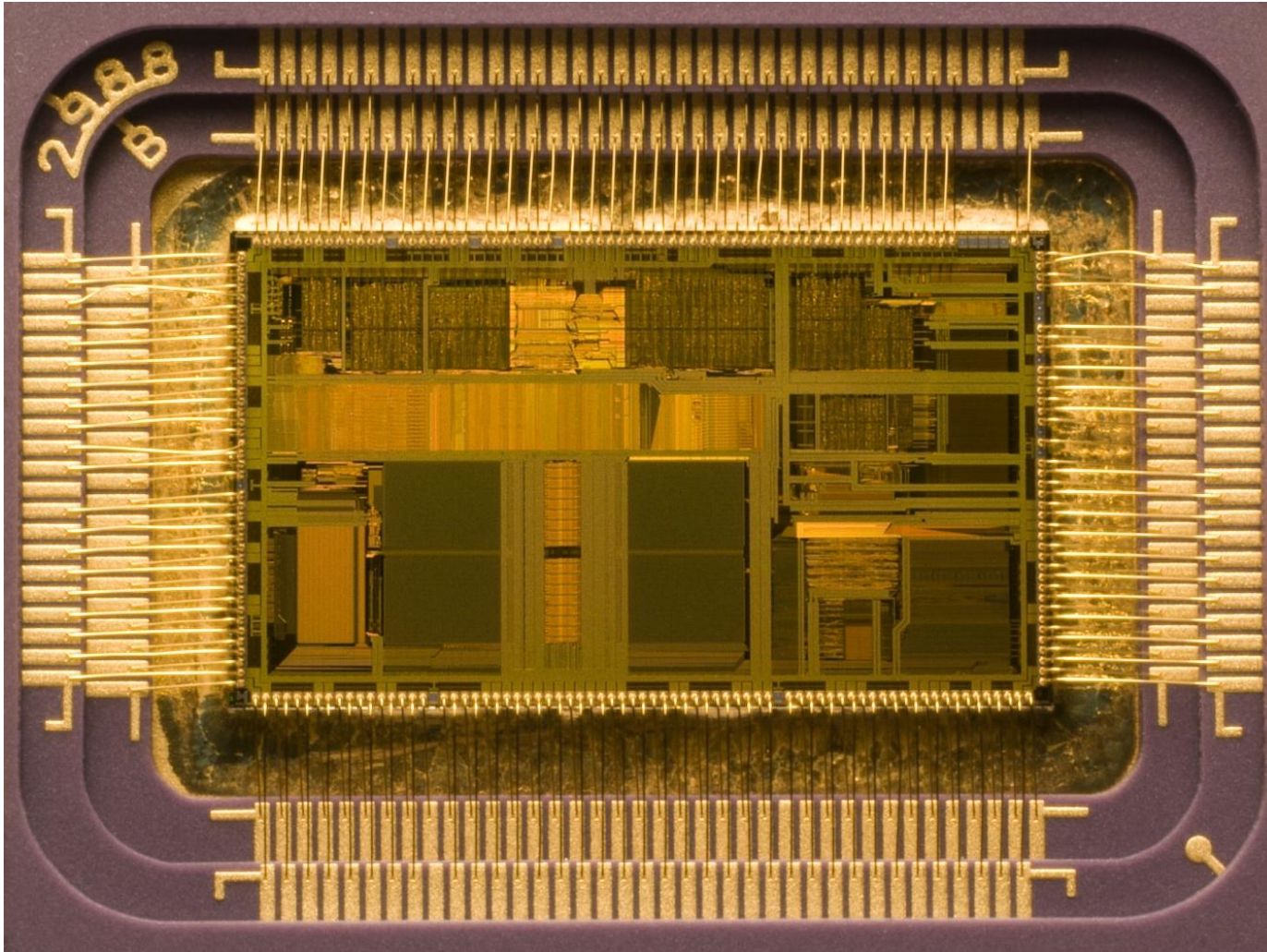

Intel 80486DX2
microprocessor

Digital circuits-FPGA



FPGA from Altera






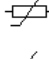

 
 
 

 

 

 



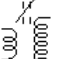









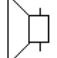
 
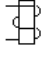
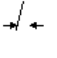

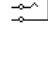


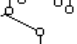
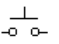
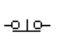

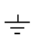
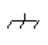


FPGA from Xilinx

Mixed-signal circuits






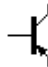

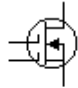
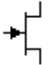





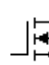
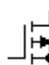








- Definition: Mixed-signal or hybrid circuits contain elements of both analog and digital circuits.
- Examples: Comparators, timers, phase-locked loops, analog-to-digital converters, and digital-to-analog converters (E.g., A laser marking machine).
- Most modern radio and communications circuitry uses mixed signal circuits. For example, a receiver.
 - Analog: amplification, frequency conversion
 - Digital: signal processing




Circuit symbols-passive components

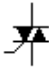Resistor	Variable Resistor	Preset	Thermistor	
				
<hr/>				
Capacitor	Electrolytic Capacitor	Variable	Trimmer	Ganged Variable Capacitors
				
<hr/>				
Air Wound Coils	Iron Core	Dust Core	Preset	Variable Inductor
				
<hr/>				
Transformer	Centre Tapped Transformer	IFT	Variable IFT	
				
<hr/>				
Dynamic MIC	ECM MIC	Loudspeaker	Piezo	Crystal
				
<hr/>				
Indicator Lamps		Motor	Voltmeter	Terminal or Test Point
				
<hr/>				
Battery	Relay	Alternative Relay Contacts	Fuse	Stereo Jack
				
<hr/>				
Switch	SPDT Switch	Rotary Switch	Push Button Switch	NC PBS
				
<hr/>				
Aerial	Earth	Chassis	Wires (Joined)	(Not Joined)
				

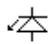Circuit symbols-active components

Diode	Triode	Tetrode	Pentode
			
Transistors		Unijunction Transistor	Double Gate MOSFET
			
Field Effect Transistors		Darlington Transistors	
			
MOSFETS Depletion Mode		MOSFETS Enhancement Mode	
			
Schottky Diode	Diac	Triac	SCR
			
Diode	LED	Zener	Varactor
			

Circuit types


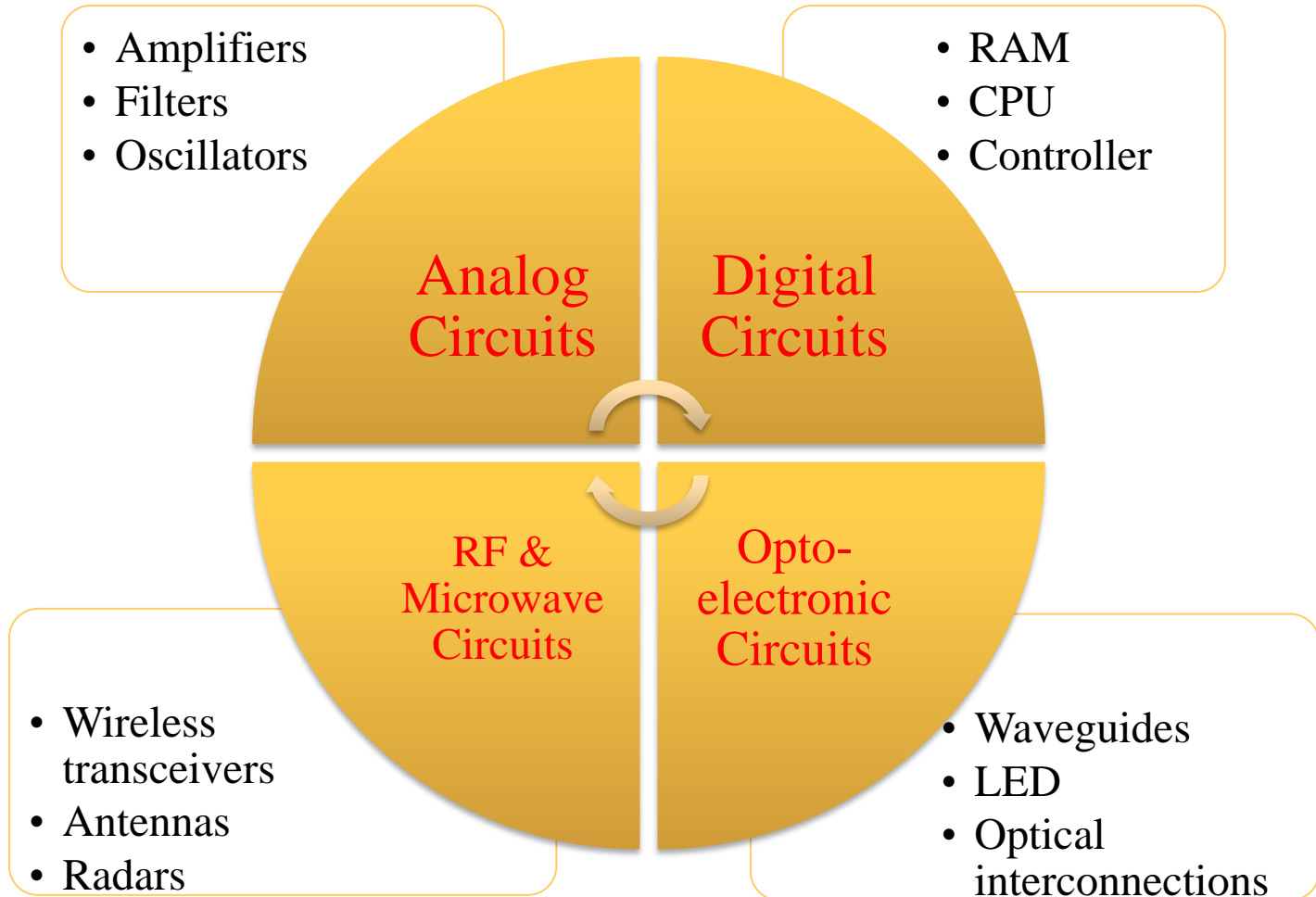


Circuit types




Electrical
Circuits

Magnetic
Circuits

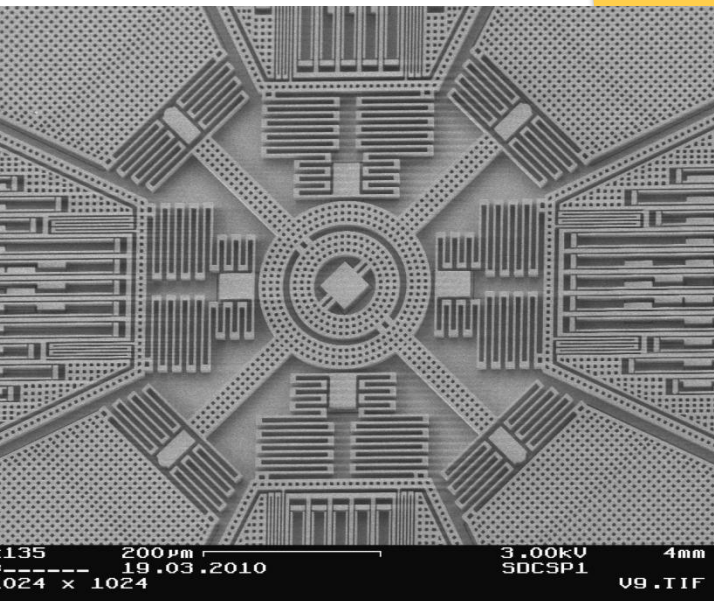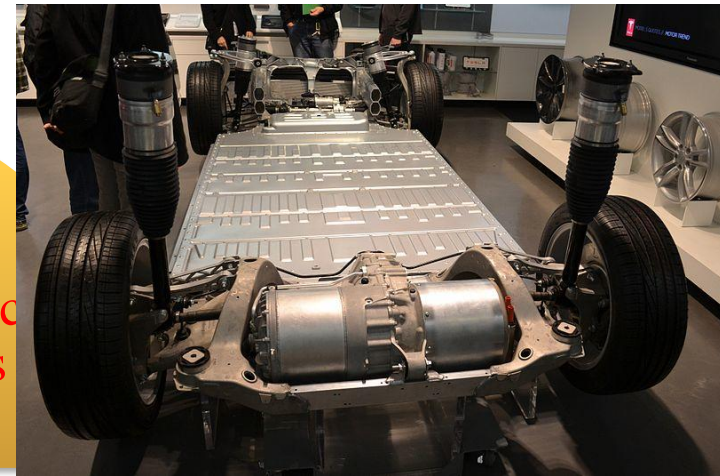


Mechanical
Circuits

Bio
Circuits

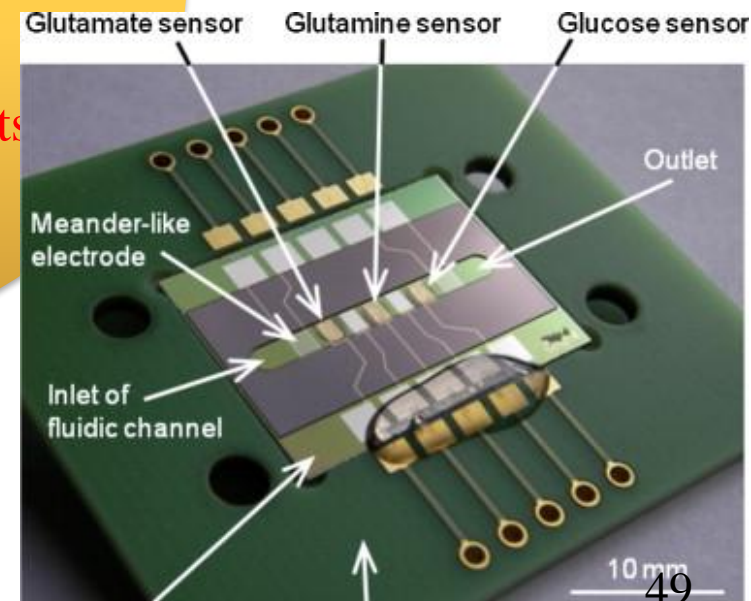

Circuit hierarchy

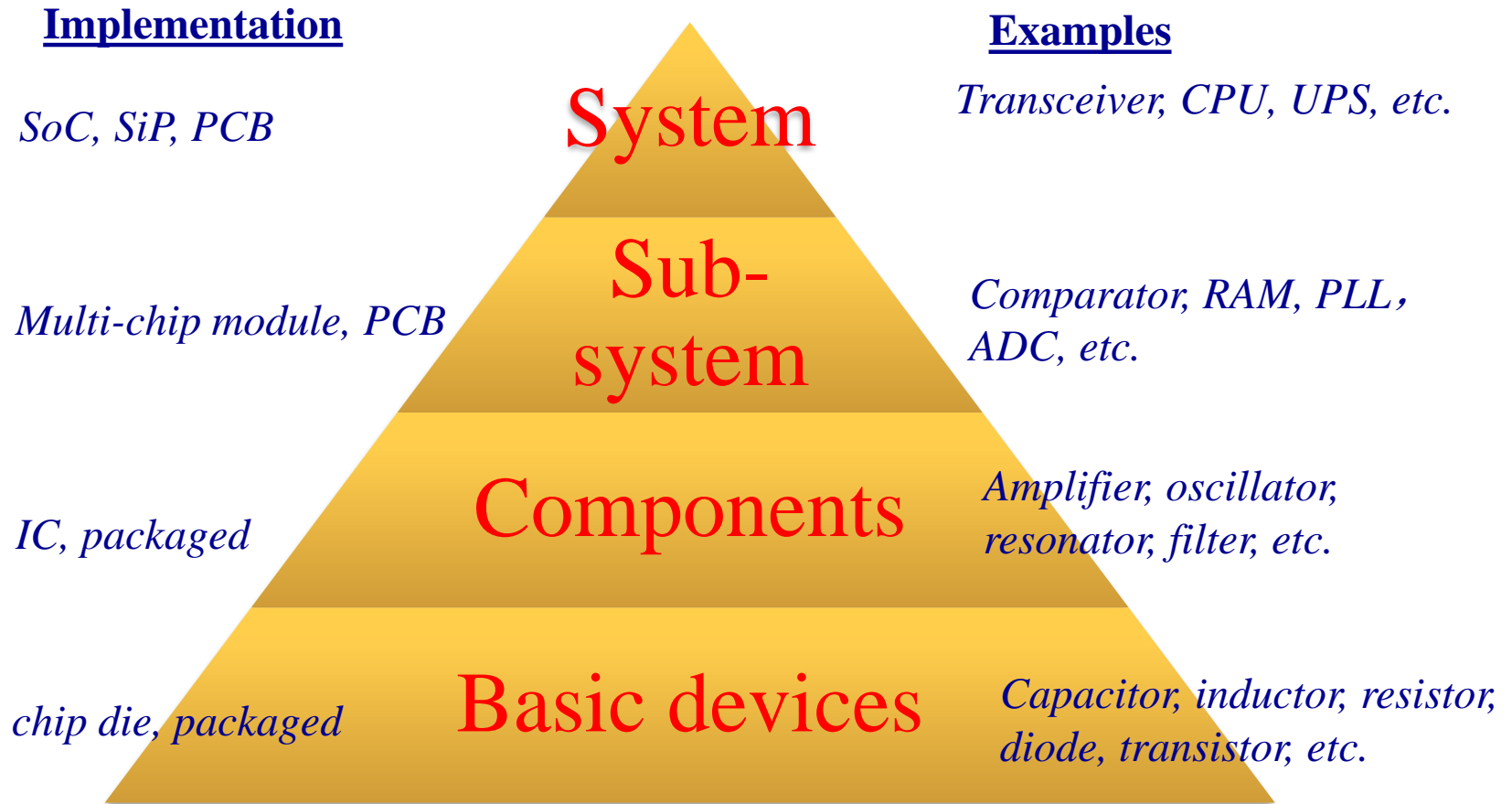

Circuit related curriculum in JI

Freshmen

- Math
- Physics
- Programming

Sophomore

- **VE215**
Introduction to Circuits
- **VE216**
Signal and System
- **VE230**
Electromagnetics
- **VE270**
Introduction to Logic Design

Junior

- **VE311**
Analog circuits
- **VE320**
Semiconductor
- **VE330**
Electromagnetics II
- **VE312**
Digital Integrated Circuits
- **VE334**
Optics

Senior

- **VE413**
Analog IC
- **VE411**
RF Microwave Circuits
- **VE427**
VLSI I
- **VE434**
Photonics

